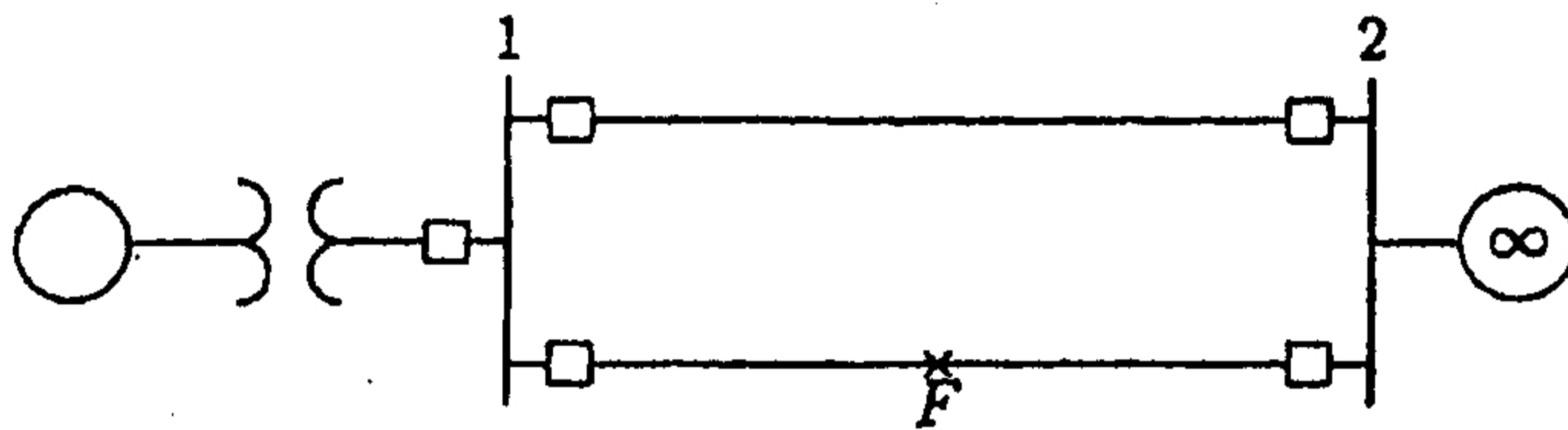


1. (20%) One 60 Hz machine system connected to infinite bus is shown below. Assume the input mechanical power P_m is constant, the generator is delivering power steadily with a power angle δ_0 . Consider a temporary three-phase bolted fault occurs at point F where F is at some distance away from the sending end. The fault is then cleared at power angle δ_C by removing the faulty line. Due to the energy conversion, the power angle reaches δ_{max} at the stable operating region. The power angle finally returns to a new stable operating point at δ_1 .



Please answer the following:

- I. (15%) Draw the power angle curves (electric power P_e vs. power angle δ), and power line P_m . Label the operating points associated with δ_0 , δ_C , δ_{max} , δ_1 on the curves.
 - II. (5%) Mark and discuss the areas for the stability criteria.
2. (20%) With the same 60Hz power system structure in the previous question, assume the generator has inertia constant $H=5\text{MJ/MVA}$, a direct transient reactance $X_d'=0.3$ pu is connected to a transformer with reactance $X_t=0.1$ pu. Between the transformer and infinite bus, a pair of transmission lines (each line's reactance is 0.6pu) are delivering real power $P_e=0.8$ pu and $Q=0.08$ pu to the infinite bus at a voltage of $V=1$ pu.
- I. (10%) Consider the first-order differential equation

$$\frac{dx}{dt} = f(x)$$

Express the solution $x(t)$ by using Euler's method and point out its flaw

- II. (10%) A sudden line trip occurs on one of the transmission line and the faulty line is removed immediately at $t=0$ second. Please find the power angle δ in degree and rotor speed deviation $\Delta\omega$ in rad/sec after the fault at $t=0.02$ second. Using the Euler method with a step size of $\Delta t=0.01$ second. Perform two iterations.

swing equation:
$$\frac{d^2\delta}{dt^2} = \frac{\pi f_0}{H} (P_m - P_{max} \sin\delta)$$

(背面仍有題目,請繼續作答)

3. (20%) The following data were obtained for a 20kVA, 60Hz, 2kV: 200V distribution transformer tested at 60Hz:


With high-voltage winding open-circuited 240V 1A 120Watts

With low-voltage terminals short-circuited 50V 8A 280Watts

- (10%) Compute the efficiency at full-load current and the rated terminal voltage at 0.8 lagging power factor.
- (10%) Assume that the load power factor is varied while the load current and secondary terminal voltage are held constant. Use a phasor diagram to determine the load power factor for which the regulation is greatest. What is this regulation?

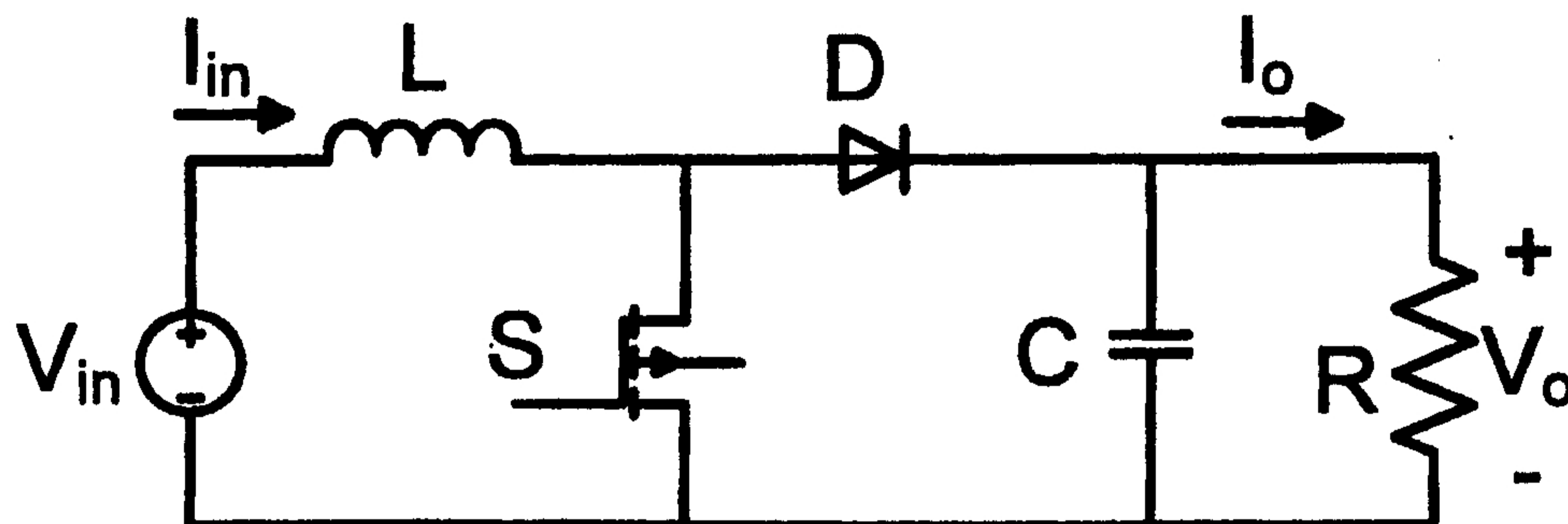4. (20%) As following figure, $V_{in}=10V$, $L=1mH$, $R=500\Omega$, the switching frequency is 100kHz and duty cycle of S is 50%.

- (10%) Is this converter operating in continuous mode or discontinuous mode? And why?
- (10%) What is the output voltage V_o and the average input current I_{in} ?



5. (20%) Short Answer

- (7%) What are the differences between ZCS (zero current switching) and ZVS (zero voltage switching)?
- (7%) What are the advantages of the double-squirrel-cage rotors?
- (6%) How to obtain the reverse rotation of the single-phase induction motors?