

元智大學 九十七 學年度研究所 碩士班 招生試題卷

系(所)別：電機工程學系碩士班

組別：電腦通訊組

科目：電子學

用紙第 1 頁共 2 頁

●不可使用電子計算機


1. (10%) 解釋名詞：

channel length modulation effect, body effect (以 n-channel depletion-mode MOSFET 為例)


2. (20%) Consider the common-gate circuit in the following figure, $V_{TP} = -1V$, $K_p = 0.5 \text{ mA/V}^2$, $\lambda = 0$, $R_S = 3.71\text{k}\Omega$, $R_D = 1.62\text{k}\Omega$, $I_{DQ} = 0.75\text{mA}$, and $V_{SDQ} = 6\text{V}$.

(a) Draw the small-signal equivalent circuit and determine the input resistance R_i . (10%)

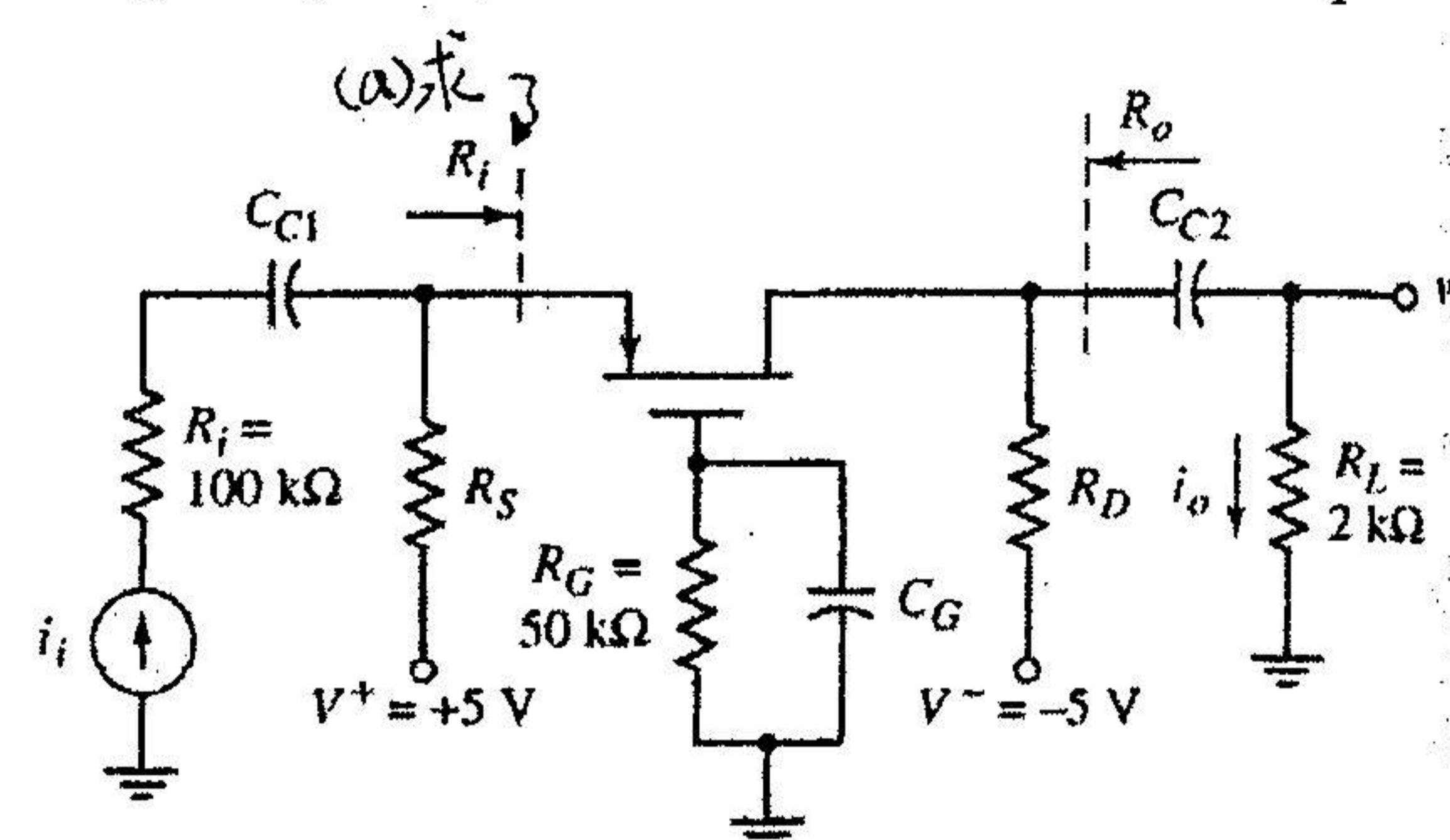(b) Draw the small-signal equivalent circuit and determine the output resistance R_o . (10%)



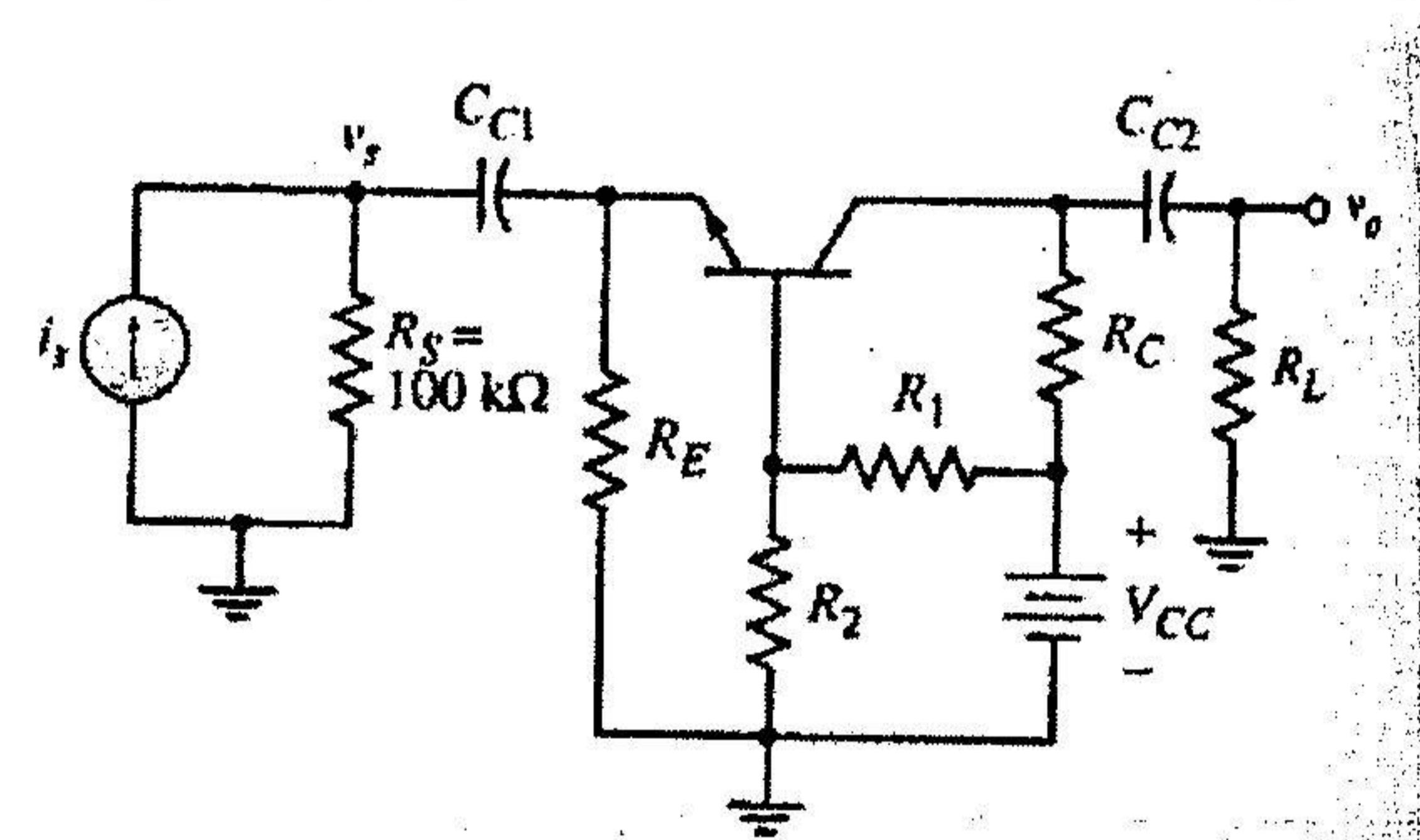3. (20%) For the circuit in the following figure, $\beta = 125$, $V_A = \infty$, $I_{CQ} = 1.46 \text{ mA}$, $R_L = 4\text{k}\Omega$, $R_E = 3\text{k}\Omega$, $R_C = 4\text{k}\Omega$, $R_1 = 25.6\text{k}\Omega$, and $R_2 = 10.4\text{k}\Omega$. (a) Determine g_m and r_π ; (4%) (b) draw the small-signal equivalent circuit; (4%) and (c) determine the trans-resistance $R_{in} = v_o/i_s$. (12%)



元智大學 九十七 學年度研究所 碩士班 招生試題卷

系(所)別：電機工程學系碩士班

組別：電腦通訊組

科目：電子學

用紙第 > 頁共 > 頁

●不可使用電子計算機

4. (10%) (a) Would you characterize the following circuit in Fig. P4(a) as being **inverting** or **noninverting**? Explain your answer. (5%) (b) Write an approximated equation describing the differential voltage gain (in terms of component values) for a differential pair circuit as shown in Fig. P4(b). (5%)

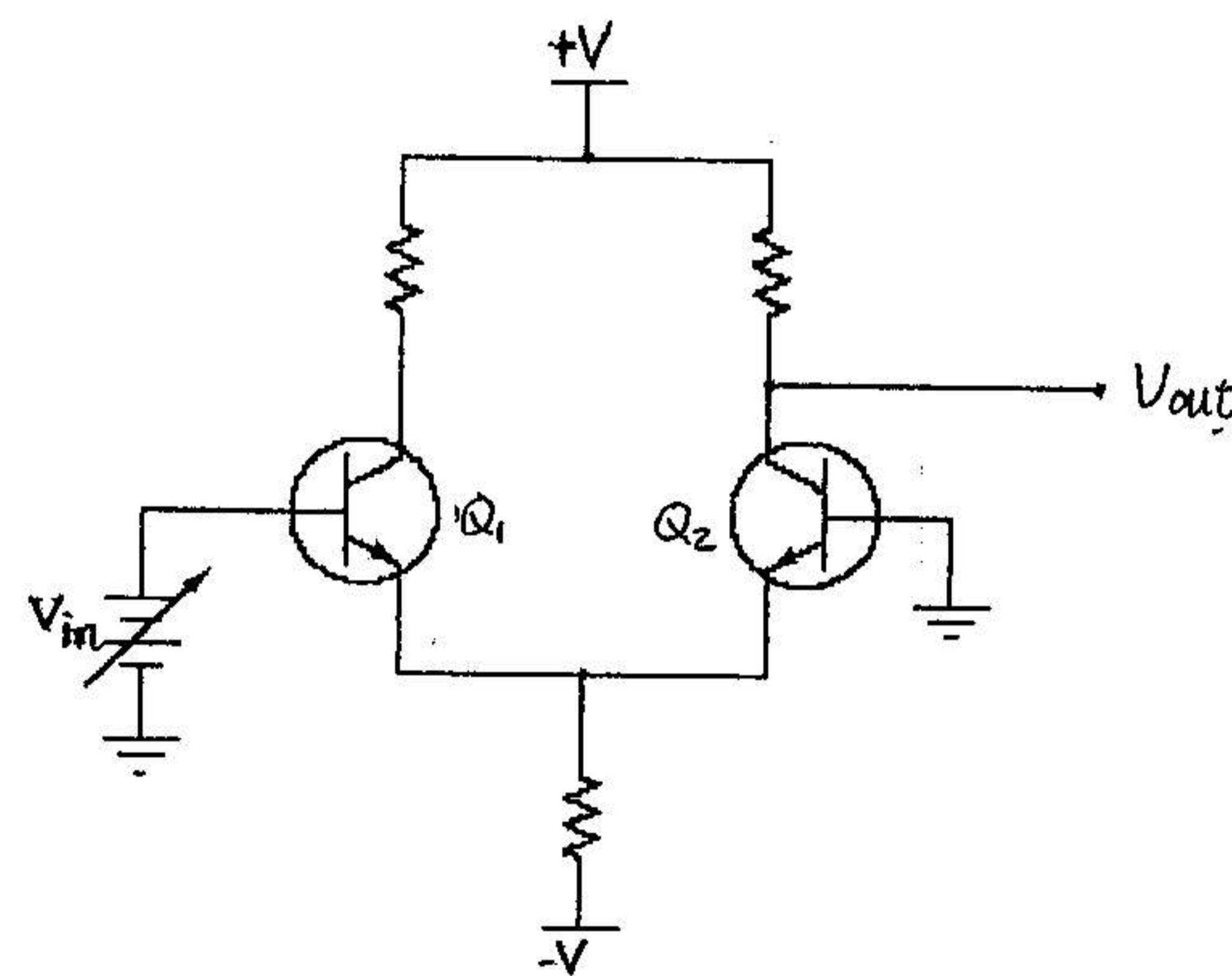


Figure P4(a)


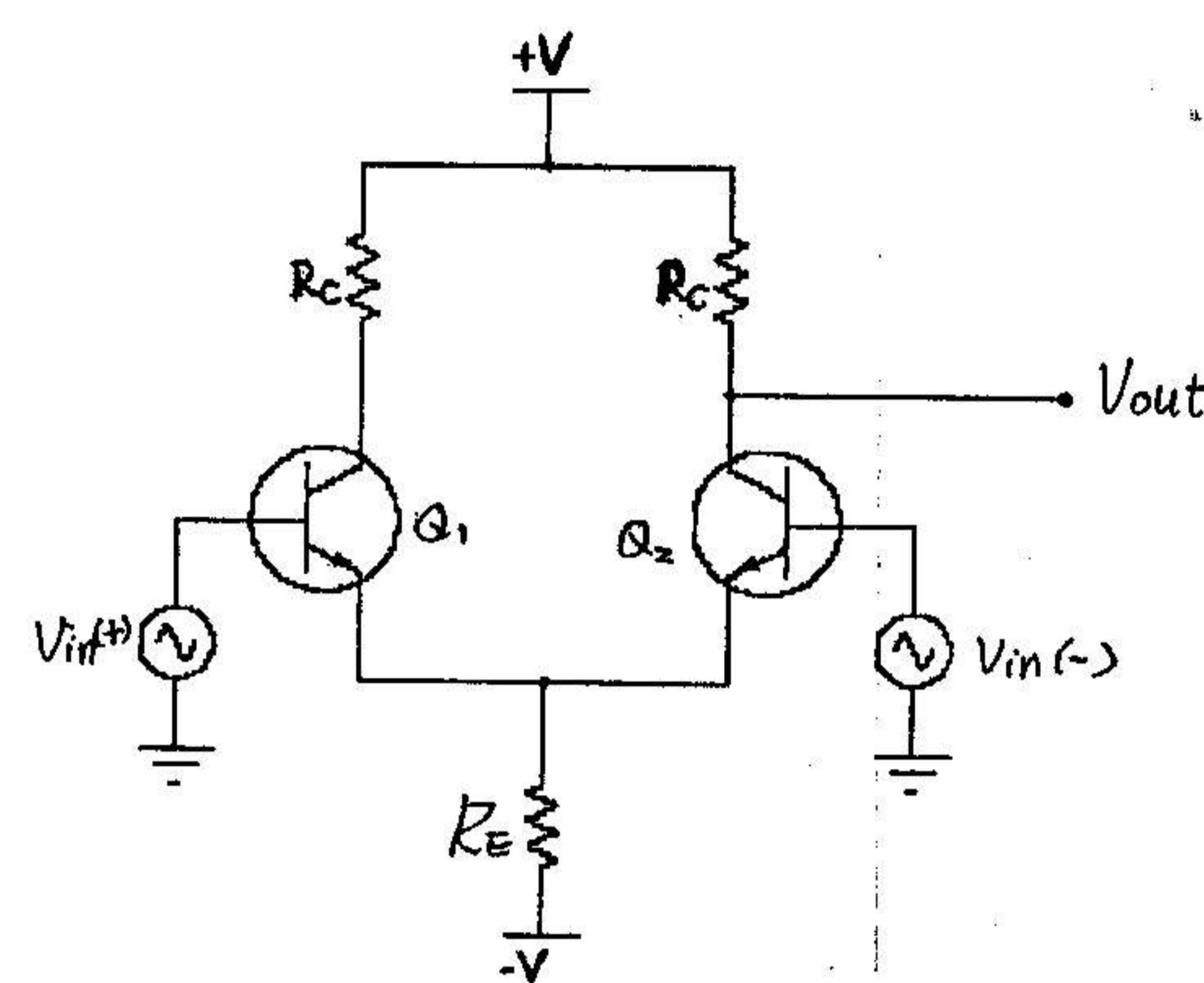


Figure P4(b)

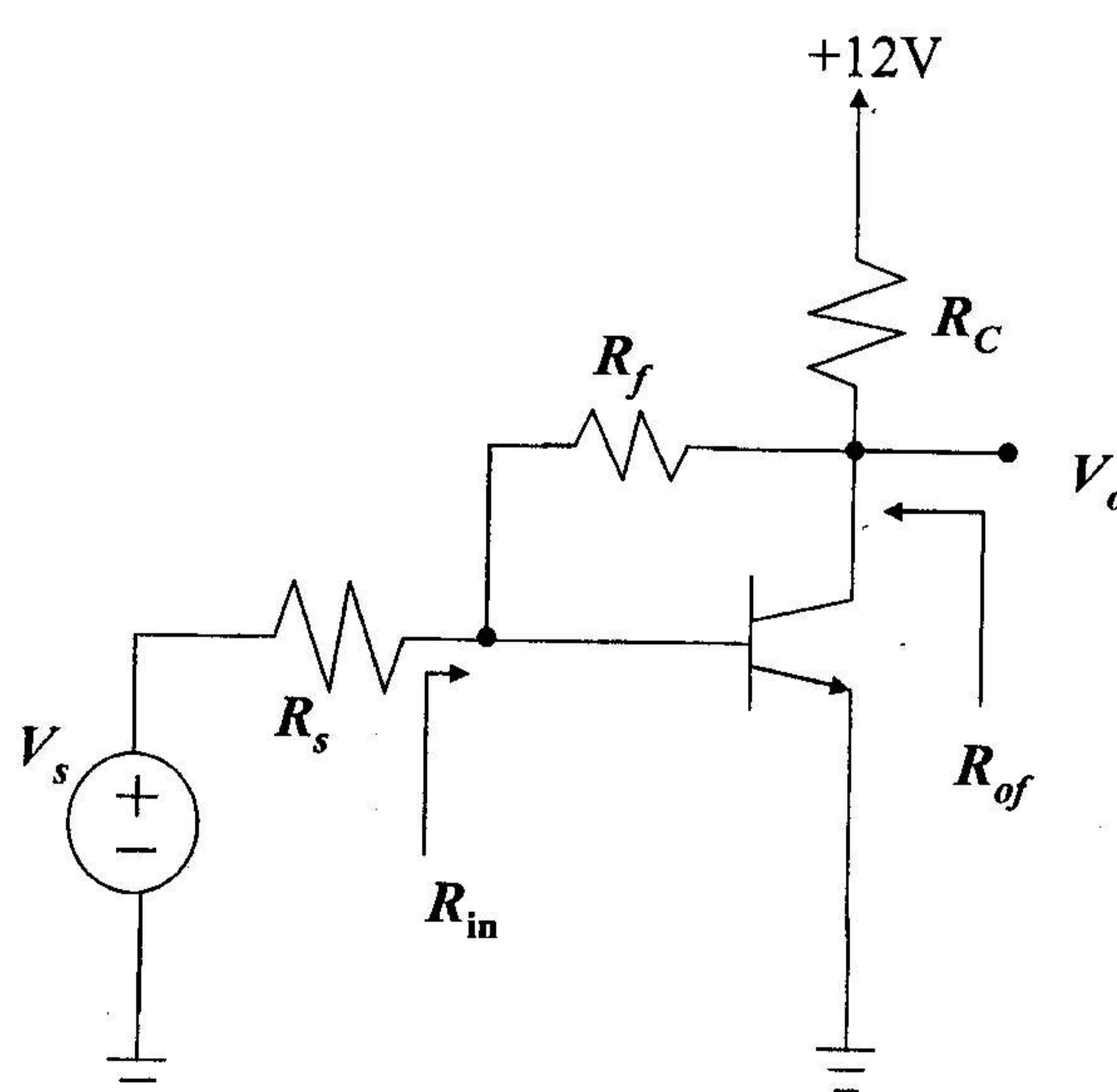5. (20%) (a) Using a common source amplifier circuit to explain the “Miller effect”. (10%) (b) Consider an ideal voltage amplifier with a gain of 0.95 V/V and a resistance $R=100k\Omega$ connected in the feedback path, that is, between the output and input terminals. Use Miller’s theorem to find the input resistance of this circuit. (10%)
6. (20%) Use the feedback theorem to analyze the following circuit with $R_C=4.7k\Omega$, $R_f=47k\Omega$, and $R_s=10k\Omega$. The feedback is provided by R_f . In addition, the transistor has $\beta=100$. (a) Determine the small signal voltage gain V_o/V_s . (10%) (b) Determine the input resistance R_{in} and output resistance R_{out} . (10%)



(命題請用黑色鋼筆、原子筆繪寫或電腦打字；試題字體務求清晰，並一律以正面單頁書寫，背面請勿書寫。)