

1. (15%) A Si $p-n$ junction diode with a cross-sectional area of $3 \times 10^{-4} \text{ cm}^2$. The parameters of the diode are: acceptor concentration $N_A = 6 \times 10^{16} \text{ cm}^{-3}$, donor concentration $N_D = 2 \times 10^{16} \text{ cm}^{-3}$, intrinsic carrier concentration $n_i = 9.65 \times 10^9 \text{ cm}^{-3}$, diffusion constant of electrons $D_n = 21 \text{ cm}^2/\text{s}$, diffusion constant of holes $D_p = 10 \text{ cm}^2/\text{s}$, carriers lifetime: $\tau_p = \tau_n = 5 \times 10^{-7} \text{ s}$. (i) Calculate the built-in voltage at 300 K. (5%) (ii) Calculate the ideal reverse saturation current. (10%)
2. (10%) Consider an n-channel enhancement-mode MOSFET with the following parameters: threshold voltage $V_{TN} = 0.75 \text{ V}$, channel width $W = 100 \text{ }\mu\text{m}$, channel length $L = 10 \text{ }\mu\text{m}$, electron mobility $\mu_n = 650 \text{ cm}^2/\text{V}\cdot\text{s}$, oxide thickness $t_{ox} = 500 \text{ \AA}$, and oxide permittivity $\epsilon_{ox} = (3.9)(8.85 \times 10^{-14}) \text{ F/cm}$. (i) Determine the drain current when $V_{GS} = V_{DS} = 2.5 \text{ V}$, for the transistor biased in the saturation region. (5%) (ii) Determine the drain current when $V_{GS} = 2.5 \text{ V}$ and $V_{DS} = 1 \text{ V}$, for the transistor biased in the triode (non-saturation) region. (5%)
3. (25%) In the circuit shown in Figure 1, the transistor has a β of 250. (i) What is the dc voltage at the collector? (5%) (ii) Find the input resistances R_{ib} and R_{in} and the overall voltage gain (v_o/v_{sig}). (15%) (iii) For an output signal of $\pm 0.5 \text{ V}$, what values of v_{sig} and v_b are required? (5%)
4. (18%) Analyze the circuit of Figure 2 to determine the small-signal voltage gain V_o/V_s , the input resistance R_{in} , and the output resistance $R_{out} = R_{of}$. The transistor has $\beta = 100$.
5. (18%) Find the voltage gain v_o/v_{id} for the difference amplifier of Figure 3 for the case $R_1 = R_3 = 10 \text{ k}\Omega$ and $R_2 = R_4 = 100 \text{ k}\Omega$. What is the differential input resistance R_{id} ? If the two key resistance ratios (R_2/R_1) and (R_4/R_3) are different from each other by 1%, what do you expect the common-mode gain A_{cm} to be? Also, find the CMRR in this case.
6. (14%) A BJT is specified to have a maximum power dissipation P_{D0} of 2 W at an ambient temperature T_{A0} of 25°C , and a maximum junction temperature T_{Jmax} of 150°C . Find the following: (a) The thermal resistance θ_{JA} . (5%) (b) The maximum power that can be safely dissipated at an ambient temperature of 50°C . (5%) (c) The junction temperature if the device is operating at $T_A = 25^\circ\text{C}$ and is dissipating 1 W. (4%)

國立中山大學 101 學年度碩士暨碩士專班招生考試試題

科目：電子學【電機系碩士班甲組、乙組、戊組、電波領域聯合】

題號：4063
共 2 頁 第 2 頁

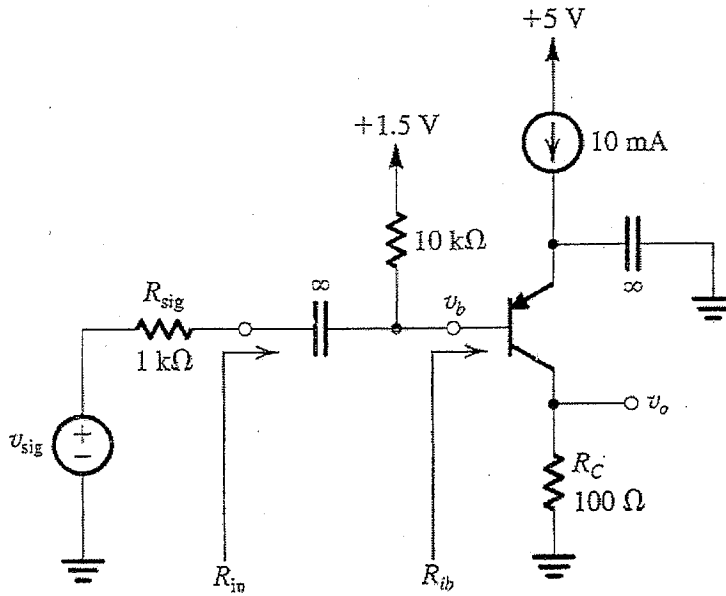


Figure 1

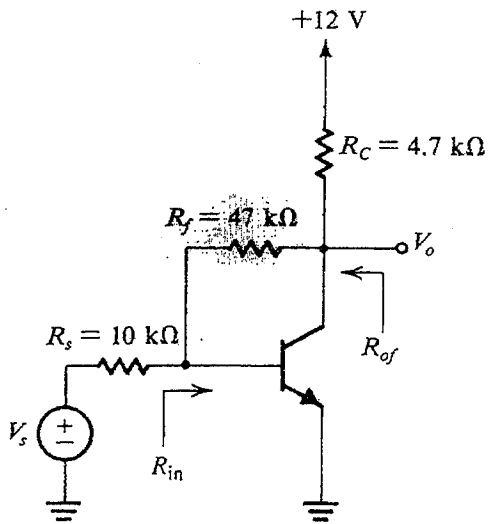


Figure 2

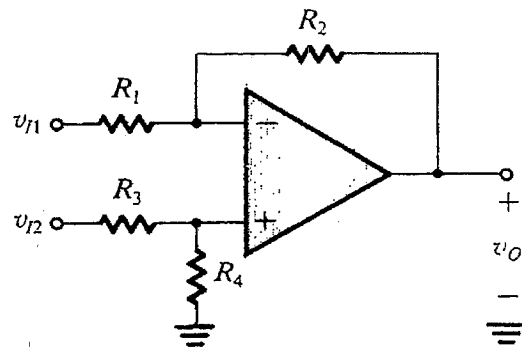


Figure 3