

- Discuss four basic losses such as core loss that occur in AC machine and draw the power flow diagrams from  $P_{in}$  to  $P_{out}$  for a three-phase AC generator and a three-phase AC motor, respectively. (20%)
- Describe the solution procedure of a power flow problem solved by a Gauss-Seidel technique. (including the procedure for swing bus, PV bus and PQ bus) (15%)
- A 200 hp, 440 V, 0.8-PF-leading,  $\Delta$ -connected synchronous motor has an armature resistance of  $0.22\Omega$  and a synchronous reactance of  $3.0\Omega$ . Its efficiency at full load is 89%.
  - What is the input power, line current and phase current to the motor at rated conditions? (10%)
  - What is the internal generated voltage of the motor at rated conditions? (10%)
- The fuel cost function in \$/h for three thermal plants are given by
 
$$C_1(P_1) = 625 + 7.3P_1 + 0.0025P_1^2$$

$$C_2(P_2) = 345 + 7.2P_2 + 0.004P_2^2$$

$$C_3(P_3) = 527 + 6.74P_3 + 0.003P_3^2$$
 where  $P_1$ ,  $P_2$  and  $P_3$  are in MW. Assume that all three units operate economically to meet the total plant load of 450MW, find the incremental cost and the required output of each plant. (20%)
- Fig. 1 shows a three-bus power system, calculate
  - Admittance matrix ( $Y_{bus}$ ). (10%)
  - Impedance matrix ( $Z_{bus}$ ). (10%)
  - If a balanced short-circuit fault occurred on bus 2, find the short-circuit current (The voltage at bus 2 is 1.0 p.u.). (5%)

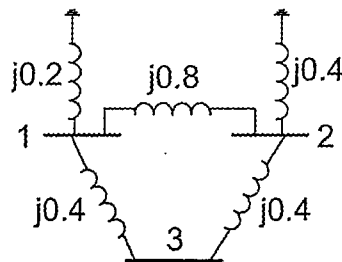


Fig. 1: Three-Bus Power System