

國立交通大學 97 學年度碩士班考試入學試題

科目：電子學(1801)電機車控制工程字，乙組、丙組、

考試日期：97 年 3 月 8 日 第 2 節

系所班別：電控系跨組聯招

組別：電控聯招

第 1 頁，共 4 頁

【可使用計算機】*作答前請先核對試題、答案卷(試卷)與准考證之所組別與考科是否相符！！

1. (20% in total) Consider the MOSFET class-AB output stage shown in Fig.1. The parameters are $V_{BB}=3\text{ V}$, $V_{DD}=10\text{ V}$ and $R_L=20\Omega$. The transistors are matched, and the parameters are $k'_n(W/L)_n=k'_p(W/L)_p=0.4\text{ A/V}^2$ and $|V_t|=1\text{ V}$.

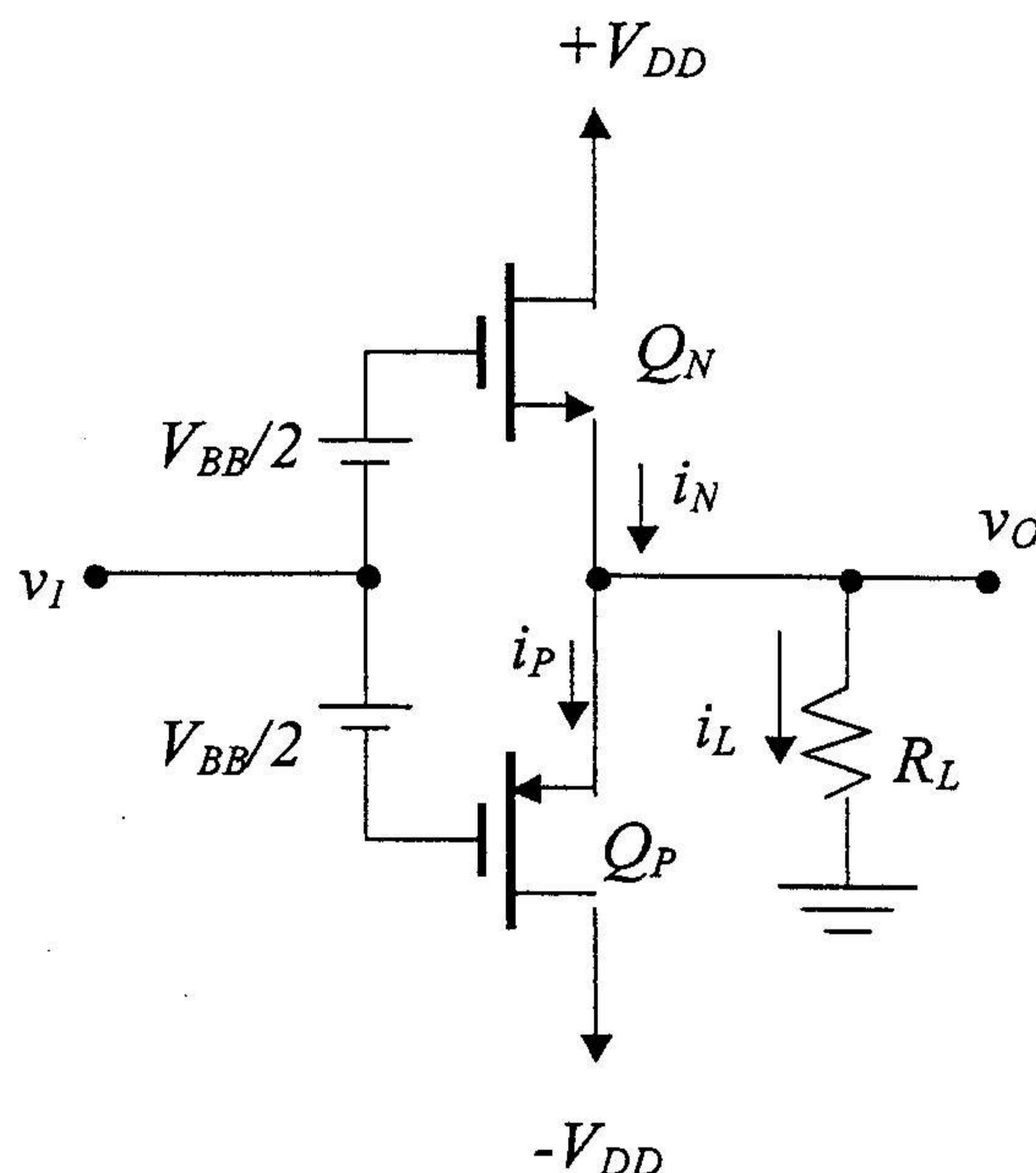


Fig.1

Let $V_{BB}=3\text{ V}$.

- (a) (4%) Determine the quiescent drain current (when $v_O=0$).
- (b) (8%) Determine the small-signal voltage gain A_v , evaluated at $v_O=0$.
- (c) (8%) Determine the small-signal voltage gain A_v , evaluated at $v_O=5\text{ V}$.

2. (15% in total) Consider the following circuits shown in Fig. 2.

- (a) (6%) The circuit A is a HPN filter. Please determine the notch frequency ω_n and the pole frequency ω_0 in terms of L_1 , L_2 , C , or R .
- (b) (3%) What is the filter type of the circuit B?
- (c) (6%) Let ϕ_1 and ϕ_2 be two non-overlapped clock signals. What is the filter type of the circuit C? Given the equivalent resistance R_{eq} of a switched-capacitor circuit is equal to T_c/C_{sw} where T_c is the clock period and C_{sw} is the switched-capacitor, please determine ω_0 in terms of C , C_1 , and T_c .

國立交通大學 97 學年度碩士班考試入學試題

科目：電子學(1801)


考試日期：97 年 3 月 8 日 第 2 節

系所班別：電控系跨組聯招


組別：電控聯招

第 2 頁，共 4 頁

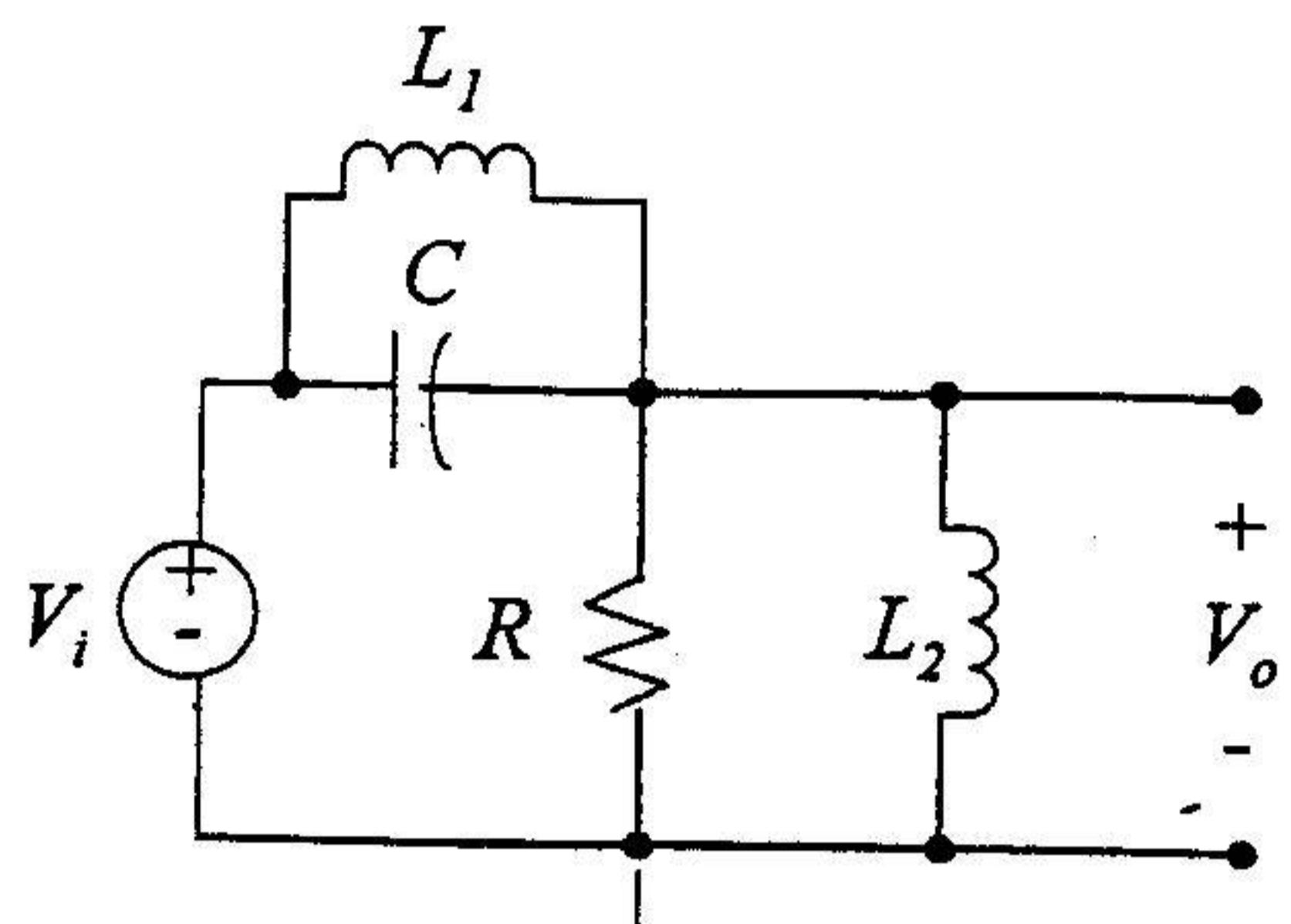
【可使用計算機】*作答前請先核對試題、答案卷(試卷)與准考證之所組別與考科是否相符！！



Circuit A

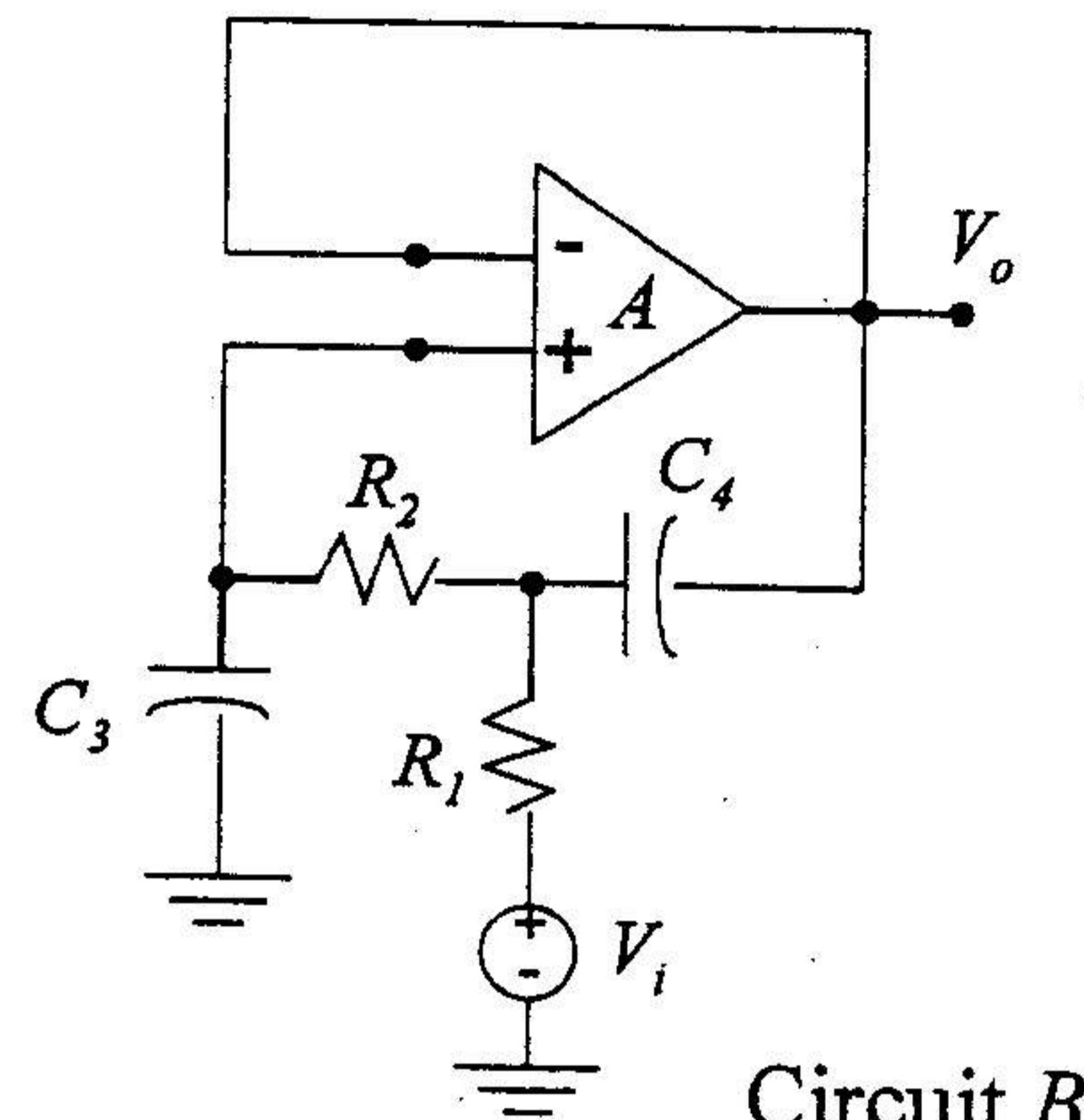

Circuit B

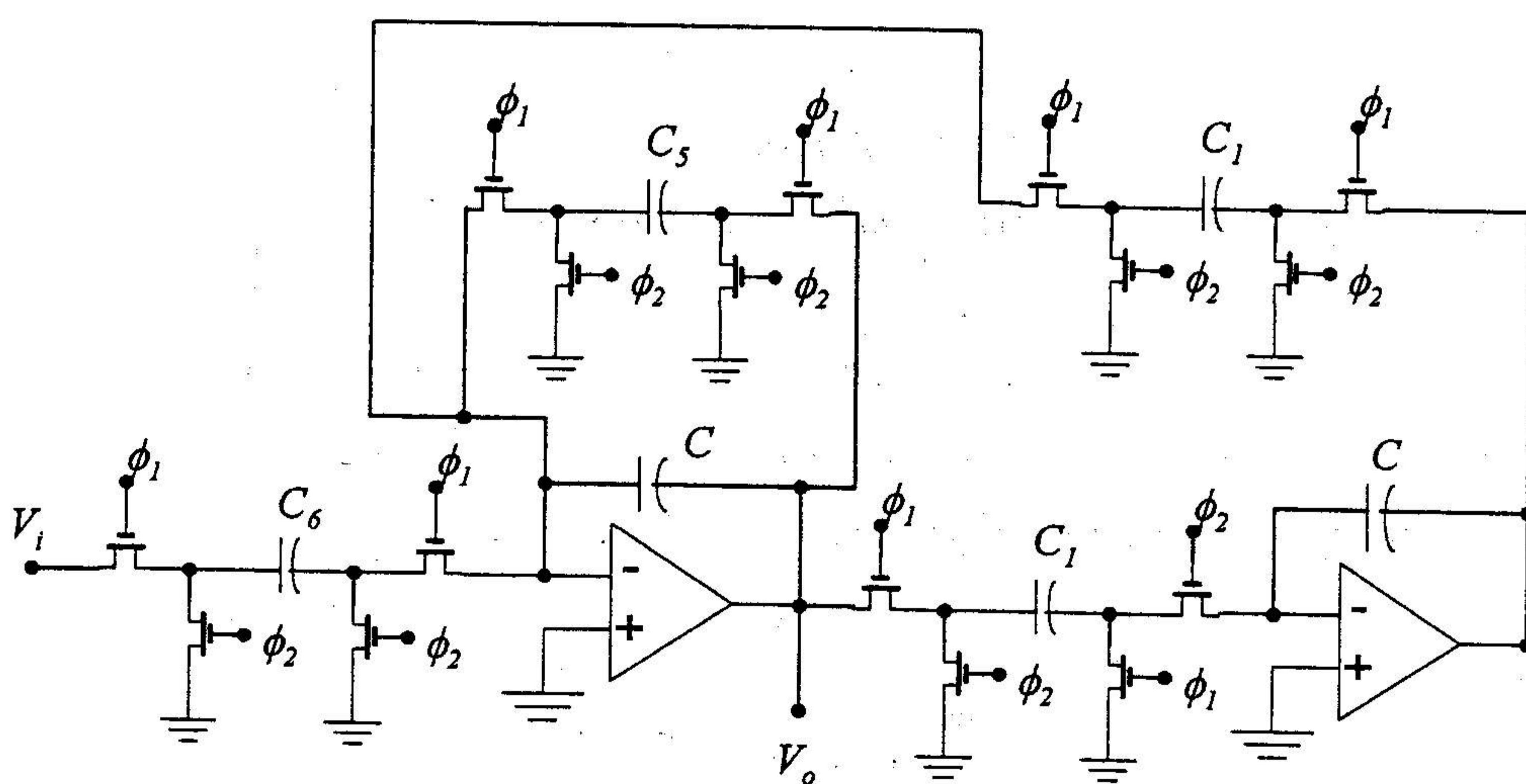

Circuit C

Fig. 2

3. (17% in total)

(a) Design an op-amp with feedback network in Fig. 3 (a).

- If the open-loop gain (A) is equal to 10^4 and the close-loop gain (A_f) is equal to 10, find the value of R_2/R_1 . (2%)
- If $V_S=1V$, find $V_o=?$ $V_f=?$ and $V_i=?$ (6%)
- How large is the value of $\Delta A_f/A_f$ when the value of A is decreased 20%? (2%)

(b) Find the equivalent output resistance in Fig. 3(b). V_{in} is the input signal and V_o is

國立交通大學 97 學年度碩士班考試入學試題

科目：電子學(1801)


考試日期：97 年 3 月 8 日 第 2 節

系所班別：電控系跨組聯招 組別：電控聯招


第 3 頁，共 4 頁

【可使用計算機】*作答前請先核對試題、答案卷(試卷)與准考證之所組別與考科是否相符！！

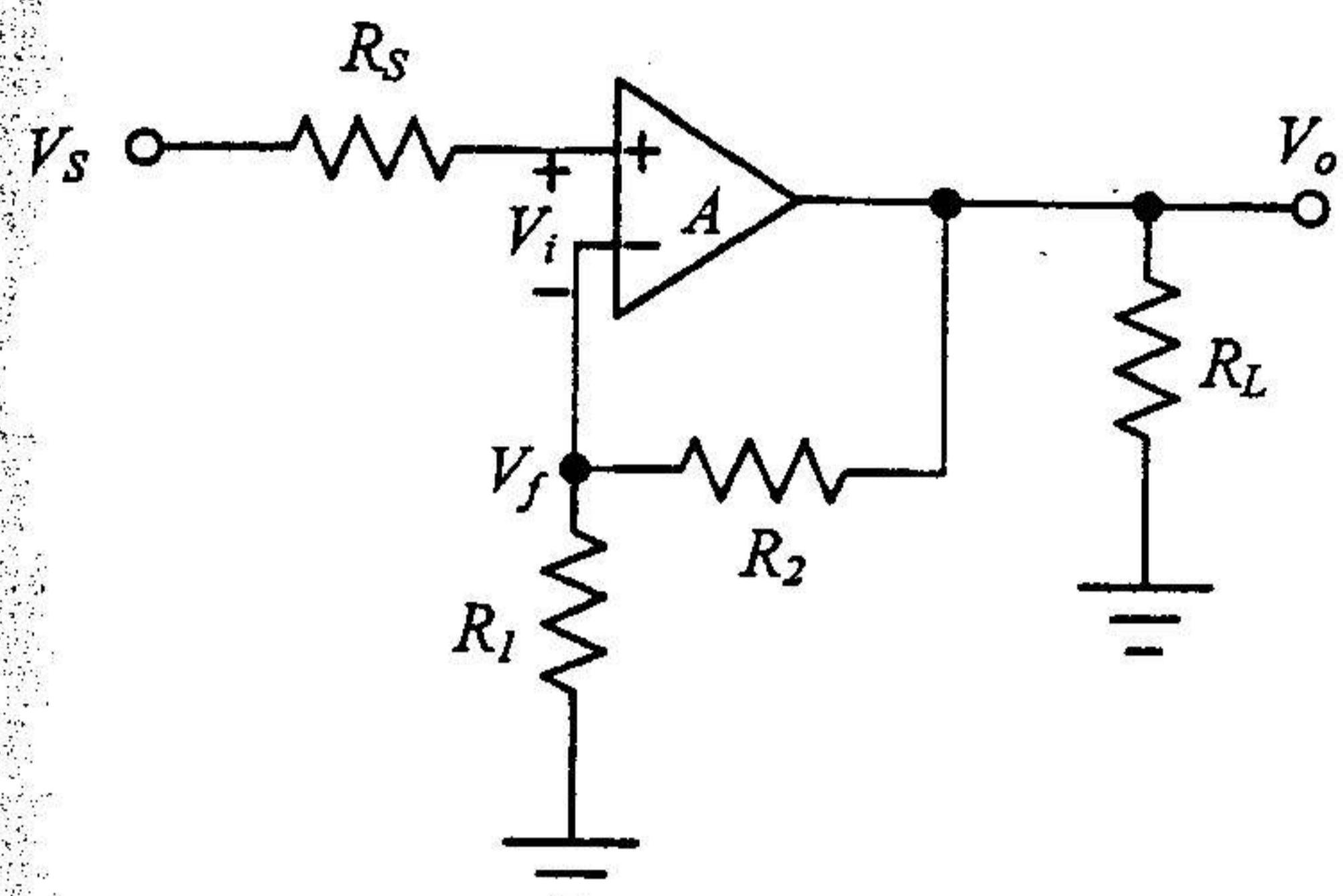the output signal. (7%) (Hint: Express it by g_{m1} , g_{m2} , r_{o1} , and r_{o2})



(a)

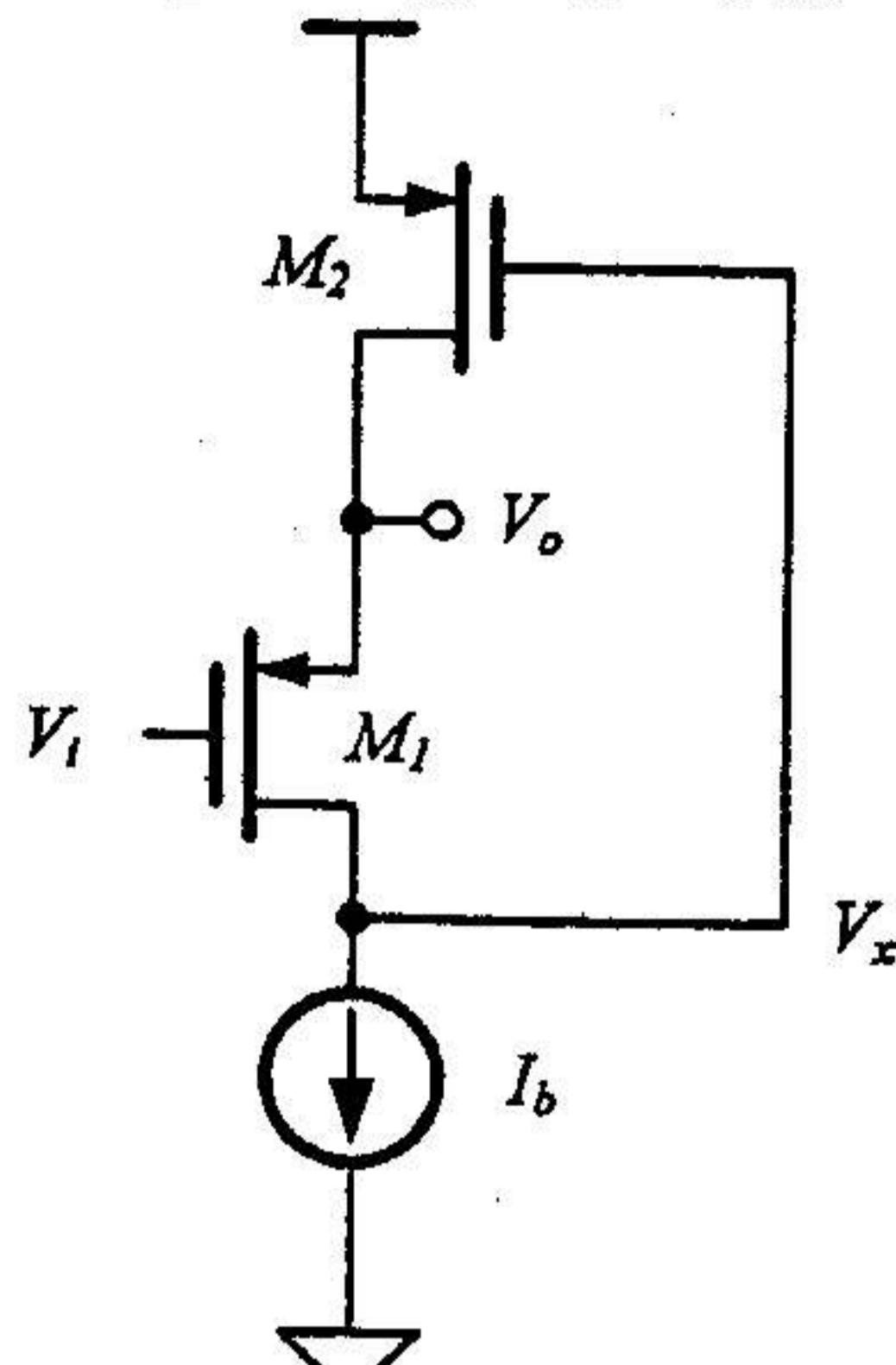

(b)

Fig. 3.

4. (16% in total) The threshold voltages of transistors $M_1 \sim M_8$ are $V_{TH1} \sim V_{TH8}$ in Fig. 4. V_{in} is the input signal and V_b is a biasing voltage for biasing the gates of transistors M_3 and M_4 .

- Describe the function of the circuit in Fig. 4. (4%)
- Find out the V_{out} range that the circuit can correctly operate when V_{in} is increased from 0V to V_{DD} . (12%) (Hint: V_{DD} is high enough to provide suitable voltage headroom. Express the range by V_{GS} , V_{TH})

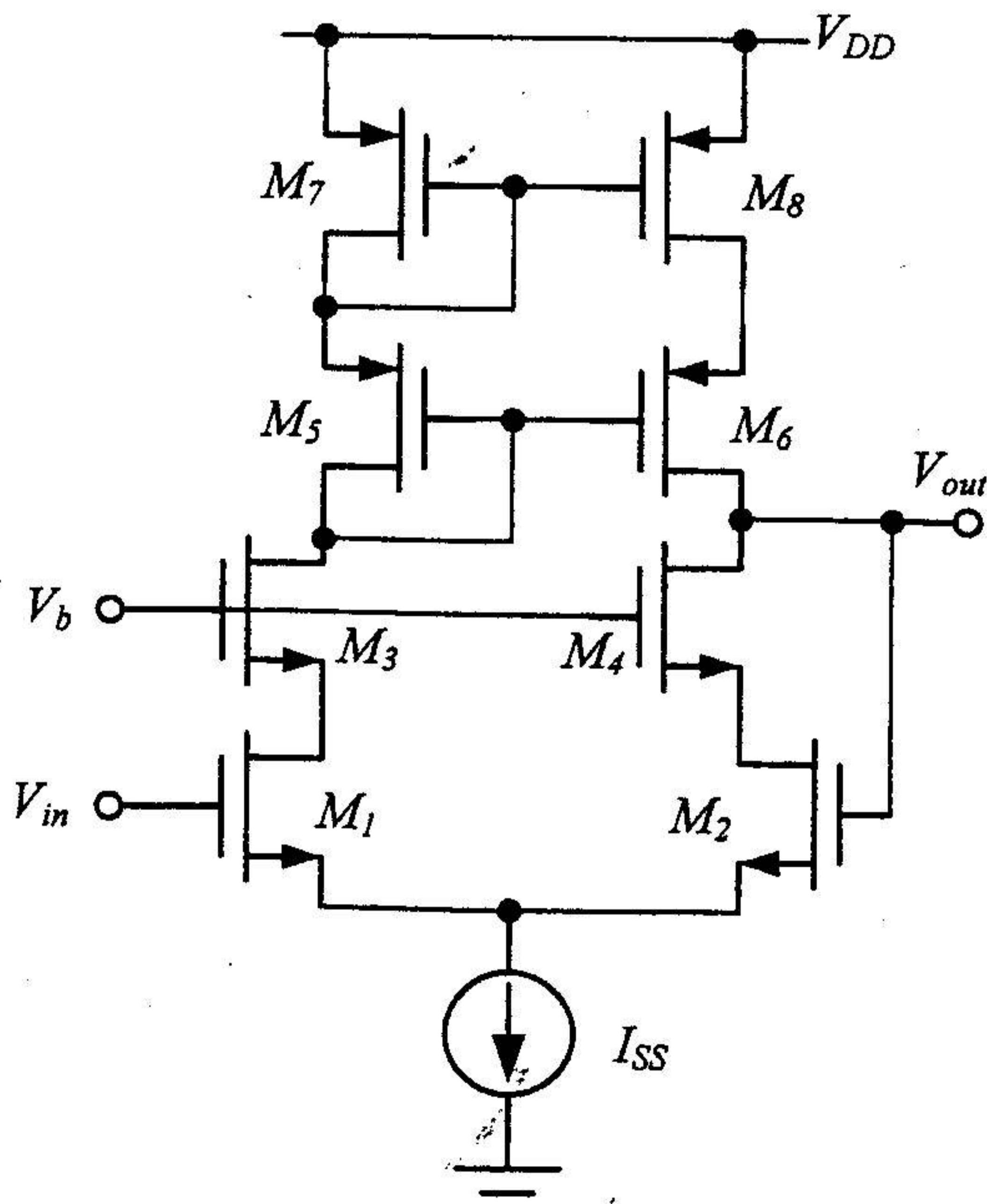


Fig. 4.

國立交通大學 97 學年度碩士班考試入學試題

科目：電子學(1801)

考試日期：97 年 3 月 8 日 第 2 節

系所班別：電控系跨組聯招

組別：電控聯招

第 4 頁，共 4 頁

【可使用計算機】*作答前請先核對試題、答案卷(試卷)與准考證之所組別與考科是否相符！！

5. (18% in total) **D1** and **D2** shown in Fig. 5 are identical. They have zero on-resistances and a constant voltage drop of 0.7V when being forward biased. Ignore their reverse biased currents. The threshold voltages of **M1** and **M2** are $V_{th1} = -0.6V$ and $V_{th2} = 0.6V$, respectively, and $\mu_p C_{ox}(W/L)_{M1} = \mu_n C_{ox}(W/L)_{M2} = 1mA/V^2$.

Let $V_1(t=0)$ and $V_o(t=0)$ be 0V, $C_1 = C_2 = 1\mu F$, $V_{DC} = 1.2V$, and ϕ be the waveform shown in Fig. 5.

- (a) Find V_1 at $t=0.99$ sec (4%)
- (b) Find V_o at $t=1.99$ sec (5%)
- (c) Find V_1 at $t=3.99$ sec (4%)
- (d) Find V_o at $t=3.99$ sec (5%)

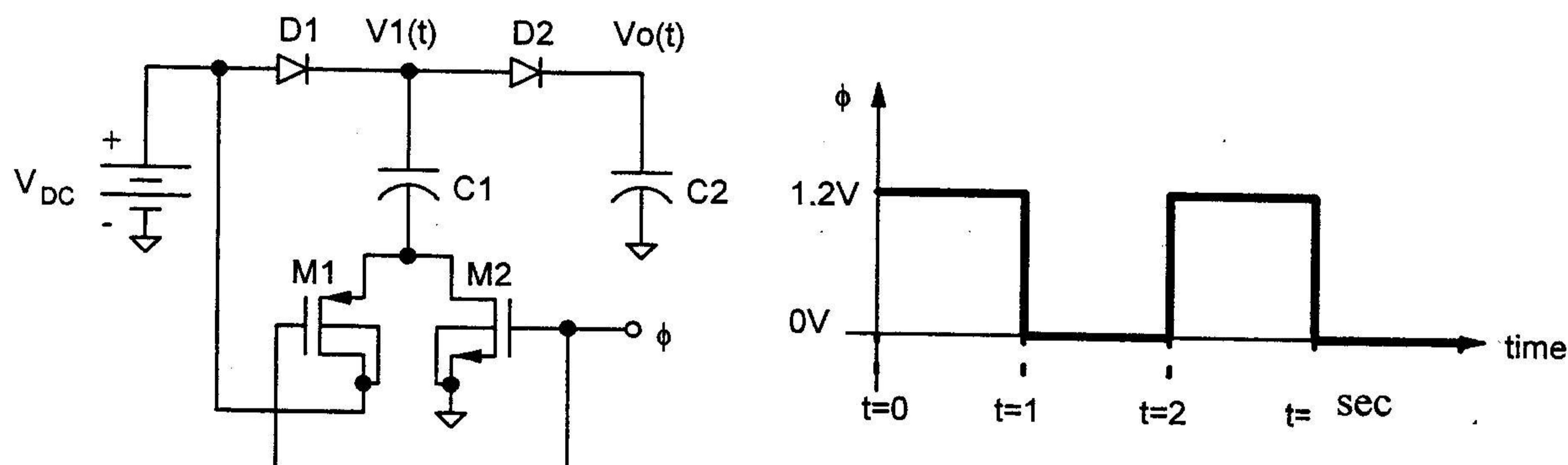


Fig.5

6. (14% in total) Refer to Fig.6, let **M1** and **M2** be identical whose threshold voltages are 0.5V and $\mu_n C_{ox}(W/L)_{M1} = \mu_n C_{ox}(W/L)_{M2} = 200 \mu A/V^2$. Meanwhile, **M3** and **M4** have the same threshold voltage of -0.5V and $\mu_p C_{ox}(W/L)_{M3} = 200 \mu A/V^2$, $\mu_p C_{ox}(W/L)_{M4} = 50 \mu A/V^2$. Given $R_S = 20K\Omega$ and $V_{DC} = 3.3V$. This circuit has two static states.

- (a) Find I_{DS1} in both static states. (7%)
- (b) Find V_{G3} and V_{G1} in both static states. (7%)

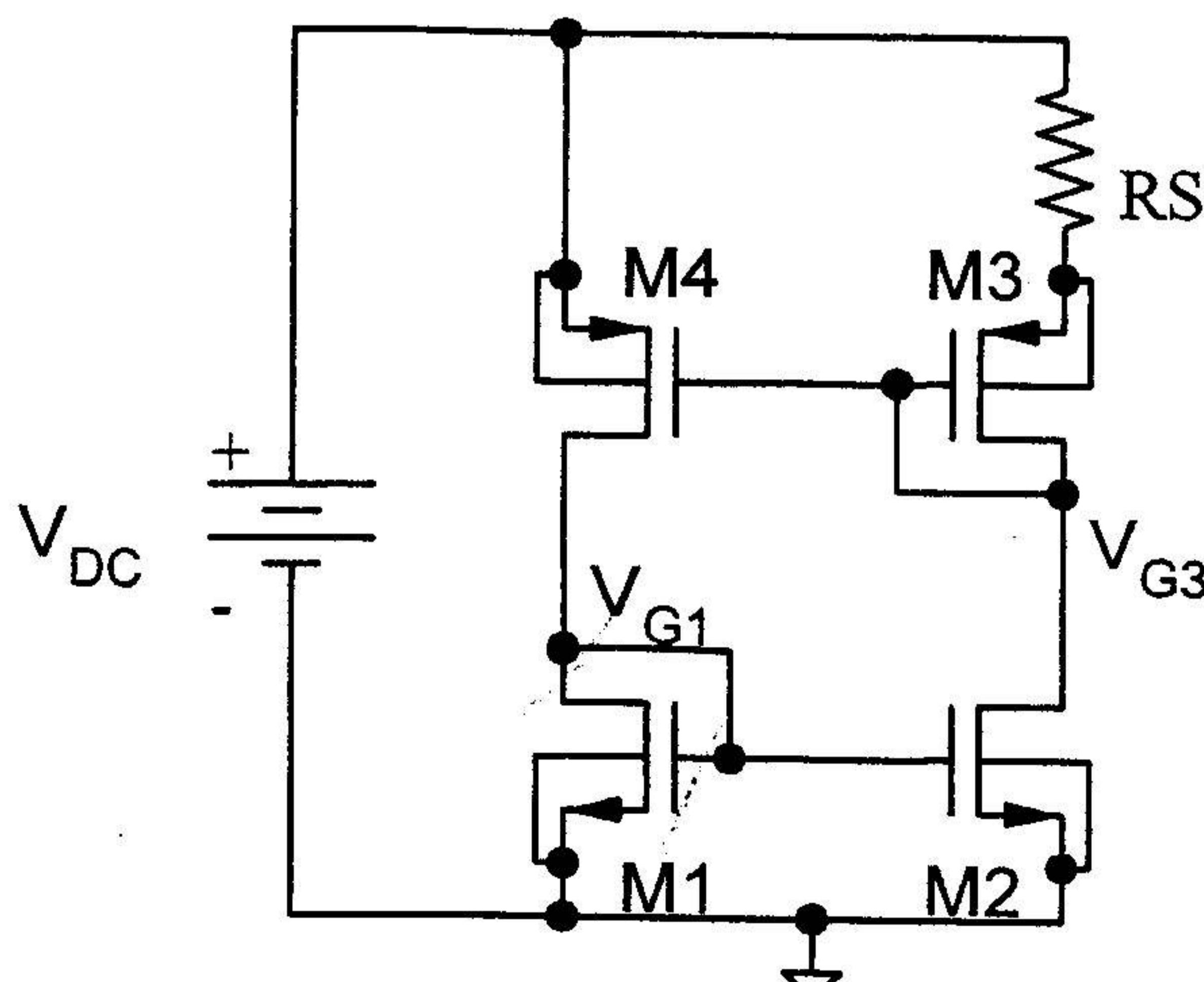


Fig. 6