

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (15%) Assume the operating cost function of the generating unit is $C_i = \alpha_i + \beta_i P_i + \gamma_i P_i^2$

For the control area contains n generators to provide total load demand P_T ,

I. specify the **objective function** of minimal operating cost C_i and its **constraint** without considering the loss.

II. Use the Lagrange method $L = C_i + \lambda \left(P_T - \sum_{i=1}^n P_i \right)$

Prove that the analytical solution for optimal λ is:

$$\lambda = \beta_i + 2\gamma_i P_i = \frac{P_T + \sum_{i=1}^n \frac{\beta_i}{2\gamma_i}}{\sum_{i=1}^n \frac{1}{2\gamma_i}}$$

2. (15%) Consider a system with the one-line diagram shown in the figure below, the per-unit ratings of the generator, transformers, transmission line, and motor are listed as follows:

Generator: 20MVA, 13.8kV, $X''_d=j0.1pu$, $X^2=j0.1pu$, $X^0=j0.05pu$


Transformer T_1 : 20MVA, 13.8kV-69kV, $X_l=j0.1pu$

Transformer T_2 : 20MVA, 69kV-13.8kV, $X_l=j0.1pu$

Transmission line : $X^1_{line} = X^2_{line}=j0.1pu$, $X^0_{line}=j0.3pu$ with 20MVA, 13.8kV base


Motor: 20MVA, 13.8kV, $X''=j0.2pu$, $X^2=j0.2pu$, $X^0=j0.1pu$

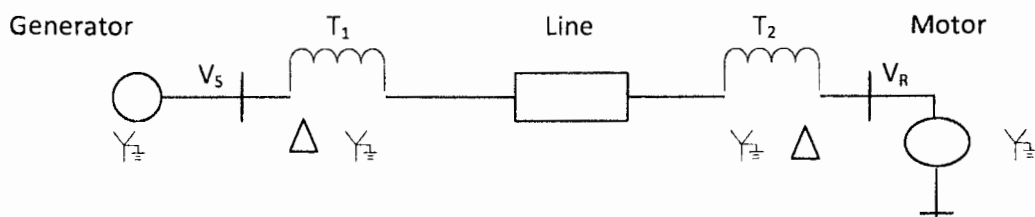The neutrals of the generator, motor, and Δ -Y transformers are solidly grounded.



Assume the pre-fault voltage is $1\angle 0^\circ pu$, please **derive the Thevenin equivalents** of the **zero-, positive-, and negative-** sequence networks in per-unit **as viewed from bus V_s** . Label all the per-unit voltages and impedances for the network diagram.

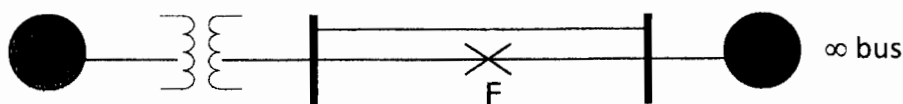3. (10%) A temporary three phase fault occurs away from sending end of bus as shown below:




Prove that the **critical clearing angle** δ_c has the following relationship with the variables shown in the figure below

$$\cos \delta_c = \frac{P_m (\delta_{max} - \delta_0) + P_{3max} \cos \delta_{max} - P_{2max} \cos \delta_0}{P_{3max} - P_{2max}}$$


, where P_{1max} , P_{2max} , P_{3max} are the peaks of the power curve,

(背面仍有題目,請繼續作答)

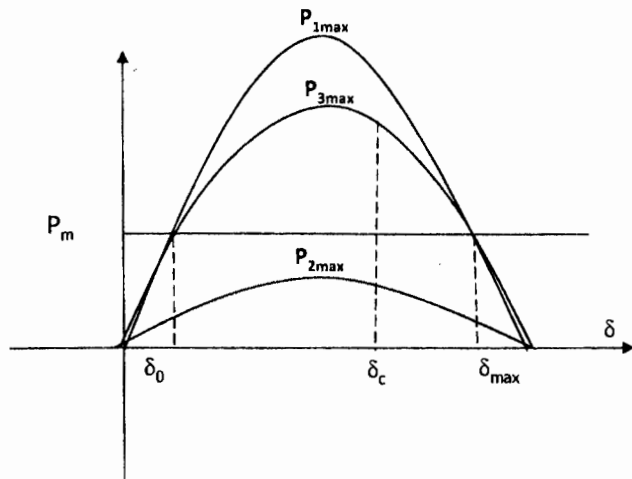
※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。
respectively.



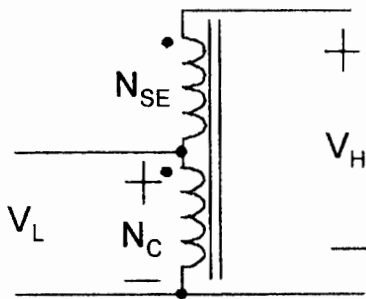4. (10%) Derive the voltage conversion ratio V_H/V_L for the step-up autotransformer, as shown below.



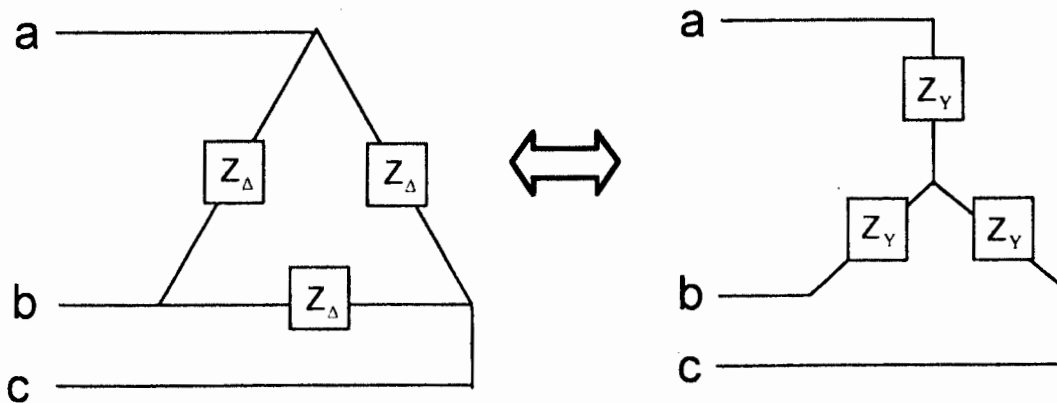5. (10%) Prove $Z_\Delta = 3Z_Y$ for the following two equivalent three-phase networks.



6. (10%) Draw the equivalent circuits of (1) long-shunt differentially compound DC generator, (2) long-shunt differentially compound DC motor.

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

7. (10%) Prove the output voltage ripple ratio $\frac{\Delta V_o}{V_o}$ of the following continuous-conduction mode (CCM)


buck converter equal to $\frac{\pi^2 \cdot (1-D)}{2} \cdot \frac{f_c^2}{f_s^2}$, where

D is the duty cycle of the main switch S ,

f_s is the switching frequency of the main switch S ,

f_c is equal to $\frac{1}{2\pi\sqrt{L \cdot C}}$.

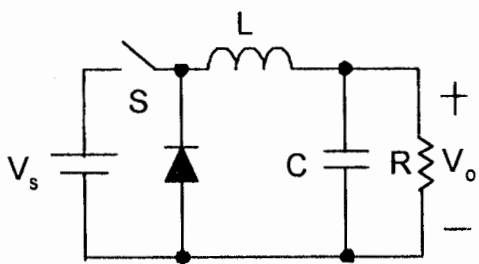Note: ALL components used in this circuit are ideal.



8. (10%) Derive the maximum current value of the inductor L in the above CCM buck converter.

9. (10%) Derive the minimum current value of the inductor L in the above CCM buck converter.