

國立臺北科技大學 103 學年度碩士班招生考試

系所組別：1523 自動化科技研究所乙組


第三節 電路學 試題（選考）

第一頁 共二頁


注意事項：

1. 本試題共七題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

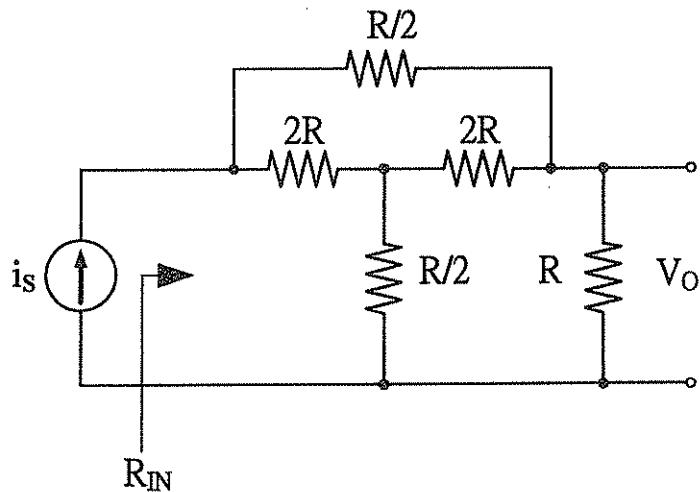
1. For the circuit shown below, find the output voltage V_o and the input resistance R_{in} seen by the current source in terms of R . (20%)



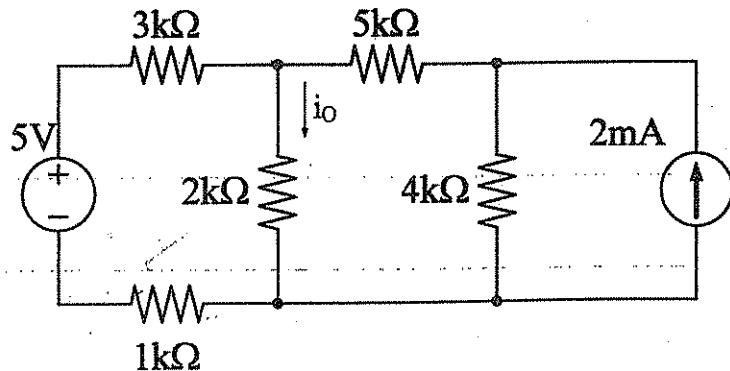
2. For the circuit shown below, find the value of i_o . (10%)



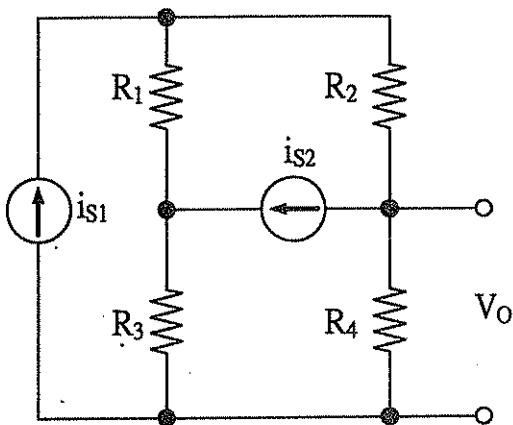
3. Find the value of V_o in terms of i_{S1} and i_{S2} for the circuit shown below where $R_1=1\Omega$, $R_2=4\Omega$, $R_3=4\Omega$ and $R_4=10\Omega$. (10%)



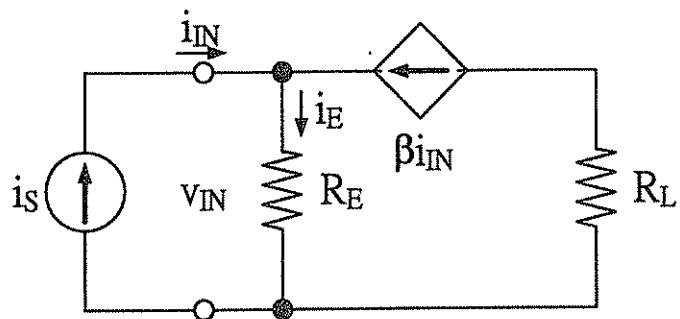4. Find the input resistance of the circuit shown below. (10%)



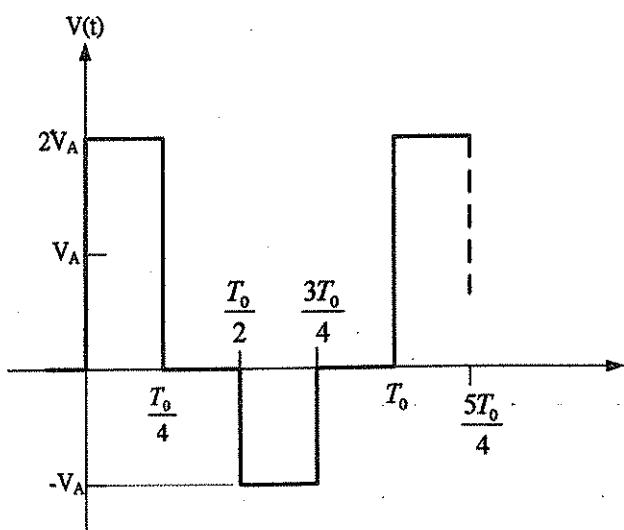
5. Find the average and RMS values of the periodic waveform shown below. (10%)



注意：背面尚有試題

6. The switch shown in the circuit below has been open for a long time and is closed at $t=0$.

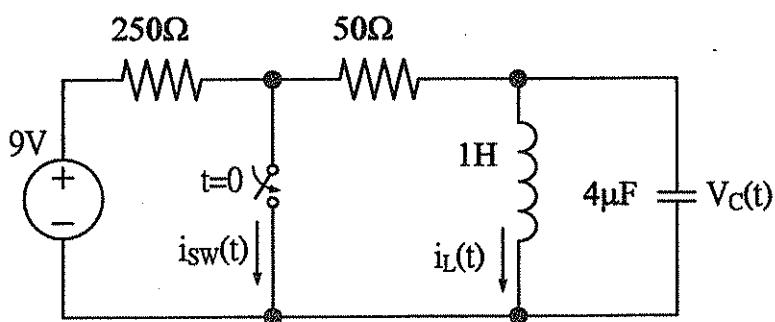- 1) Find the voltage across the capacitor and the current through the inductor just before $t=0$. (5%)
- 2) Find the inductor current i_L for $t \geq 0$. (5%)
- 3) Find the capacitor voltage V_C for $t \geq 0$. (5%)
- 4) Find the current through the switch for $t \geq 0$. (5%)



7. The input impedance and the voltage of the voltage source, V_s , in the circuit shown below are $Z_s=j20\Omega$ and $V_s=2500\angle0^\circ$ V at 377 rad/s respectively. The transformer has $L_1=2H$, $L_2=0.2H$, and $M=0.6H$. The load impedance is $Z_L=25+j15\Omega$. Find I_A , I_B , V_1 , V_2 and the average power delivered by the voltage source. (20%)

