

元智大學 103 學年度研究所 碩士班 招生試題卷

系(所)別：光電工程學系碩
士班

組別：不分組

科目：電子學

用紙第 / 頁共 2 頁

● 可使用現行『國家考試電子計算器規格標準』規定第二類之計算機

元智大學一百零三學年度 研究所考試 招生試題卷

系別：光電工程研究所 科目：電子學

Parameter: $V_t = 0.026 \text{ mV}$ ($T = 300 \text{ K}$), $\ln 10 = 2.3$, $e^{-1} = 0.37$, $e^{-3} = 0.05$

- (5%) What is the reasonable value for the intrinsic carrier concentration in silicon at $T = 300 \text{ K}$: (a) $1.5 \times 10^{10} \text{ cm}^{-3}$ (b) $1.5 \times 10^{18} \text{ cm}^{-3}$ (c) $1.5 \times 10^5 \text{ cm}^{-3}$ (d) $1.5 \times 10^{25} \text{ cm}^{-3}$
- (5%) What is the suitable doping species for the N-type Si: (a) N (b) Al (c) B (d) As
- (5%) What is the ideal gate current for the MOS field-effect transistor: (a) 0 A (b) 1 mA (c) 10 A (d) 1000 μA .
- The hole concentration in silicon is given by $p(x) = 10^4 + 10^{15} \exp(-x/L_p)$, $x > 0$. The value of L_p is $10 \mu\text{m}$. The hole diffusion coefficient is $D_p = 15 \text{ cm}^2/\text{s}$. Determine the hole diffusion current density at (a) $x = 0$, (3%) (b) $x = 10 \mu\text{m}$ (3%), and (c) $x = 30 \mu\text{m}$. (4%)
- (5%) (a) The applied electric field in p-type silicon is $E = 10 \text{ V/cm}$. The semiconductor conductivity is $\sigma = 1.5 \text{ (ohm-cm)}^{-1}$ and the cross-sectional area is $A = 10^{-5} \text{ cm}^2$. Determine the drift current. (5%) (b) The cross-sectional area of a semiconductor is $A = 1.2 \times 10^{-3} \text{ cm}^2$ and the resistivity is $\rho = 0.4 \text{ (ohm-cm)}$. If the drift current is $I = 1.2 \text{ mA}$, what applied electric field must be applied?
- Consider the rectifier circuits shown in Figure 1 and 2. Assume the input voltage is from a 110 V (rms) , 60 HZ ac source. The desired peak output voltage v_o is 9 V , and the diode turn on voltage is assumed to be $V_f = 0.7 \text{ V}$. Compare the characteristics of (a) and (b) in these two full-wave rectifier circuits:
(a) transformer turns ratio. (5%)
(b) peak inverse voltage. (5%)
(c) Which rectifier is better? (5%)
- Determine the current in each diode (I_{D1} , I_{D2} , and I_{D3}) and the voltages of V_A and V_B in the multidiode circuit shown in Figure 3. Let $V_f = 0.7 \text{ V}$ for each diode. (10%)
- (5%) (a) Please describe the "Body effect" in MOSFET.
(5%) (b) Please describe the "Early Voltage" in Bipolar Junction Transistor.
(5%) (c) For small signal consideration, an NMOS transistor biased in the saturation region, with a drain current of I_{DQ} , prove $g_m = 2(K_n I_{DQ})^{1/2}$ in MOSFET.
- For the circuit in Figure 4 let $\beta = 100$, $V_A = 200 \text{ V}$, $V_{CC} = 10 \text{ V}$, $V_{BE(\text{on})} = 0.7 \text{ V}$, $R_C = 15 \text{ k}\Omega$, $R_B = 100 \text{ k}\Omega$, and $V_{BB} = 0.96 \text{ V}$. (a) Determine the small-signal hybrid- π parameters r_x , g_m , and r_o . (10%) (b) Find the small-signal voltage gain $A_v = V_o/V_i$. (5%)
- Determine the small-signal voltage gain of a common-source circuit containing a source resistor. Consider the circuit in Figure 5 with parameters: $V_{TN} = 0.8 \text{ V}$, $K_n = 1 \text{ mA/V}^2$, and $\lambda = 0$. (Note: $V_{GSQ} = 1.5 \text{ V}$, $I_{DQ} = 0.5 \text{ mA}$, and $V_{DSQ} = 6.25 \text{ V}$) (10%)

元智大學 103 學年度研究所 碩士班 招生試題卷

系(所)別： 光電工程學系碩士班 組別： 不分組 科目： 電子學 用紙第 2 頁共 2 頁

● 可使用現行『國家考試電子計算器規格標準』規定第二類之計算機

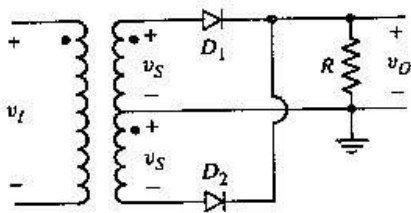


Figure 1

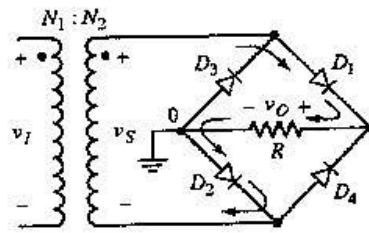


Figure 2

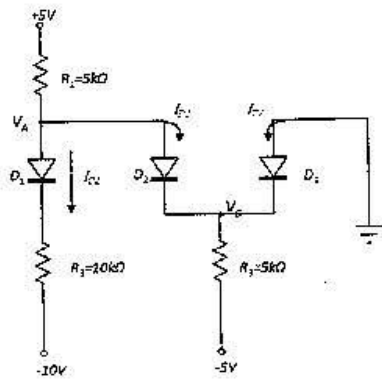


Figure 3

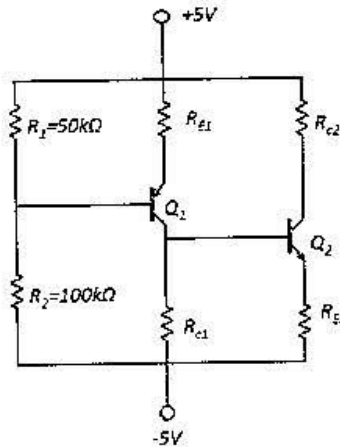


Figure 4

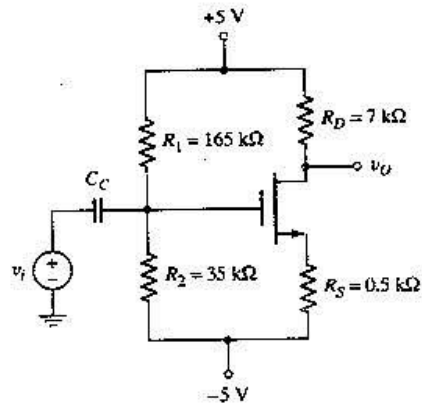


Figure 5