

中原大學99學年度碩士班入學考試

03/20 14:00~15:30 電機工程學系電子電路組

科目：電子學

(共 2 頁第 1 頁)

可使用計算機，惟僅限不具可程式及多重記憶者

- (1) Please derive the input resistance of the following OP amplifier, assuming the finite open-loop gain is **A**. (10%)

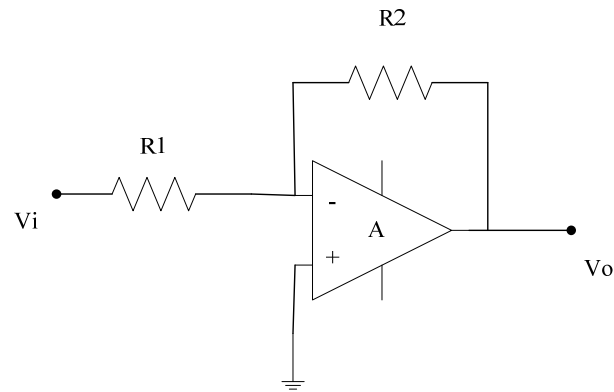


figure 1

- (2) What is the name of the following circuit, as shown figure 2? (5%)


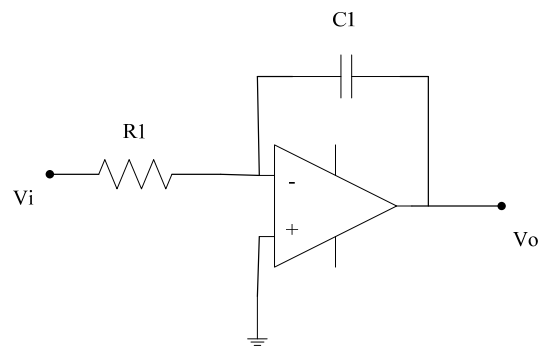


figure 2

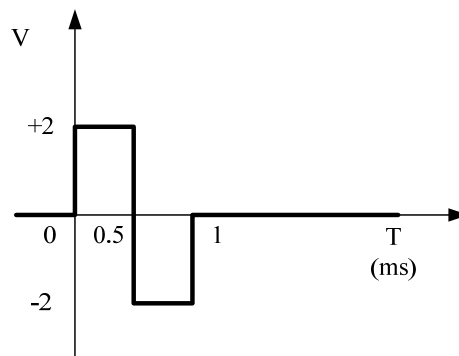- (3) Assuming the time constant is 1ms, Please derive all the necessary equations and draw the output waveform of the circuit in figure 2 based on the following input signal. (15%)



中原大學99學年度碩士班入學考試

03/20 14:00~15:30 電機工程學系電子電路組

科目：電子學

(共 2 頁第 2 頁)

可使用計算機，惟僅限不具可程式及多重記憶者

(4) The parameters of the transistor shown in figure 3 are:

$\beta = 100$, $V_A = 80v$. Assuming the values of all capacitors are infinite,

Please find:

- The dc voltage of collector, base and emitter. (15%)
- What is the g_m ? r_π ? (10%)
- Assuming A is connected to ground, B is attached to a load resistance of 10k ohm, and C is connected to a voltage source V_s with 200ohm source resistance. What is the voltage gain of

$$\frac{v_B}{v_s} ? (20\%)$$

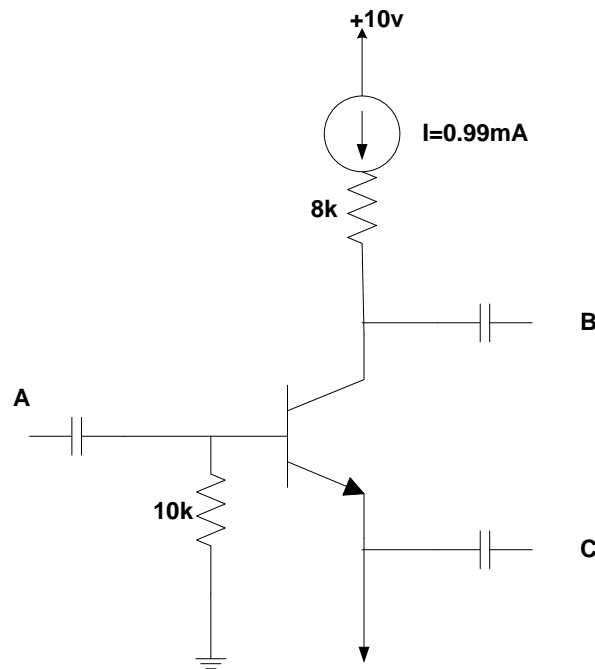


figure 3

(5) Please draw a typical CMOS inverter using n and p channel devices (2.5%), Please explain noise margin (2.5%).

(6) Based on the above question, assuming the sizes of both n and p channel MOS are identical, and $\mu_n = 2\mu_p$, $|V_t| = 1v$, $V_{DD} = 5v$, what are the values of V_{IH}, V_{IL} ? And noise margin? (20%)