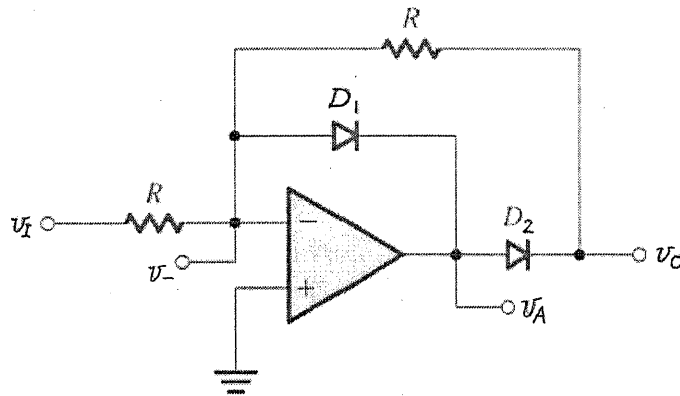



科目	電子學	適用系所	電子工程學系固態電子組、電路與系統組	時間	100 分鐘
----	-----	------	--------------------	----	--------

※請務必在答案卷作答區內作答。 共 3 頁第 1 頁

- A $p-n$ silicon step junction diode has $N_A = 10^{17} \text{ cm}^{-3}$, $N_D = 10^{16} \text{ cm}^{-3}$, $D_n = 30 \text{ cm}^2/\text{s}$, $D_p = 10 \text{ cm}^2/\text{s}$, $\tau_n = \tau_p = 0.1 \mu\text{s}$, $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, $A = 5 \times 10^4 \mu\text{m}^2$, and $\epsilon_s = 11.7\epsilon_0$. Assume that the forward current is $I = 0.5 \text{ mA}$. (a) Find the built-in potential voltage V_0 . (5%) (b) Find the forward voltage V . (5%) (c) Find the diffusion capacitance C_D . (5%) (d) Find the junction capacitance C_J (Assume that $C_J \approx 2C_{J0}$ where C_{J0} is the junction capacitance with no bias). (5%)
- The opamp in the following figure is ideal with output saturation levels of $\pm 10 \text{ V}$. The diodes have a constant 0.7 V drop when conducting. Find v_- , v_A , and v_O for (a) $v_I = 2 \text{ V}$. (7%) (b) $v_I = -2 \text{ V}$. (7%)




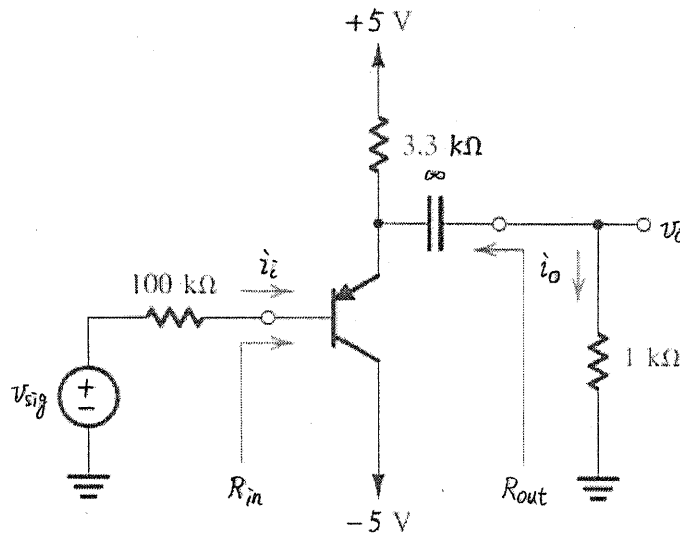- Consider the emitter follower shown below. The BJT has $\beta = 100$ and $r_o = \infty$. (a) Find the dc emitter current I_E . (4%) (b) Find R_{in} , R_{out} , i_o/i_i , and v_o/v_{sig} . (12%)



4. Consider the circuit shown below with the following cases: $V_{CC}=V_{EE}=10V, I=1mA$
 $R_B=100K\Omega, R_C=8K\Omega, R_{sig}=R_L=5K\Omega, \beta=100, V_A=100V, C_u=1pF, f_T=800MHz$,
 Please calculate

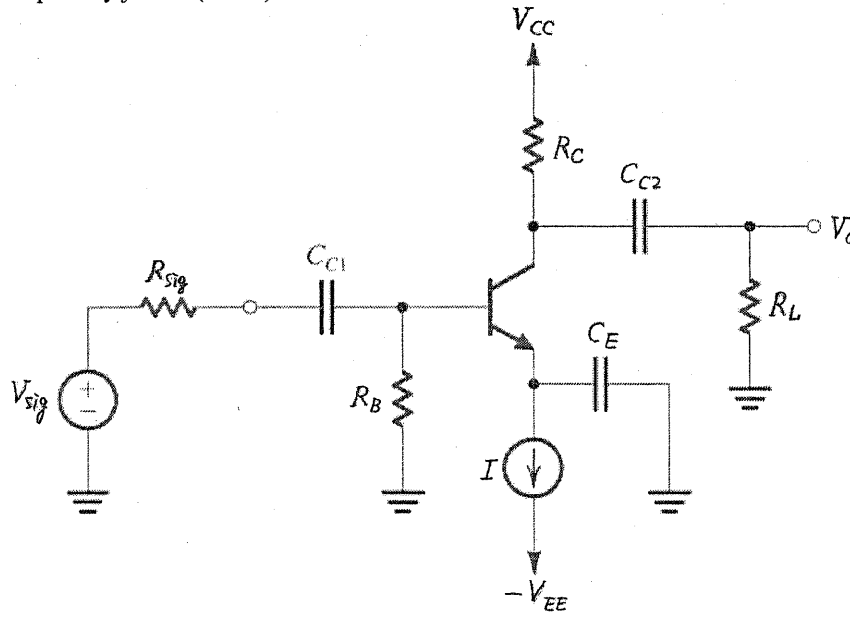
- (a) Midband voltage gain $A_M=? (V_o/V_{sig})$ (10%)
- (b) Upper -3dB frequency $f_H=?$ (10%)



(a)

5. Analyze the circuit shown below to answer the following questions

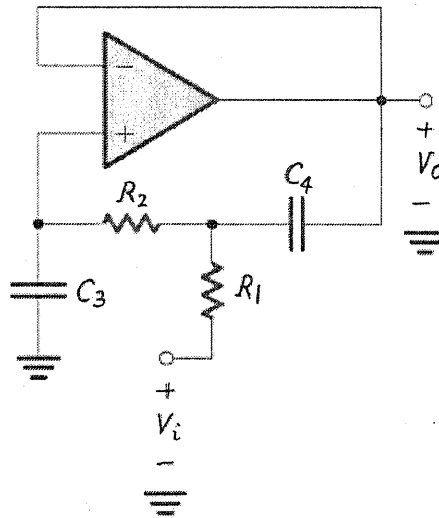- (1) The transfer function $V_o(s)/V_i(s)$ (5%)
- (2) The pole quality factor Q (5%)
- (3) The pole frequency ω_o (5%)
- (4) The DC gain=? (5%)



(c)

6. Consider the bias circuit shown below with the geometric ratio $(W/L)_8=(W/L)_9=(W/L)_{10}=(W/L)_{11}=(W/L)_{13}=20$, and $(W/L)_{12}=80$. Also, we have $\mu_n C_{ox} = 90 \mu A / v^2$, answer the following questions

- (1) Find the value of R_B that makes bias current $I_B=10 \mu A$ (5%)
- (2) Find the transconductance gm_{12} (5%)

