


科目	數位電路(含邏輯設計)	適用系所	電子工程學系電路與系統組	時間	100 分鐘
----	-------------	------	--------------	----	--------

※請務必在答案卷作答區內作答。 共 2 頁第 1 頁

1a. (15%)


Use $\mu_n C_{ox} = 25\mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 10\mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$ and $V_{TP} = -1\text{V}$.

 Find V_{OH} and V_{OL} for the following CMOS gate.



1b. (10%)

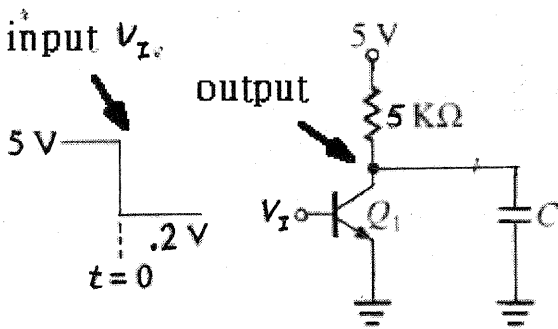Determine the output rise time for the following circuit with $C=1\text{ pF}$.



2. (25%)

Use $V_{DD} = 3.3\text{V}$, $\mu_n C_{ox} = 25\mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 10\mu\text{A}/\text{V}^2$, $V_{TN} = 0.75\text{V}$ and $V_{TP} = -0.75\text{V}$.

Find the noise margins NM_H and NM_L for a CMOS inverter having $(W/L)_N = (W/L)_P$.

3. (1) 5% Please **minimize** the following expression:

$$\overline{CD} + \overline{BCD} + \overline{ACD} + ACD$$


(2) 5% Please design and make the logic circuit as simple as possible of $Y(A, B, C, D) = \Sigma m(0, 1, 2, 3, 12, 13, 14, 15)$.

4. (1) 5% Please design a **logic gate** circuit, to implement a **De-Multiplexer** for the function of 1-2 (1-input and 2-output).


(2) 5% Please design a **concept logic circuit (block diagram only)**, to implement a **Decoder** for the function of 3-8 (3-input and 8-output) by using two 2-4 (2-input and 4-output) **Decoders**.

5. 10% Please draw the **output waveforms** for the follows logic device for \overline{Q}

(1) **D-type Flip-Flop**

 

(2) **D-type Latch**

 

6. (1) 10% Please use the **JK-FF** to design a **Synchronous counter** with the counting sequence of 0->1->2->3->4->5->6->7->0..... (repeat)

(2) 10% Please use the **D-FF** to design a **Asynchronous counter** with the counting sequence of 0->7->6->5->4->3->2->1->0.... (repeat)