

國立高雄應用科技大學
101 學年度碩士班招生考試
電機工程系

准考證號碼 (考生必須填寫)

電路學 (甲組)

試題 共 2 頁, 第 1 頁

- 注意：a. 本試題共 5 題，每題 20 分，共 100 分。
b. 作答時不必抄題。
c. 考生作答前請詳閱答案卷之考生注意事項。

1. A circuit is shown in Fig. 1, determine (1) i_s and (2) the power of the dependent current source. (20%)

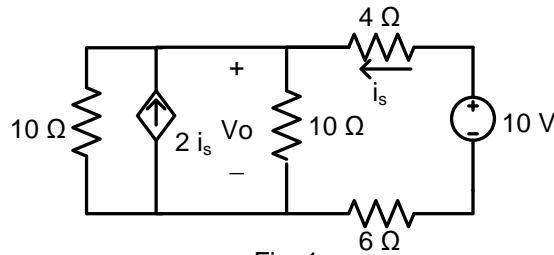


Fig. 1

2. A circuit is shown in Fig.2, use Node-Voltage-Method to calculate i_o and the power of the dependent voltage source. (20%)


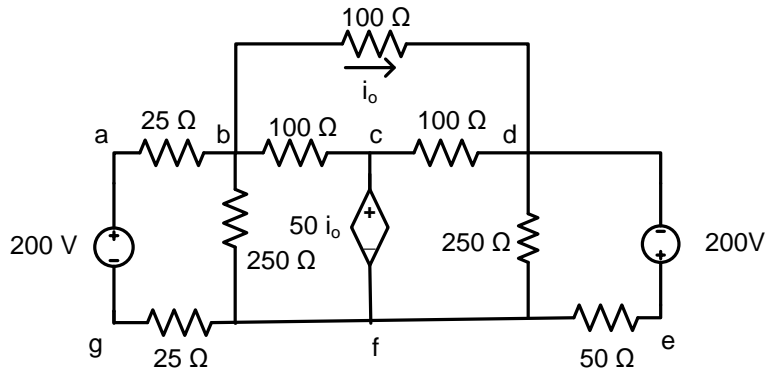


Fig. 2

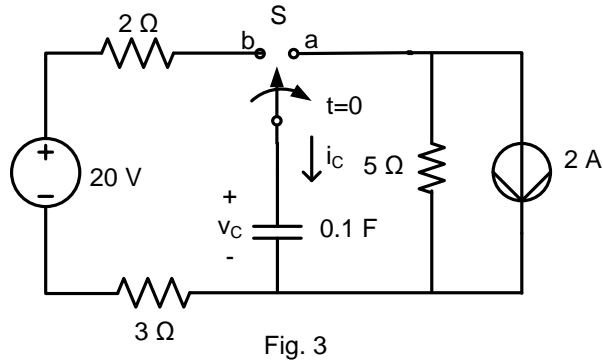3. A circuit is shown in Fig. 3, the switch S has been in position b for a long time. At $t=0$, S is moved to position a. Find (1) $v_c(t)$ $t>0$, (2) $v_c(t)=0$, $t=?$ (20%)



4. The voltage and current functions of an electrical load are as follows :

$$v=110\sqrt{2}\cos(377t) \text{ V} \quad i= 10\sqrt{2}\sin(377t+37^\circ) \text{ A}$$

Calculate average power (P), reactive power (Q), apparent power (S), and power factor (PF) of the load. (20%)

5. A circuit is shown in Fig. 4, find (1) the transfer function (V_o/V_i), (2) the output steady-state response ($v_o(t)$) as $\omega=10\text{M rad/s}$. (20%)

