

國立高雄應用科技大學
101 學年度碩士班招生考試
光電與通訊工程研究所

准考證號碼□□□□□□□□□□ (考生必須填寫)

電子學

試題 共 4 頁第 1 頁

- 注意：a. 本試題共 5 題、每題 20 分，共 100 分。
b. 作答時不必抄題，但必須書寫計算過程否則不予計分。
c. 考生作答前請詳閱答案卷之考生注意事項，各試題答案必須依題號順序寫在試卷指定的答案欄；寫錯位置不予計分。

1. For the circuit shown in Fig. 1, derive the transfer function $T(s) = V_o(s)/V_i(s)$. For $R_1 = 10 \text{ k}\Omega$, $R_2 = 40 \text{ k}\Omega$, and $C = 0.1 \mu\text{F}$, find the 3-dB frequency f_o . (20%)

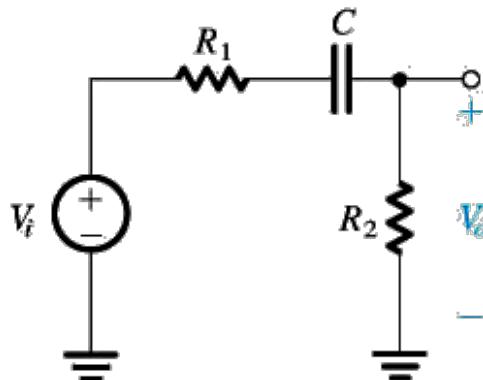


Fig. 1

2. Design the circuit shown in Fig. 2 to have an input resistance of $100 \text{ k}\Omega$ and a gain that can be varied from -1 V/V to -10 V/V using the $10 \text{ k}\Omega$ potentiometer R_4 . What voltage gain results when the potentiometer is set exactly at its middle value? (20%)

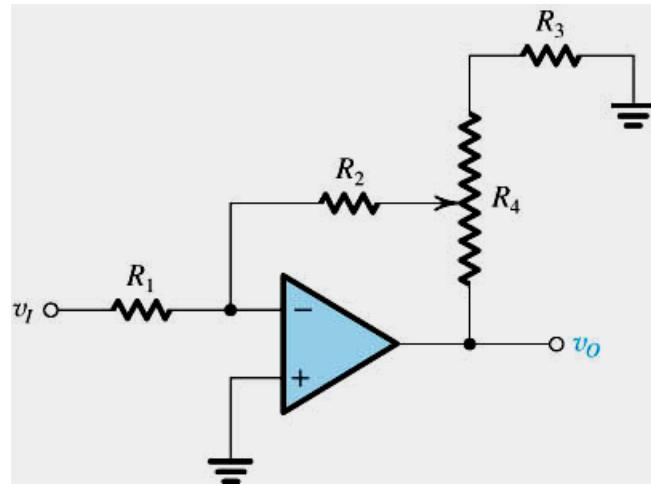


Fig. 2

3. Consider the half-wave rectifier circuit of Fig. 3 with the diode reversed. Let v_s be a sinusoid with 15 V peak amplitude, and let $R = 1.5 \text{ k}\Omega$. Use the constant-voltage-drop diode model with $V_D = 0.7 \text{ V}$. (a) Sketch the transfer characteristic. (b) Sketch the waveform of v_o . (20%)

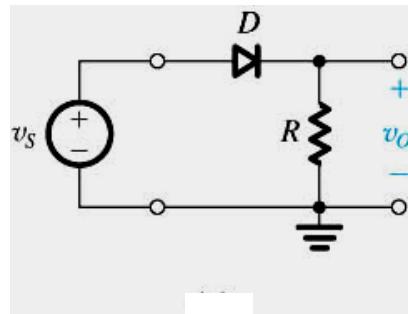


Fig. 3

試題 共 4 頁第 3 頁

4. For the circuit shown in Fig. 4, find the labeled node voltages V_1 and V_2 . The NMOS transistors have $V_t = 1 \text{ V}$, $k_n W/L = 2 \text{ mA/V}^2$, and $\lambda = 0$. (20%)

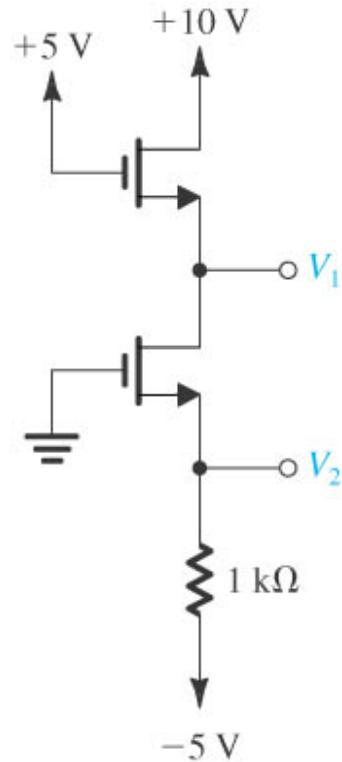


Fig. 4

5. Find the voltages at nodes V_A , V_B , V_C , and V_D in the circuit of Fig. 5. Assume $|V_{BE}| = 0.7 \text{ V}$ and $\beta = \infty$. (20%)

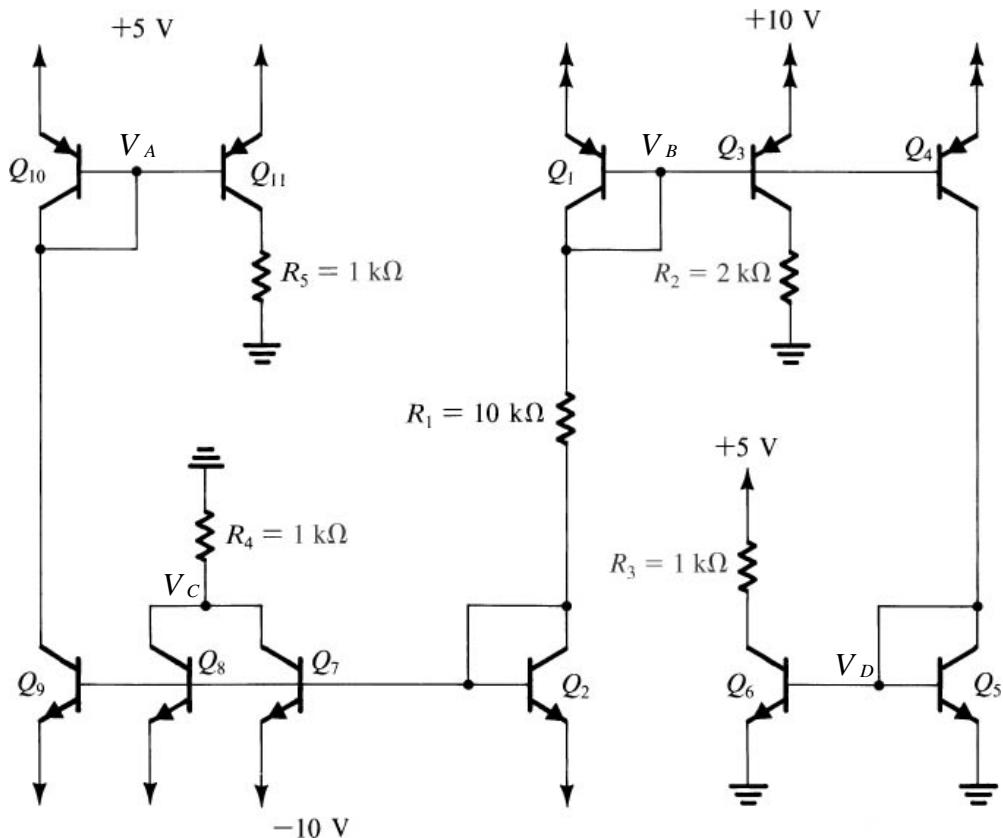


Fig. 5