



系組：電機系丙組、電機系海外、光電系、生醫所

准考證號碼：□□□□□□□

科目：電子學(145)

(請考生自行填寫)

注意事項	一、請先檢查准考證號碼、報考系(組)別、考試科目名稱，確定無誤後再作答。 二、所有答案應寫於答案紙上，否則不予計分。 三、作答時應依試題題號，依序由上而下書寫，作答及未作答之題號均應抄寫。
------	--


1. For the circuit in Fig. 1, assume that the diode has the cut-in voltage of  $V_T = 0.6$  V and the forward resistance of  $r_f = 10 \Omega$ .

(1) If  $V_{PS} = 2$  V and  $R = 2 \text{ k}\Omega$ , determine the diode voltage  $V_D$ . (5%)

(2) If  $V_{PS} = 5$  V and  $R = 2 \text{ k}\Omega$  and the diode forward resistance  $r_f$  is changed to be  $0 \Omega$ , plot the diode I-V characteristics and the load line to find the Q-point ( $V_D$  and  $I_D$ ). (5%)

(3) If  $V_{PS} = 0.2$  V and  $R = 2 \text{ k}\Omega$ , determine the diode current  $I_D$ . (5%)

Fig. 1

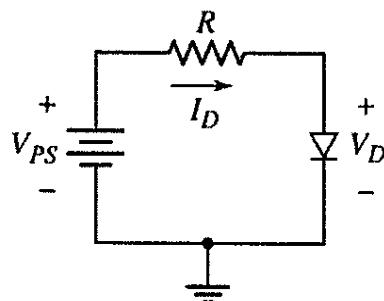

2. For the circuit in Fig. 2, the transistor parameters are:  $V_{BE(ON)} = 0.7$  V,  $\beta = 100$ , and  $V_A = \infty$ .


(1) If  $I_{CQ} = 2.16$  mA and  $V_{CEQ} = 4.81$  V, determine the value of  $R_C$ . (5%)

(2) Plot the small-signal equivalent circuit of the circuit. (5%)

(3) Determine the input resistance looking into the base of the transistor. (5%)

(4) Determine the small-signal approximate voltage gain  $A_v \approx v_o / v_s$ . (5%)


Fig. 2

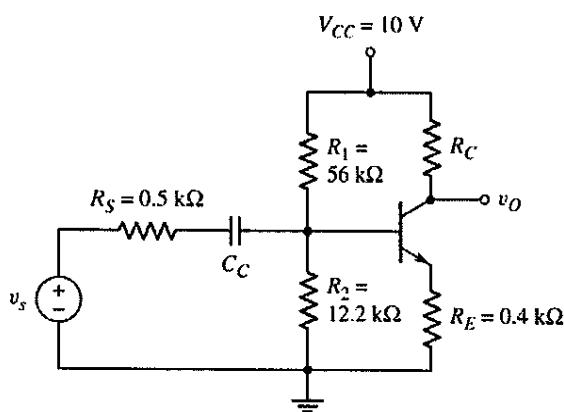

3. In Fig. 3, assume the op amps are ideal and let  $v_{I1} = 1\text{ V}$  and  $v_{I2} = 2\text{ V}$ .


- (1) Determine the output voltage  $v_o$  in Fig. 3 (a). (5%)
- (2) Determine the output voltage  $v_o$  in Fig. 3 (b). (5%)
- (3) In Fig. 3 (b), if  $R_4$  is changed to be  $55\text{ k}\Omega$ , determine the CMRR (dB). (10%)

**Fig. 3**

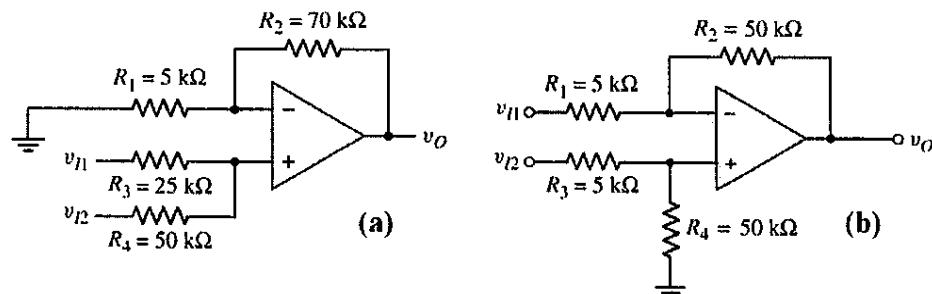

4. The circuit in Fig. 4 has  $R_D = 4\text{k}\Omega$ ,  $I_Q = 0.5\text{ mA}$  and transistor parameters  $V_{TN} = 1.5\text{ V}$ ,  $\mu_n C_{ox} = 40\mu\text{A/V}^2$ , and  $\lambda = 0$ . If the small-signal voltage gain is  $A_v = v_O / v_i = -4$ ,

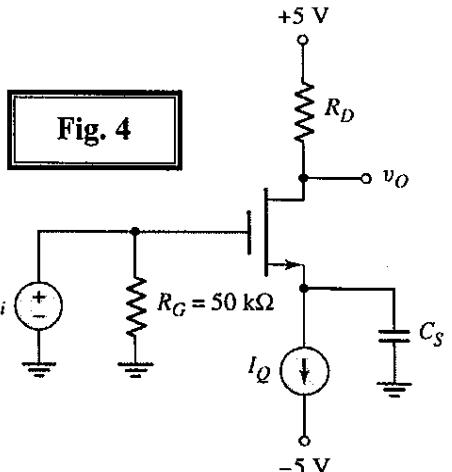- (1) Find the transconductance  $g_m$  of the transistor. (5%)
- (2) Determine the width-to-length ratio  $W/L$  of the transistor. (5%)
- (3) Calculate  $V_{GSQ}$  and  $V_{DSQ}$ . (10%)




5. Consider the circuit shown in Fig. 5. The transistor parameters are:

$$V_{TN} = 2\text{ V}, K_{n1} = K_{n2} = 0.4\text{ mA/V}^2, K_{n3} = 0.1\text{ mA/V}^2 \text{ and } \lambda = 0.$$

All transistors labeled  $M_2$  are identical.

Determine  $I_{REF}$  and  $I_O$ . (10%)

**Fig. 5**

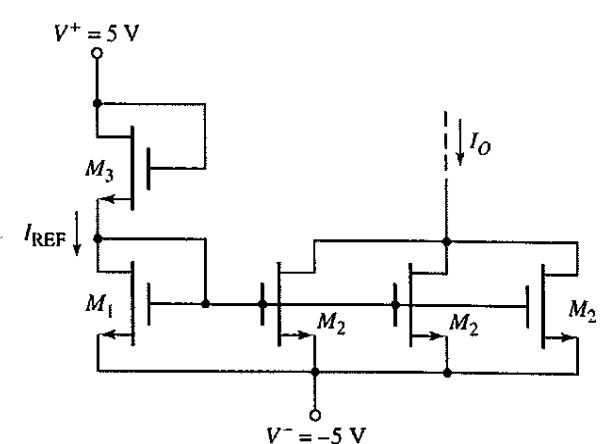

6. Consider the circuit in **Fig. 6**, with transistor parameters:  $\beta = 100$ ,  $V_{BE(on)} = 0.7\text{V}$ , and  $V_A = \infty$ .

(1) Show  $I_{C2} = \frac{I_1}{1 + \frac{2}{\beta(1 + \beta)}} \quad (5\%)$

(2) Find  $I_{C4}$  and  $V_{CE4}$ . (10%)

**Fig. 6**

