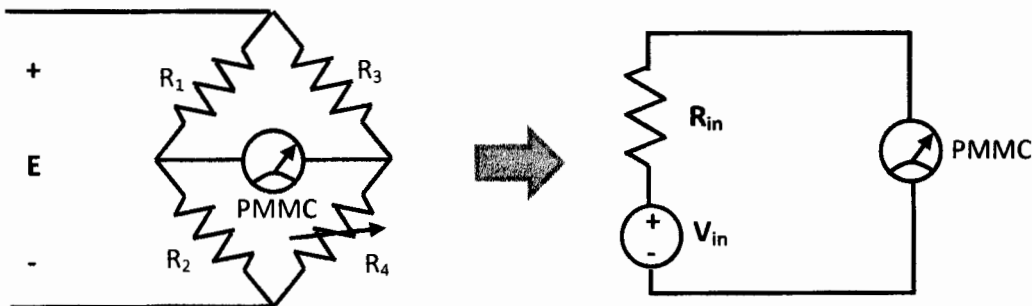


※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (10%) The current flowing through a  $1\text{ k}\Omega$ ,  $\pm 5\%$  resistor was measured as  $2.5\text{ mA}$ . The measuring error is  $3\%$ . Please calculate the possible range of the voltage across the resistor.
2. (10%) Please explain the meanings and definitions of the following two terms: (a) Accuracy (b) Precision.
3. (15%) Please list and explain the three main forces that influence the movement of the pointer in a Permanent Magnet Moving Coil (PMMC) deflection meter.
4. (15%) When calculating the sensitivity/resolution of a Wheatstone bridge using a PMMC, most of the bridge circuit can be replaced by its Thévenin equivalent circuit, as shown in the figure below. For the case that  $E=5\text{V}$ ,  $R_1=10\text{ k}\Omega$ ,  $R_3=16\text{ k}\Omega$ ,  $R_4=8\text{ k}\Omega$ , and the PMMC points at zero (i.e., the null condition is reached), please calculate  $R_{in}$  and  $V_{in}$ .




5. (a) (5%) In a frequency counter, find the frequency of a signal in Hertz if the Decimal Counting Assembly (DCA) reads 4236 and the time base is set to  $5\text{ ms}$ .  
(b) (8%) List all factors that affect time base inaccuracy and explain them briefly.
6. (a) (6%) Please define resolution bandwidth (RBW) selectivity in a spectrum analyzer.  
(b) (6%) If the settings of a spectrum analyzer are  $k = 3$ ,  $\text{RBW} = 1000\text{ Hz}$ , and  $\text{span} = 30\text{ kHz}$ , please calculate the sweep time (ST).

7. The figure below is a rectifier, where  $R_1=2k\Omega$ ,  $R_2=2k\Omega$ ,  $R_3=3k\Omega$ ,  $R_4=R_5=6k\Omega$ .

(a) (6%) Explain the operation of the circuit when a sine wave is applied to  $V_{in}$ .

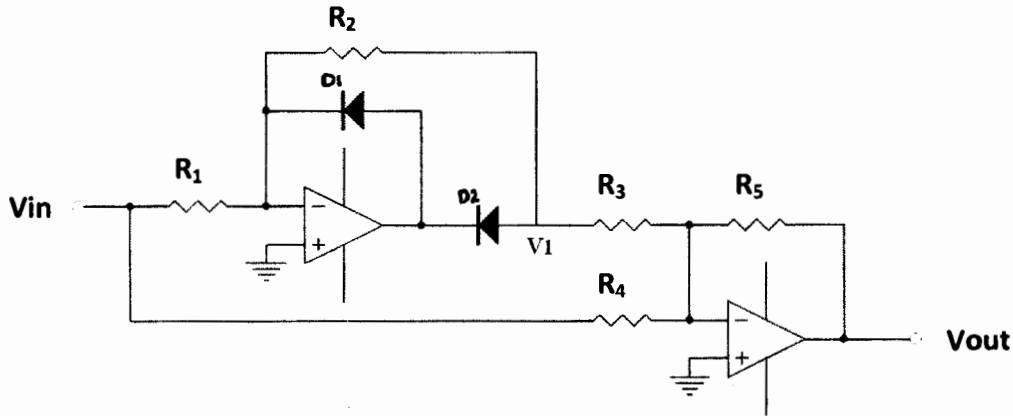(b) (6%) Plot the related waveforms of  $V_1$  and  $V_{out}$  when  $V_{in}$  is a 5Vp-p sine wave with 0.2s period.



8. The figure below is an operational amplifier voltage regulator, given that  $R_2 = 4\text{ k}\Omega$  and  $V_z = 6\text{ V}$ .

(a) (5%) If the range of  $V_o$  is 8 V-40 V, choose the proper  $R_3$  and  $R_4$ .

(b) (8%) To avoid short circuit, the current-limiting circuits are absolutely necessary in this system. Please add a current-limiting circuit for this system and explain its operation.

