

# 國立中山大學 104 學年度碩士暨碩士專班招生考試試題

科目名稱：電力工程【電機系碩士班丁組】

題號：431010

※本科目依簡章規定「可以」使用計算機（廠牌、功能不拘）（問答申論題）

共 2 頁第 1 頁

1. The impedance matrix ( $Z_{BUS}$ ) for Fig.1 can be expressed as eq. (1). (25%)  
 (a) Calculate the Z matrix after the line between Bus 2 and Bus 4 is removed; (15%)  
 (b) Assuming the bus voltages before fault are all 1.0p.u. Calculate the short circuit current when a three-phase short-circuit fault occurred at Bus 3 for (a) and bus voltages after this fault. (10%)

$$Z_{BUS} = j \begin{bmatrix} 0.71160 & 0.60922 & 0.53340 & 0.58049 \\ 0.60922 & 0.73190 & 0.64008 & 0.69659 \\ 0.53340 & 0.64008 & 0.71660 & 0.66915 \\ 0.58049 & 0.69659 & 0.66915 & 0.76310 \end{bmatrix} \quad (1)$$

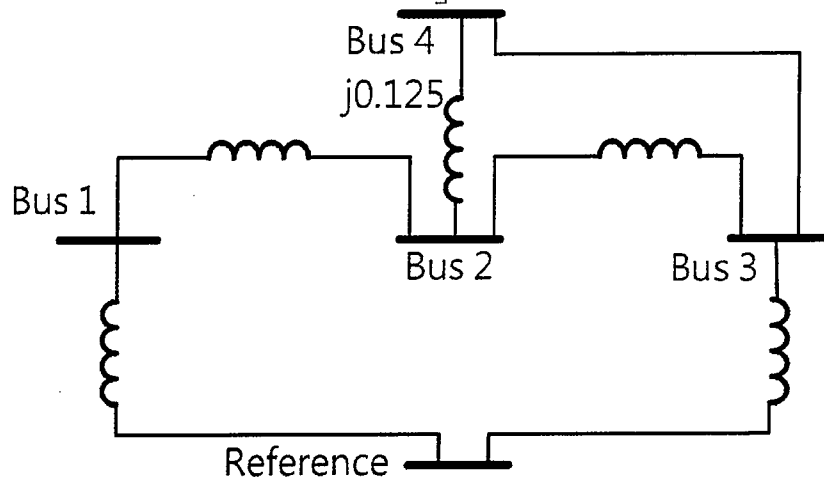


Fig. 1

2. A Y-connected load bank with a three-phase rating of 1000 kVA and 1150 V consists of three identical resistors of 1.3225 ohms. The load bank has the following applied voltages:  $V_{ab} = 920 \angle 82.8^\circ$ ,  $V_{bc} = 1380 \angle -41.4^\circ$ , and  $V_{ca} = 1150 \angle 180^\circ$  V. Determine (15%)  
 (a) the zero-, positive- and negative-sequence line-to-neutral voltages  $V_{an0}$ ,  $V_{an1}$ , and  $V_{an2}$ ; (5%)  
 (b) the zero-, positive- and negative-sequence line-to-line voltages  $V_{ab0}$ ,  $V_{ab1}$ , and  $V_{ab2}$ ; (5%)  
 (c) the zero-, positive- and negative-sequence line currents  $I_{a0}$ ,  $I_{a1}$ , and  $I_{a2}$ . (5%)  
 (All answers should be in p.u.)
3. Calculate the line flows and power flows from Bus  $i$  to Bus  $j$  and Bus  $j$  to Bus  $i$  for Fig. 2 and the line loss for this line (all values in Fig. 2 are in p.u.). (20%)

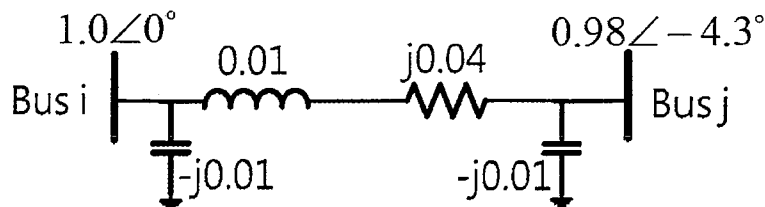


Fig. 2

4. The inertia constant (H) of a three-phase 60-Hz generator is 1.5 p.u.-s. The electrical power delivery by the generator ( $P_e$ ) versus its power angle ( $\delta$ ) can be expressed as eq. (2). The mechanical power input to the generator ( $P_m$ ) is 0.5 p.u. (25%)  

$$P_e = 1.2319 \sin(\delta) \quad (2)$$
 (a) Determine the swing equation and the initial operating power angle. (10%)  
 (b) Calculate the critical clearing time for the generator when a three-phase bolted short-circuit at the generator terminals causes  $P_e = 0$ . (15%)

國立中山大學 104 學年度碩士暨碩士專班招生考試試題

科目名稱：電力工程【電機系碩士班丁組】

題號：431010

※本科目依簡章規定「可以」使用計算機（廠牌、功能不拘）（問答申論題） 共 2 頁第 2 頁

5. Draw the phasor diagrams between the voltages and current of a synchronous generator of Fig. 3 at (a) unity power factor, (b) lagging power factor and (c) leading power factor. (15%)

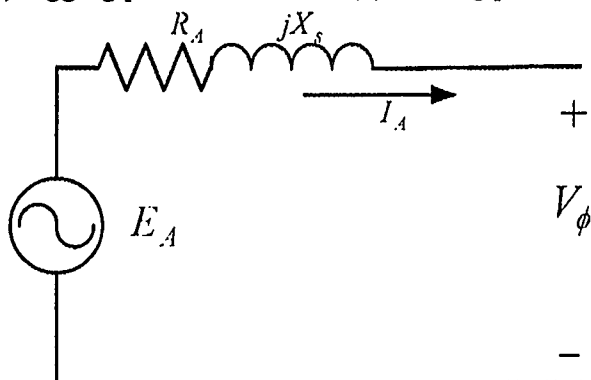


Fig. 3