

國立臺北科技大學 104 學年度碩士班招生考試

系所組別：2401 光電工程系碩士班

第三節 電子學 試題 (選考)

第一頁 共二頁

注意事項：

1. 本試題共 6 題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. For a pn junction of which the doping concentrations in the p side and n side are $N_A = 10^{17} / \text{cm}^3$ and $N_D = 10^{16} / \text{cm}^3$, respectively, please find at temperature $T = 300 \text{ K}$, (a) the built-in voltage, (b) the width of the depletion region, and (c) the distance it extends in the p side and in the n side of the junction. Use the intrinsic carrier density $n_i = 1.5 \times 10^{10} / \text{cm}^3$. (每個 5%，共 15%)
2. The op amp in the circuit of Fig.1 is ideal with output saturation levels of $\pm 12 \text{ V}$. The diodes exhibit a constant 0.7-V drop when conducting. Find V_- , V_A , and V_O for (a) $V_I = +2 \text{ V}$ (b) $V_I = -2 \text{ V}$. (每個 9%，共 18%)

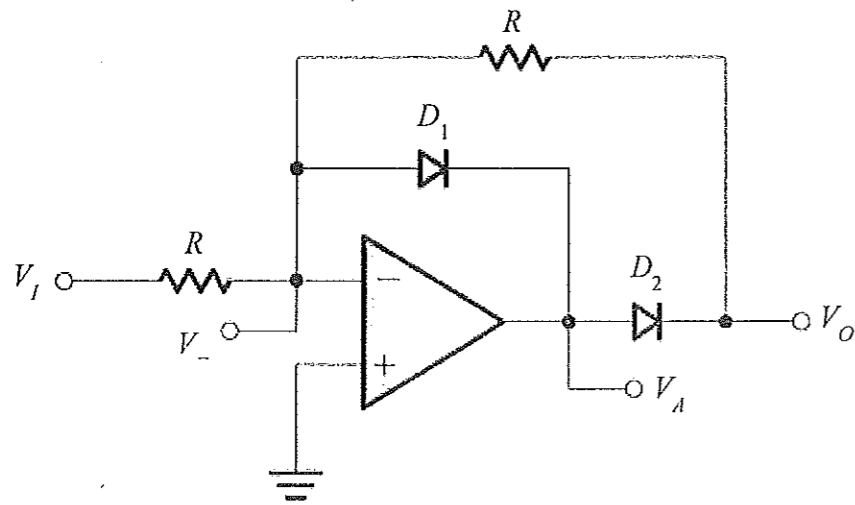


Fig. 1

3. Consider the low-frequency response of the CS amplifier of Fig. 2. Let $R_{sig} = 0.5 \text{ M}\Omega$, $R_G = 2 \text{ M}\Omega$, $g_m = 3 \text{ mA/V}$, $R_D = 20 \text{ k}\Omega$, and $R_L = 10 \text{ k}\Omega$. (a) Find midband gain $A_M \equiv V_o/V_{sig}$. (b) Also, design the bypass capacitor C_S and the coupling capacitors C_{C2} and C_{C1} to locate the three low-frequency poles at 50 Hz, 10 Hz, and 3 Hz, respectively. (c) Use a minimum total capacitance, with capacitors specified only to a single significant digit. What value of the lower 3-dB frequency f_L results? (5% , 9% , 5% , 共 19%)

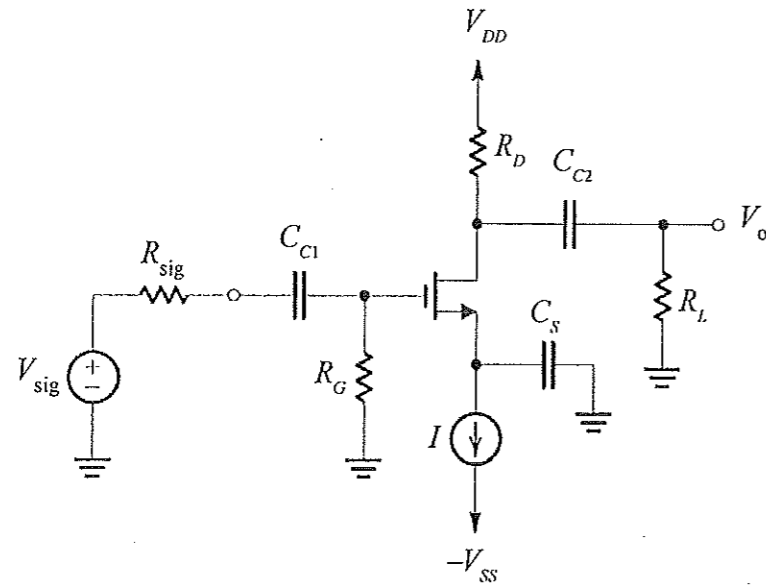


Fig. 2

4. Consider the common-emitter amplifier of Fig. 3 under the following conditions: $R_{sig} = 5 \text{ k}\Omega$, $R_1 = 33 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, $R_E = 3.9 \text{ k}\Omega$, $R_C = 4.7 \text{ k}\Omega$, $R_L = 5.6 \text{ k}\Omega$, $V_{CC} = 5 \text{ V}$. The dc emitter current can be shown to be $I_E \cong 0.3 \text{ mA}$, at which $\beta_0 = 120$, $r_o = 300 \text{ k}\Omega$, and $r_x = 50 \Omega$. Find (a) the input resistance R_{in} and (b) the midband gain A_M . If the transistor is specified to have $f_T = 700 \text{ MHz}$ and $C_{\mu} = 1 \text{ pF}$, find (c) the upper 3-dB frequency f_H . (5% , 5% , 8% , 共 18%)

注意：背面尚有試題

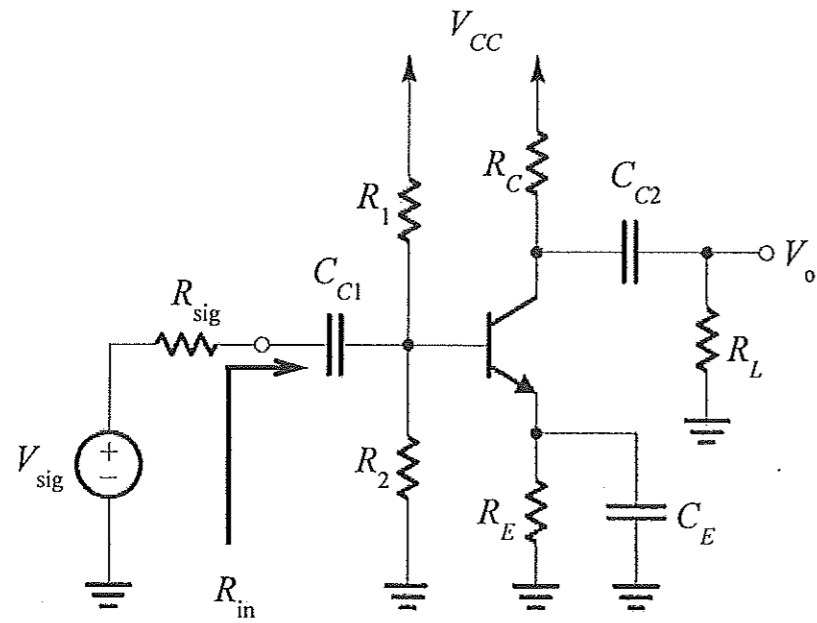


Fig. 3

5. For the series-series feedback amplifier in Fig. 4, the op amp is characterized by an open-loop voltage gain μ , an very large input resistance R_{id} , and an output resistance r_o . The amplifier supplies a current i_o to a load resistance R_L . The feedback network is composed of resistors r , R_2 , and R_1 . Please find (a) an expression for the gain-with-feedback $A_f \equiv i_o/V_s$ and (b) an expression for A_f if $\mu = \infty$. (10%, 5%, 共 15%)

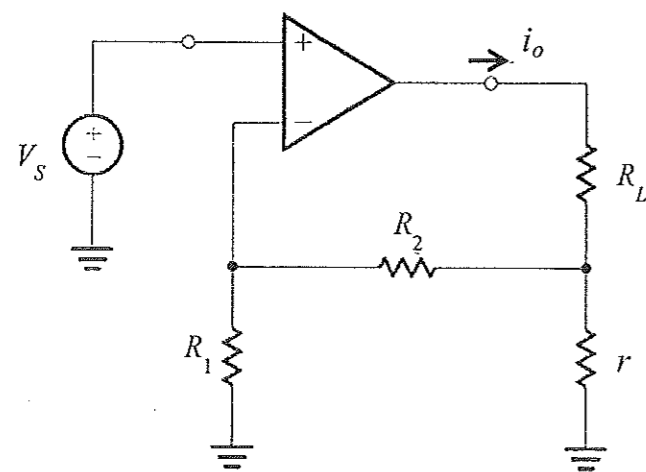


Fig. 4

6. For the circuit in Fig. 5 find (a) the loop gain $L(s)$, (b) the frequency for zero loop phase, and (c) the condition of R_2/R_1 for oscillation. (每個 5% , 共 15%)

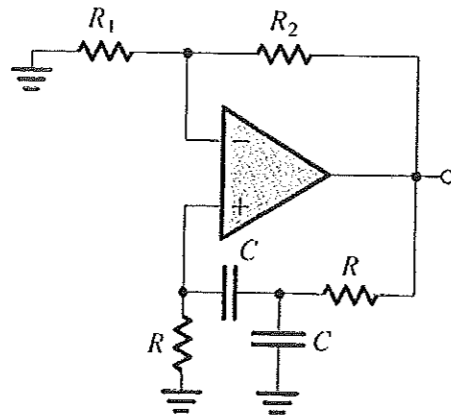


Fig. 5