

科目：電子學甲 適用：電機系(電子組)

編號：452

考生注意：

1. 依序作答，只要標明題號，不必抄題。

2. 答案必須寫在答案卷上，否則不計分。

3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題

共 3 頁

第 1 頁

1. Fill the blanks with either 0 or  $\infty$ . [6 pts, each blank 1 pts](a) An ideal current amplifier has its input resistance,  $R_{in} = \underline{\quad}$ , and output resistance,

$$R_{out} = \underline{\quad}$$

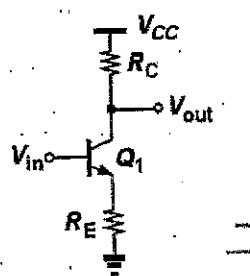
(b) An ideal operational amplifier would provide  $\underline{\quad}$  voltage gain,  $\underline{\quad}$  input impedance,  $\underline{\quad}$  output impedance, and  $\underline{\quad}$  bandwidth.2. For a saturation MOSFET, how the transconductance,  $g_m$ , changes for the following conditions? [8 pts, each blank 2 pts](a)  $W/L$  is doubled but  $I_D$  remains constant.  $g_m$  will  $\underline{\quad}$ .(b)  $V_{GS} - V_{TH}$  is doubled but  $I_D$  remains constant.  $g_m$  will  $\underline{\quad}$ .(c)  $I_D$  is doubled but  $W/L$  remains constant.  $g_m$  will  $\underline{\quad}$ .(d)  $I_D$  is doubled but  $V_{GS} - V_{TH}$  remains constant.  $g_m$  will  $\underline{\quad}$ .3. In Fig. 1, assume  $Q_1$  remains at active region, and  $V_A \neq \infty$ . Fill the blanks with either decrease or increase. When  $R_E$  becomes larger, then gain ( $v_{out}/v_{in}$ )  $\underline{\quad}$ , input resistance ( $R_{in}$ )  $\underline{\quad}$ , and output resistance ( $R_{out}$ )  $\underline{\quad}$ . [6 pts, each blank 2 pts]

Fig. 1

$$I_D = I_S e^{\frac{V_D}{V_T}}$$

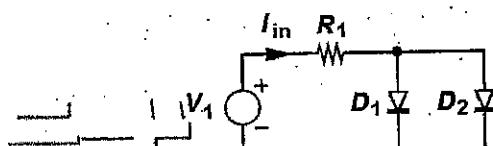


Fig. 2

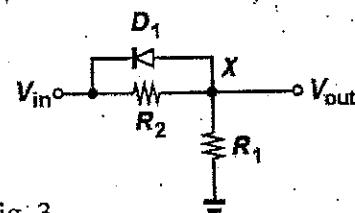
4. In Fig. 2,  $D_1$  and  $D_2$  are identical except the reverse saturation currents are  $I_{S1}$  and  $I_{S2}$ , respectively. (a) Determine the current flowing through each diode,  $I_{D1}$  and  $I_{D2}$ , in terms of  $I_{in}$ ,  $I_{S1}$  and  $I_{S2}$ . [5 pts] (b) What are the diode currents if  $I_{S1} = 4 I_{S2}$ ? [3 pts]5. If the electron density in pure silicon,  $n_i$ , is equal to  $1.0 \times 10^{10}$  electrons/cm<sup>3</sup>. A pn junction employs doping levels of  $N_A = 2.0 \times 10^{16}$  cm<sup>-3</sup> and  $N_D = 5.0 \times 10^{15}$  cm<sup>-3</sup>, where  $N_A$  and  $N_D$  are the acceptor and donor densities, respectively. Determine the majority and minority carrier concentrations on both sides. [10 pts]6. In Fig. 3,  $R_1 = 2 R_2$ . Assume  $D_1$  behaves as an ideal switch with a turn on voltage of 0.6V. Plot the input/output characteristic. [6 pts]

Fig. 3

7. Assume  $V_T = 25$  mV. An NPN transistor,  $Q_1$ , has  $\beta = 100$ ,  $V_A = 13V$ , and the following I/V characteristic shown in the table.

$V_{BE}$ (V)	0.70	0.71	0.72	0.73	0.74	0.75	0.76	0.77	0.78	0.79	0.80
$I_C$ (mA)	0.26	0.36	0.53	0.77	1.15	1.75	2.50	3.60	5.34	7.85	13.0

- (a) Find the voltage at point X in Fig. 4? [5 pts]  
 (b) For the circuit in Fig. 5, determine its operating point. [5 pts]

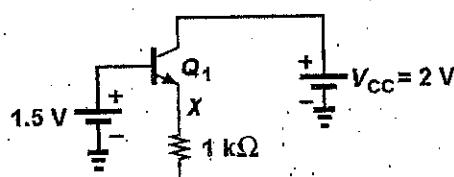


Fig. 4

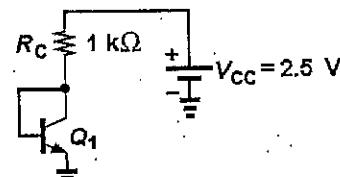


Fig. 5

8. Assume the op amp in Fig. 6 is ideal. (a) Derive the transfer function,  $V_{\text{out}}/V_{\text{in}}(s)$ . [5 pts]  
 (b) What type of filter the circuit realized? [3 pts]

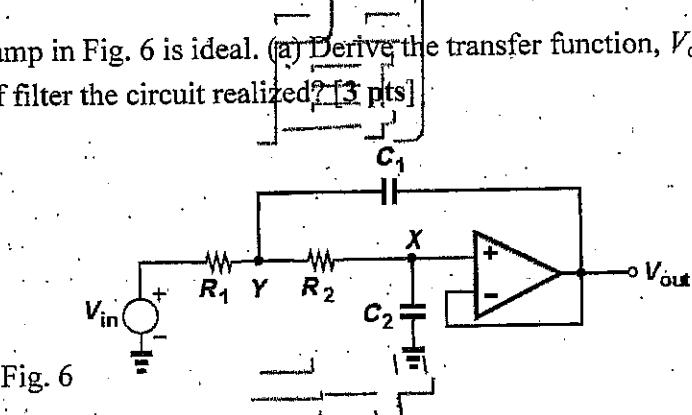


Fig. 6

9. Determine  $R_1$ ,  $R_2$ ,  $R_D$ , and  $R_S$  for the circuit in Fig. 7 with a voltage gain of 6.4,  $R_{in} = 10\text{ k}\Omega$ , and power consumption less than 4 mW. Assume  $\mu_nC_{ox} = 100\text{ }\mu\text{A/V}^2$ ,  $V_{TH} = 0.5\text{ V}$ ;  $\lambda = 0$ , and  $V_{DD} = 1.5\text{ V}$ . Also, assume  $V_{GS1}$  is 0.75 V, ( $W/L$ ) of  $M_1$  is 800, and the voltage drop across  $R_S$  is 250 mV. [12 pts]

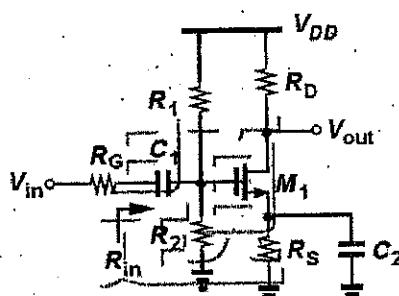


Fig. 7.

科目：電子學甲 適用：電機系(電子組)

編號：452

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題  
共 3 頁  
第 3 頁

10. Assume  $M_1$  in Fig. 8 is at saturation and  $\lambda = 0$ . Use Miller's theorem to estimate the poles of the circuit. [6 pts]

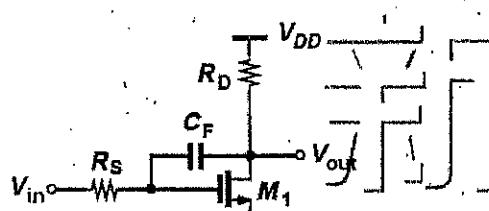


Fig. 8

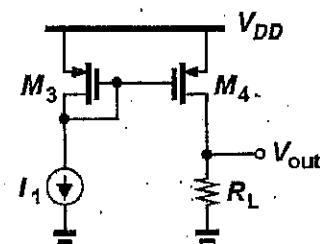


Fig. 9

11. Derive the small-signal gain  $v_{out}/i_1$  of the circuit in Fig. 9 if  $(W/L)_3 = N(W/L)_4$ . [5 pts]

12. Determine the value of  $R_P$  in Fig. 10 such that  $I_1 = I_{REF}/2$ . [5 pts]

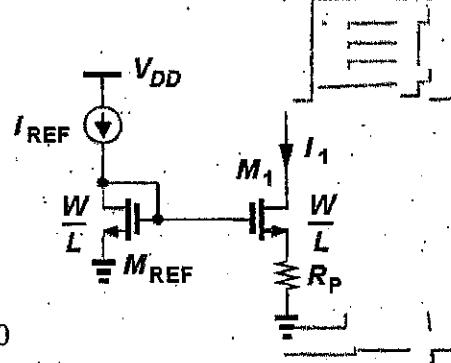


Fig. 10

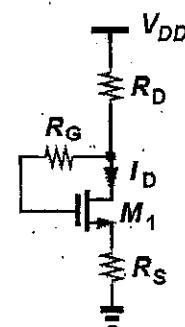


Fig. 11

13. Calculate the drain current of  $M_1$  in Fig. 11 if  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$ ,  $V_{TH} = 0.5 \text{ V}$ ,  $\lambda = 0$ ,  $V_{DD} = 2.5 \text{ V}$ ,  $R_D = 800 \Omega$ ,  $R_G = 20 \text{ k}\Omega$ ,  $R_S = 200 \Omega$ , and  $(W/L)_1 = 20$ . [10 pts]