

國立彰化師範大學 104 學年度碩士班招生考試試題

系所：機電工程學系(選考戊)

車輛科技研究所(選考戊)

電子工程學系(甲組選考乙、乙組選考丙)

電信工程研究所(選考乙)

科目：電子學

共 2 頁，第 1 頁

☆☆請在答案紙上作答☆☆

1. The circuits are connected as shown in Fig.1 with ideal diodes. Find V and I. (20%)

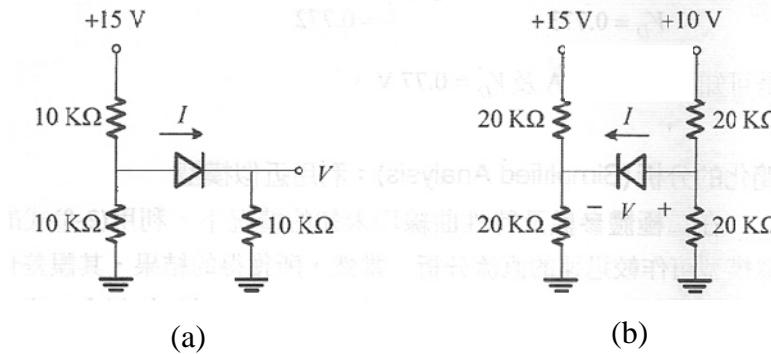


Fig.1

2. For the circuit shown in Fig.2, the transistor has $\beta=100$ and $V_A=\infty$. (a) What is the amplifier configuration? (CE, CB, CC). (b) Determine the voltage gain v_o/v_i , the input resistance R_i and the output resistance R_o . (20%)

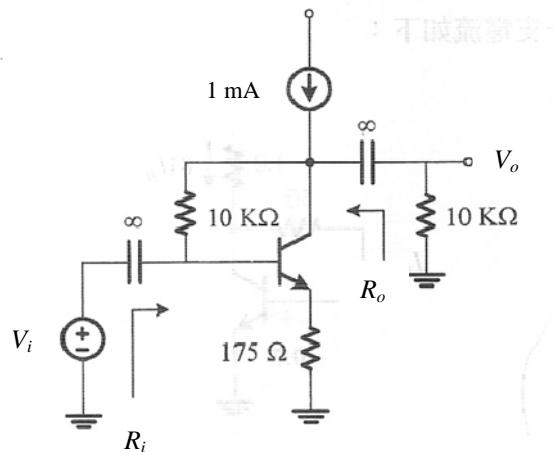


Fig.2

3. For the op amplifier circuit of Fig.3, assuming an ideal op amp, find the output voltage v_o . (10%)

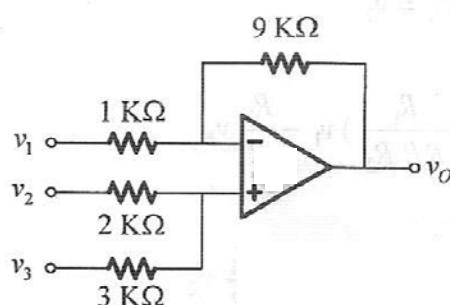


Fig.3

國立彰化師範大學 104 學年度碩士班招生考試試題

系所：機電工程學系(選考戊)

車輛科技研究所(選考戊)

電子工程學系(甲組選考乙、乙組選考丙)

電信工程研究所(選考乙)

科目：電子學

共 2 頁，第 2 頁

4. Consider the NMOS transistor in the discrete CS amplifier circuit of Fig.4 under the following conditions: $R_{sig} = 50 \text{ k}\Omega$, $R_1 = 33 \text{ M}\Omega$, $R_2 = 5 \text{ M}\Omega$, $R_D = 3.9 \text{ k}\Omega$, $R_S = 1.5 \text{ k}\Omega$, $R_L = 5.6 \text{ k}\Omega$, $C_{C1} = 0.02 \mu\text{F}$, $C_{C2} = 0.1 \mu\text{F}$, $C_S = 20 \mu\text{F}$, and $g_m = 1 \text{ mA/V}$. Find the mid band gain $A_m = v_o / v_{sig}$, f_{p1} , f_{p2} , f_{p3} and, f_L . (30%)

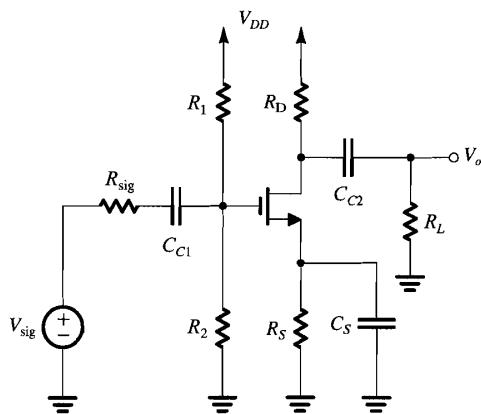


Fig.4

5. Find the voltage gain and input resistance of the amplifier in Fig.5 assuming that $\beta = 100$.

(20%)

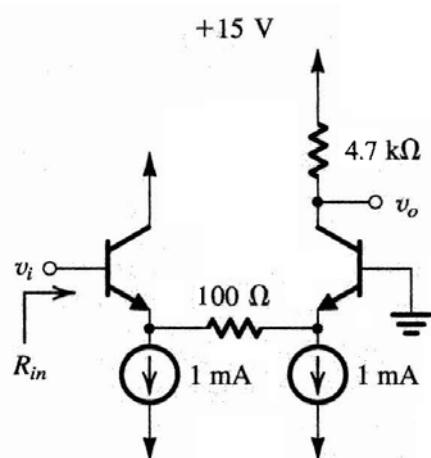


Fig.5