

國立嘉義大學 104 學年度

電機工程學系碩士班招生考試試題

科目：電子學 (可使用工程計算機)

1. If  $V_1=5 \cos 2t$  mV and  $V_2=2t$  mV, find  $V_o$  in the op amp circuit as shown in Fig. 1 below. Assume that the voltage across the capacitor is initially zero. (15 %)

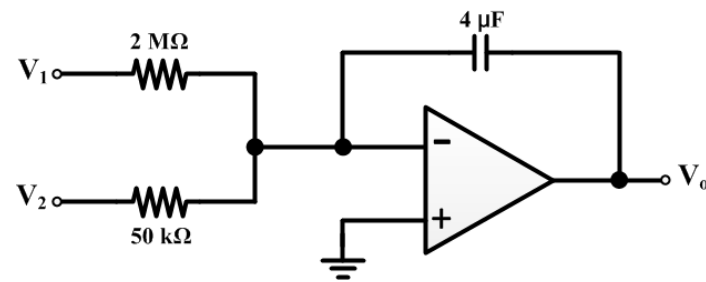


Fig. 1

2. If  $V_1=7$  V and  $V_2=3.1$  V, find  $V_o$  in the op amp circuit as shown in Fig. 2 below. (15 %)

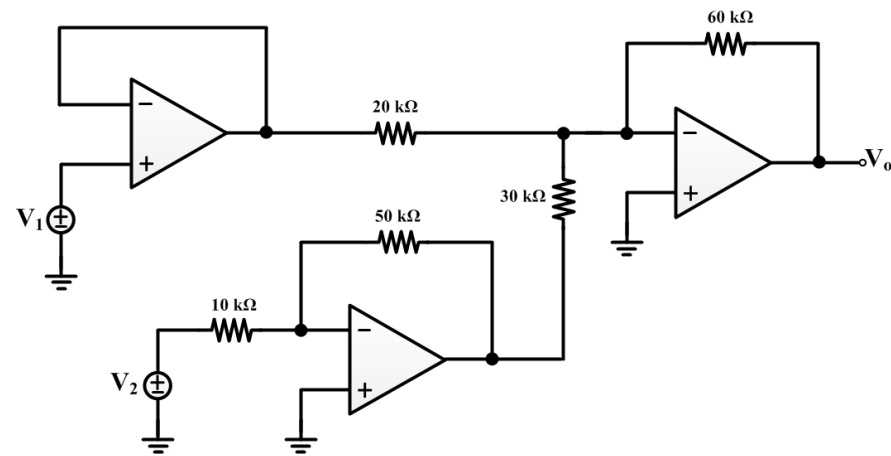


Fig. 2

3. The transistor in the circuit of Fig. 3 has a very high  $\beta$ . Assume  $V_{BE} = 0.7$  V.

Find

- (a) For  $V_B = +2$  V, find  $V_E$  and  $V_C$ . (Each answer takes 8%)  
 (b) For  $V_B = +1$  V, find  $V_E$  and  $V_C$ . (Each answer takes 8%)  
 (c) For  $V_B = 0$  V, find  $V_E$  and  $V_C$ . (Each answer takes 8%)

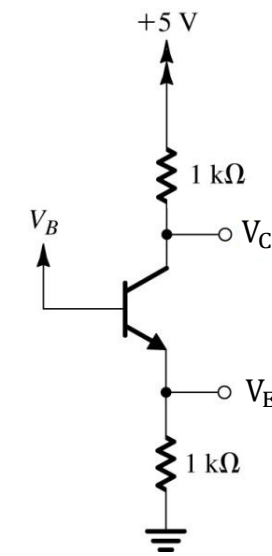


Fig. 3

4. Consider the basic BJT current mirror of Fig. 4, when  $Q_1$  and  $Q_2$  are matched devices having  $I_S = 10^{-15}$  A.
- (a) If  $\beta$  of the transistor is 20, what is the current gain " $I_O / I_{REF}$ "? Neglect the Early effect. (8%)
- (b) If  $I_{REF} = 2$  mA, and the Early voltage is 90 V. Neglecting the effect of finite  $\beta$ ,  $V_O$  changing from 1 V to 10 V, find the change in " $\Delta I_O$ ". (8%)

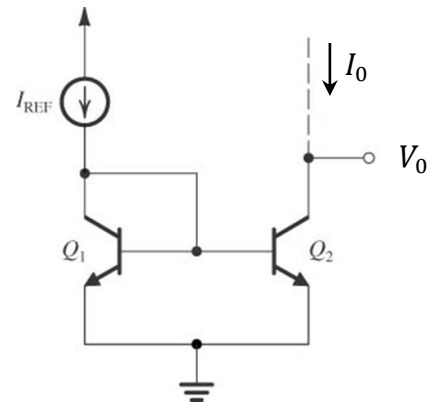


Fig. 4

5. In the circuit of Fig. 5, the NMOS transistor has  $|V_t| = 0.9$  V and  $V_A = 50$  V and operates with  $V_D = 2$  V. What is the voltage gain " $v_o/v_i$ "? (12 %)

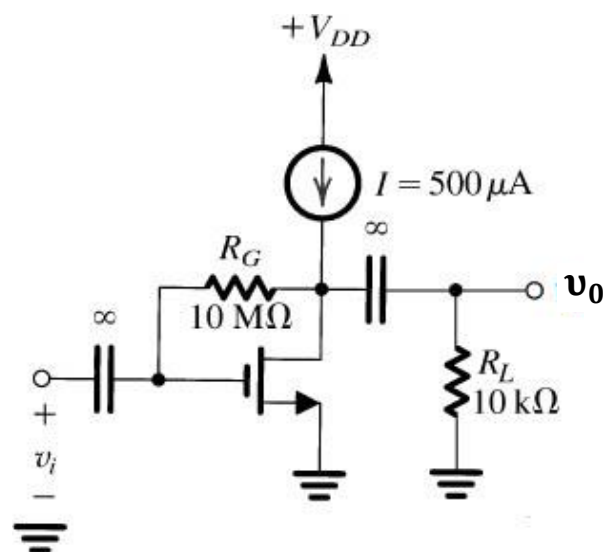


Fig. 5

6. The NMOS transistors in the circuit of Fig. 6 have  $V_t = 1$  V,  $\mu_n C_{ox} = 120$   $\mu\text{A}/\text{V}^2$ ,  $\lambda = 0$ , and  $L_1 = L_2 = 1$   $\mu\text{m}$ . Find required values to obtain the voltage and current values indicated.
- (a) Find the required value of gate width " $W_1$ " for  $Q_1$ . (6%)
- (b) Find the required value of gate width " $W_2$ " for  $Q_2$ . (6%)
- (c) Find the value of " $R$ ". (6%)

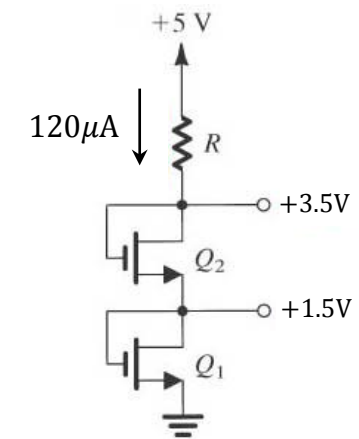


Fig. 6