
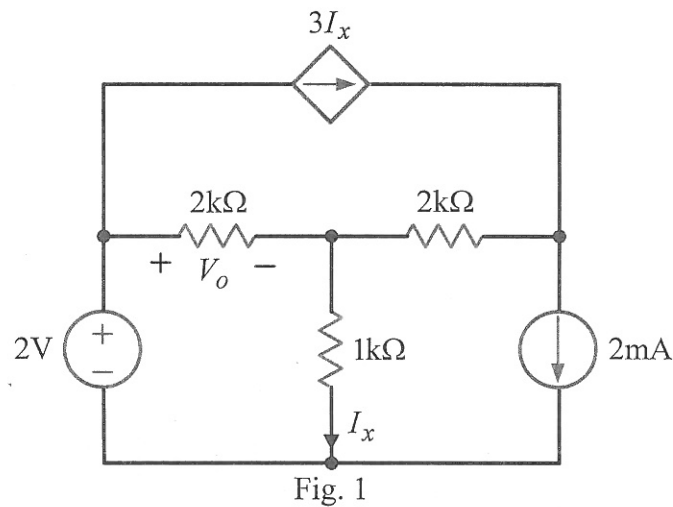


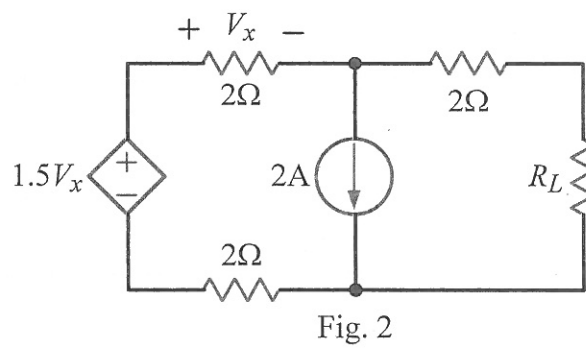
1. Find  $V_o$  in the network shown in Fig. 1. [15%]



2. Find the value of  $R_L$  in Fig. 2 for maximum power transfer. Also calculate the maximum power that can be transferred. [15%]



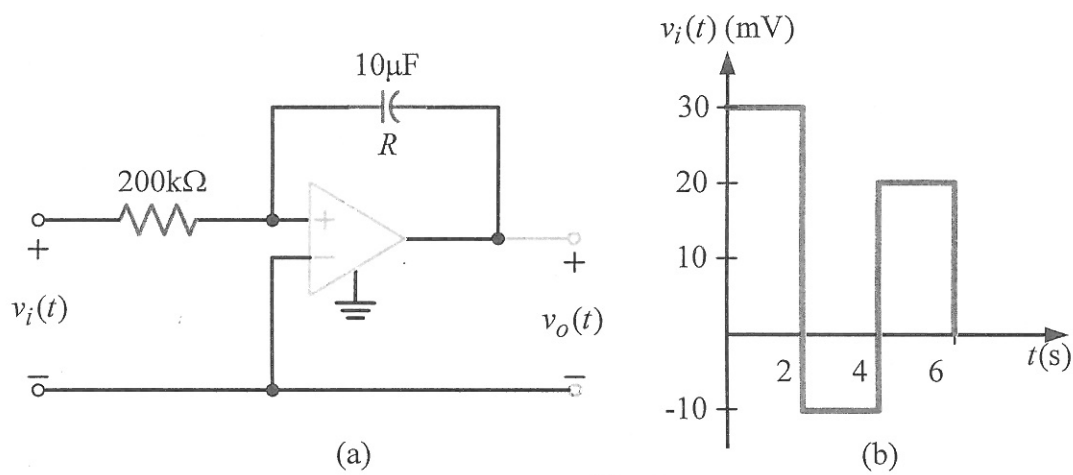3. For the op-amp circuit in Fig. 3(a), the input is given by the waveform in Fig. 3(b). Derive and plot the waveform for the output voltage  $v_o(t)$  if  $v_o(0) = 0$ . [20%]



4. Find the complex power supplied by the source, the power factor of the source, and  $V_S(t)$  if  $f = 60\text{Hz}$  in Fig.4. [18%]

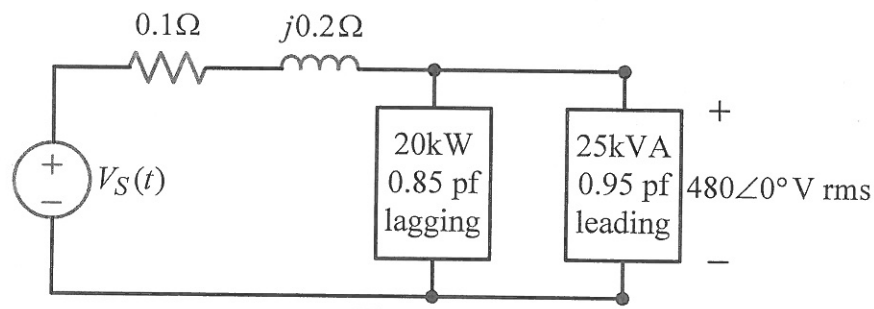


Fig. 4

5. The amplitude and phase spectra for a periodic function  $v(t)$  that has only a small number of terms is shown in Fig. 5. Determine the expression for  $v(t)$  if its period is  $T_0 = 1\text{ s}$ . [12%]

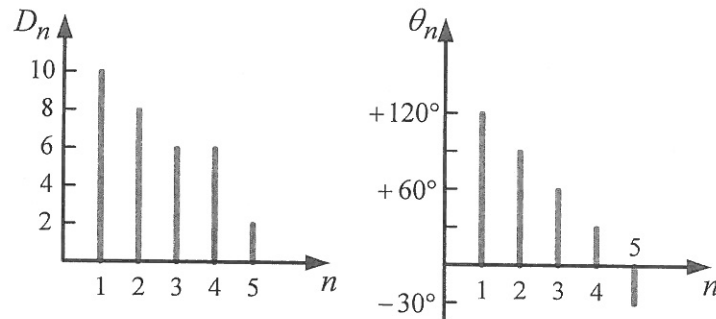


Fig. 5

- 6.(a) Determine  $Z_1, Z_2, Z_3$  so that the two-port network in Fig. 6 has the  $Z$  parameters  $[\mathbf{Z}] = \begin{bmatrix} 6+j4 & 3+j3 \\ 3+j3 & 8+j5 \end{bmatrix}$ . (b) Find the Thevenin equivalent circuit for the Part A of the circuits. (c) Determine the output voltage  $V_o$  of the network. [20%]

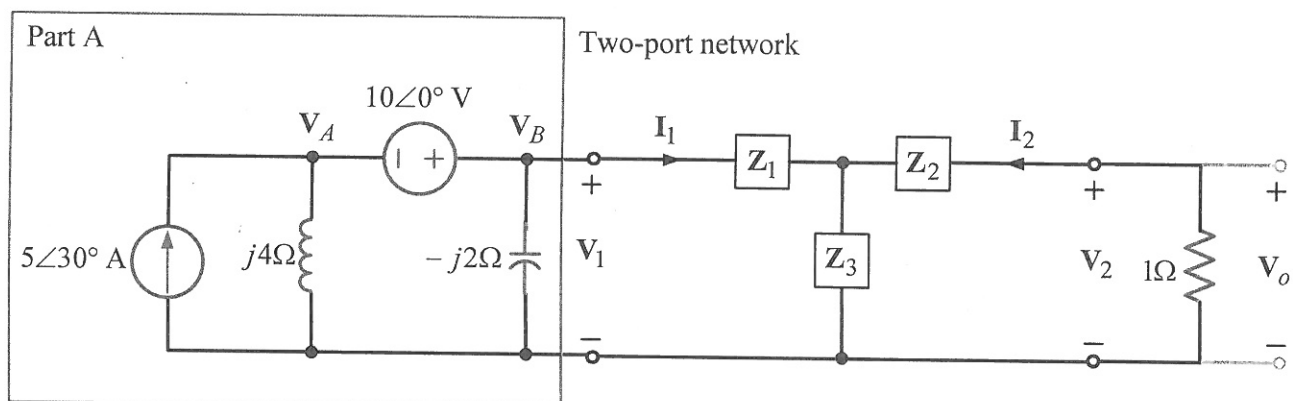


Fig. 6