

- In each of the following statements, determine whether the statement is True or False. Describe your reasons to support your choices.
 - As the biasing current increases, the MOS transconductance increases linearly with respect to biasing current. (5%)
 - The dominant current in MOS devices is drift current. (5%)
 - When the substrate reverse bias of an NMOS device is increased, the threshold voltage will decrease. (5%)

- Find the voltage gain of the differential amplifier circuit of Fig. P2 under the condition that $I_1 = 60\mu\text{A}$, $V_t = 1\text{V}$, $W_1 = W_2 = 3.5\mu\text{m}$, $L_1 = L_2 = 0.35\mu\text{m}$, $C_{ox}\mu_n = 150\mu\text{A/V}^2$, $C_{ox}\mu_p = 75\mu\text{A/V}^2$, V_A (Both NMOS and PMOS) = 20V. (10%)

 


Fig. P2


- Consider a feedback amplifier for which the open-loop transfer function $A(s)$ is given by

$$A(s) = \left(\frac{10}{1 + s/10^5} \right)^3$$


- Draw the Bode plot. (10%)
- Let the feedback factor β be a constant independent of frequency. Find the frequency ω_{180} at which the phase shift is 180° . (5%)
- Show that the feedback amplifier will be stable if the feedback factor is less than a critical value β_{cr} and find the value of β_{cr} . (10%)

4. The circuit of Fig. P4 is fabricated with the following process parameters: $C_{ox}\mu_n = 100 \mu A/V^2$, $C_{ox}\mu_p = 50 \mu A/V^2$, and $V_{tn} = |V_{tp}| = 0.5V$. Assume that $5(W/L)_{Q_{REF}} = 4(W/L)_{Q_1} = 3(W/L)_{Q_2} = 2(W/L)_{Q_3} = 1.5(W/L)_{Q_4}$, $2(W/L)_{A_1} = (W/L)_{A_2} = 20$, $L = 2 \mu m$ for Q_{A_1} and Q_{A_2} , $\lambda = 0$ for Q_{REF} and $Q_1 \sim Q_4$, $V'_A = 10 V/\mu m$ for Q_{A_1} , and $V'_A = 5 V/\mu m$ for Q_{A_2} .

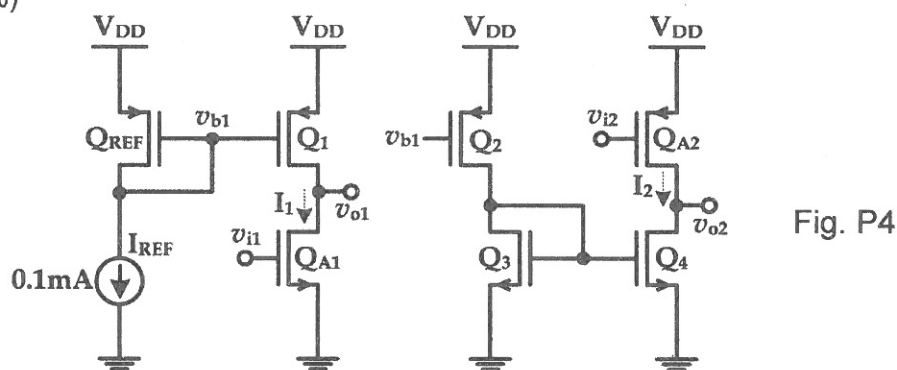- (a) Calculate I_1 and I_2 . (5%)
 (b) In case both Q_{A_1} and Q_{A_2} are biased at saturation region, please find the voltage gains v_{o1}/v_{i1} and v_{o2}/v_{i2} . (10%)



 5. (a) Please explain the miller theorem. (5%)
 (b) Please determine the input and output poles of the circuits shown in Fig. P5. Assume that the parasitic capacitances of a MOS transistor are C_{GS} , C_{GD} , and C_{DB} . (10%)



6. (a) A CMOS inverter is designated using the following parameters: $V_{DD} = 1.8 V$, $V_{tn} = 0.5 V$, $|V_{tp}| = 0.5V$, $C_{ox}\mu_n = 300 \mu A/V^2$, $C_{ox}\mu_p = 75 \mu A/V^2$, $(W/L)_{PMOS} = 1.08 \mu m/0.18 \mu m$, $(W/L)_{NMOS} = 0.27 \mu m/0.18 \mu m$, and ignore the channel length modulation. Please calculate the noise margins. (10%)

- (b) Assume that an equivalent capacitance C_L exists between the output node of the CMOS inverter and ground. In case the inverter is switched at a frequency of f Hz with a supply voltage of V_{DD} , please derive the dynamic power dissipation of the inverter. (5%)
 (c) If two CMOS inverters are designated with the characteristics shown in Fig. 6P(a), please sketch the overall voltage-transfer characteristic (VTC) for the circuit configurations shown in Fig. 6P(b). (5%)

