
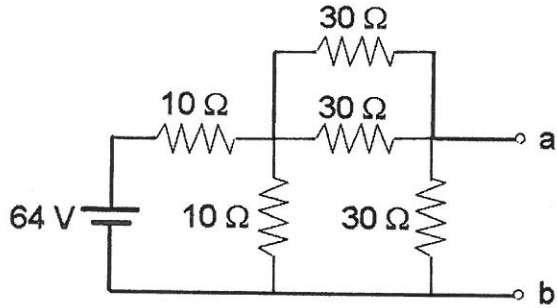


1. (15%) Determine the Thevenin equivalents of the following circuits as seen from nodes a and b.


(a) (5%)

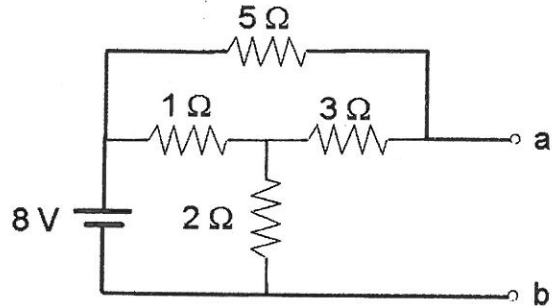


(b) (5%)




(c) (5%)

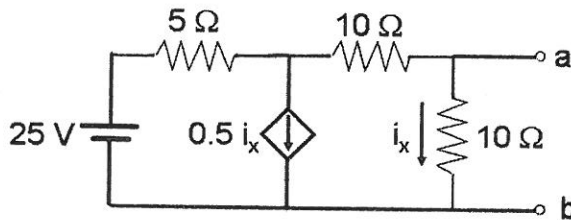

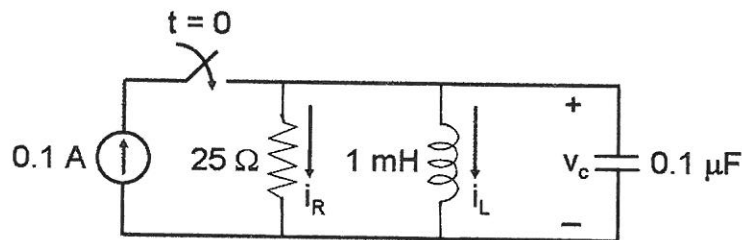2. (25%) Consider the following RLC circuit with initial values $i_L(0^-) = 0$ and $v_c(0^-) = 0$.




- (5%) Without solving the governing differential equation, determine $i_L(0^+)$, $v_c(0^+)$, and $i_R(0^+)$ immediately after the switch was turned on at $t = 0$. Justify your answer.
 - (5%) Without solving the governing differential equation, determine the steady states of $i_L(t)$, $v_c(t)$, and $i_R(t)$ as t goes to infinity. Justify your answer.
 - (5%) Write down the governing differential equation of the circuit in terms of $v_c(t)$.
 - (5%) What are the natural frequency and damping ratio of the circuit.
 - (5%) Solve explicitly for $v_c(t)$, $t > 0$.
3. (10%) Consider the following RLC circuit.

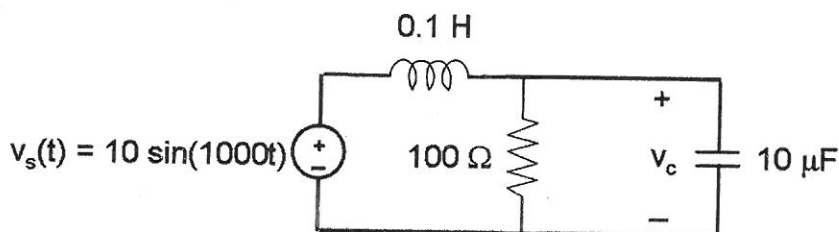


- (a) (5%) Express the circuit in terms of phasor and impedance.
- (b) (5%) Determine the phasor and corresponding time function of $v_c(t)$.

4. (22%) Find the small signal gain $\frac{\hat{v}_b}{\hat{v}_a}$ for each of the following circuits.


(a) (4%)

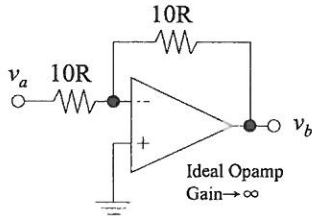


(b) (4%)

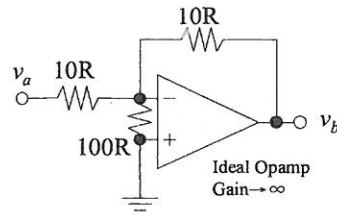


(c) (4%)

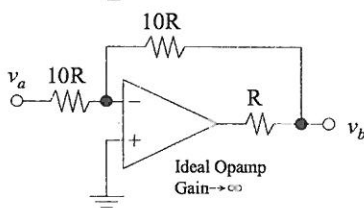

(d) (5%)

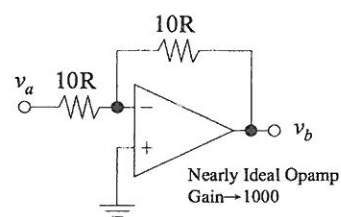

(e) (5%)

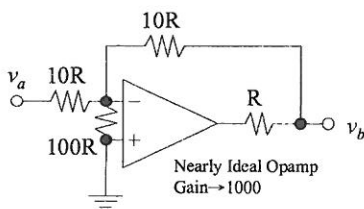

5. (12%) A common-source amplifier with its corresponding input and output waveforms are shown in Fig. 5-1. The input signal (v_a) is a 1V peak to peak sinusoid biased at V_{OP} with 500 μ s period; the output signal (v_b) is also a sinusoid signal with the same frequency but nearly 180 degree phase shift. $R_0=30$ k Ω and $R_1=20$ k Ω . The drain characteristic (I-V curve) of MOSFET (M) is shown in Fig. 5-2. For each question in the follows, please select the best answer from the provided options. Remember to provide justifications for your answers.

- (a) (4%) What is the value of R_2 ? (A) 1k Ω ; (B) 2k Ω ; (C) 3k Ω ; (D) 5k Ω .
- (b) (4%) What is the value of the capacitor C ? (A) 1 μ F; (B) 1nF; (C) 1pF; (D) 1fF.
- (c) (4%) What is the value of the MOSFET threshold voltage V_{TH} ? (A) 3.2V; (B) 1.5V; (C) 0.7V; (D) 0.2V.

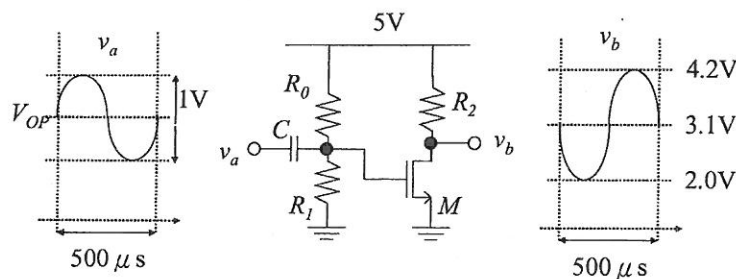


Fig. 5-1

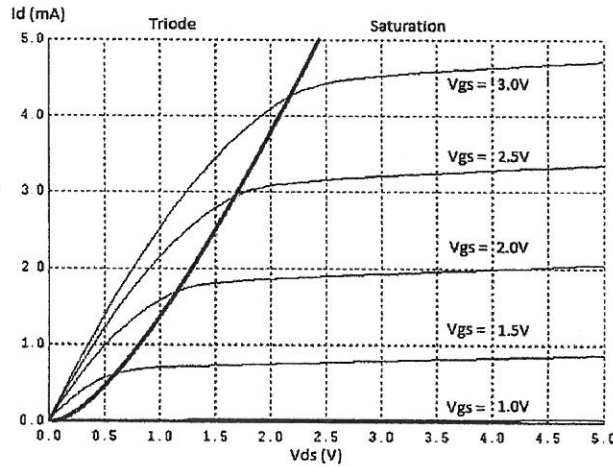


Fig. 5-2

6. (16%) Now, replace the circuit in Fig. 5-1 with the one in Fig. 6. The input (v_a) and output signals (v_b) are same as those in Problem 5. The drain characteristics of both MOSFETs (M) are the same and shown in Fig. 5-2. Both pnp transistors (Q) are operated in linear-active region with the base-emitter voltage $V_{BE}=0.7V$ and the collector to base current gain $\beta=10$. The voltage drop of the diode (D) is $1V$ ($V_D=1V$). $R_3=10k\Omega$ and $R_4=4k\Omega$. For each question in the following, please select the best answer from the provided options. Remember to provide justifications for your answers.

- (a) (4%) What is the value of V_{op} ? (A) 2.7V; (B) 3.0V; (C) 0.7V; (D) 4.0V.
- (b) (4%) What is the DC value of v_c ? (A) 3.2V; (B) 2.1V; (C) 1.0V; (D) 3.6V.
- (c) (4%) What is the DC value of load current i_L ? (A) 10mA; (B) 11mA; (C) 12mA; (D) 110mA.
- (d) (4%) If R_3 is removed, what is the possible DC value of v_c ? (A) 3.2V; (B) 2.1V; (C) 1.0V; (D) 3.6V.

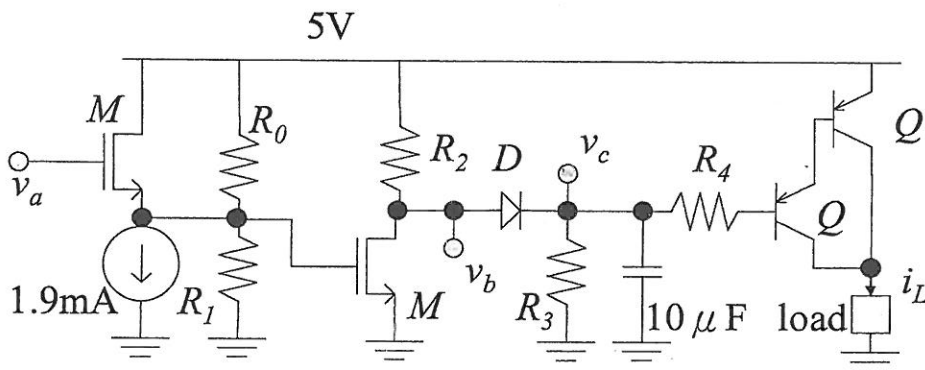


Fig. 6