

[Problem 1] Please use one 4-bit adder, one 2-bit adder, and a few logic gates (AND, OR, or NOT) to implement a one-digit BCD adder with one carry-in bit and one carry-out bit. Please note that the details of the adders are no need to show. (20%)

[Problem 2] In addition to the BCD code, 2-4-2-1 code listed below is also a useful coding to represent decimal digits in self complementing manner. Please design a function  $F$  to check if the decimal input encoded by 2-4-2-1 code can be exactly divided by three. In other words,  $F = 1$  if and only if the remainder of the division by 3 is zero. Make the truth table of this function and design the two-level NOR-NOR network with minimum number of logic gates and literals. Note that the input code words ( $a, b, c, d$ ) and their complements can be used directly as fan-in in the logic circuit. (15%)

Table 1

Decimal digit	8-4-2-1 Code (BCD)	2-4-2-1 Code
0	0000	0000
1	0001	0001
2	0010	0010
3	0011	0011
4	0100	0100
5	0101	1011
6	0110	1100
7	0111	1101
8	1000	1110
9	1001	1111

[Problem 3] The sequential circuit in figure 1 has one input signal  $X$  that is synchronized with the clock and one output signal  $Z$ .

(a) Complete the state table. (6%)

(b) It is known that this circuit is a sequence detector and is initialized to  $AB = 00$  when powered up.

What sequence(s) does it detect? (9%)

 


Figure 1

國立中山大學100學年度碩士班招生考試試題

科目：數位電路【電機系碩士班丙組選考、庚組】

[Problem 4] A Moore sequential network has one input and one output. When the input sequence 101 occurs, the output becomes 1 and remains 1 until the sequence 101 occurs again, in which case the output returns to 0. The output then remains 0 until 101 occurs a third time, and so forth. For example, the input sequence

$$X = 0101101011010011$$

has the output

$$Y = 00011110011100000$$

Derive the state diagram with a minimum number of states. Notice that you have to verify that the number of state in your design has been minimized. (15%)

[Problem 5] A timing chart as below is recorded on a Mealy machine with one input X, one output Z, and two JK flip-flops. Construct the state table and draw the sequential circuit. (15%)

 


Figure 2

[Problem 6] A switching network has three inputs and two outputs,  $a$  and  $b$ , which represent the first and second bits of a binary number ( $N$ ) respectively. Here  $N$  equals the number of inputs which are 0. For example, if  $x = 1, y = 0,$  and  $z = 0,$  then  $a = 1, b = 0.$  Please implement this network with two 4-to-1 multiplexers. (20%)

 


Figure 3