

國立中山大學100學年度碩士班招生考試試題

科目：電路學【電機系碩士班丁組】

- 1.(10pt) A battery is discharged by a constant current 5A for 5 hours. If the terminal voltage of the battery is  $(12-0.2t)$  V, where  $t$  is in hour. Draw output power-time and output energy-time waveforms of the battery for  $0 < t < 5$ , respectively.
- 2.(10pt) For a balanced three-phase system, a-phase voltage and current are described as  $v_a(t)=100\cos\omega t$  V,  $i_a(t)=10\sin(\omega t+60^\circ)$  A. Find power factor, instantaneous power, average power, reactive power, apparent power of this balanced three-phase system.
- 3.(10pt) The voltage  $v(t)=5+3\cos(t+30^\circ)+\sin(3t+20^\circ)+\cos(5t+10^\circ)$  V is applied to a  $5\Omega$  resistor. Calculate the rms current flowing through the resistor and power consumption on it.
- 4.(10pt) Find  $V_1$  and  $V_2$  in Fig. 1.

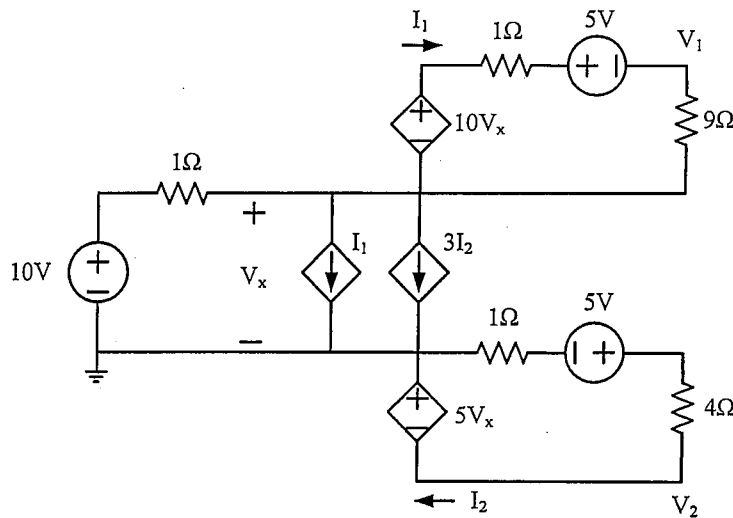


Fig. 1

- 5.(20pt) Assume the circuit of Fig. 2 is at the steady state before  $t=0$ s. The ideal switches  $S_1$  is open at  $t=0$ s. Find  $i(t)$  and  $v(t)$  for  $t>0$  if  $R=0$  and  $R=4\Omega$ , respectively.

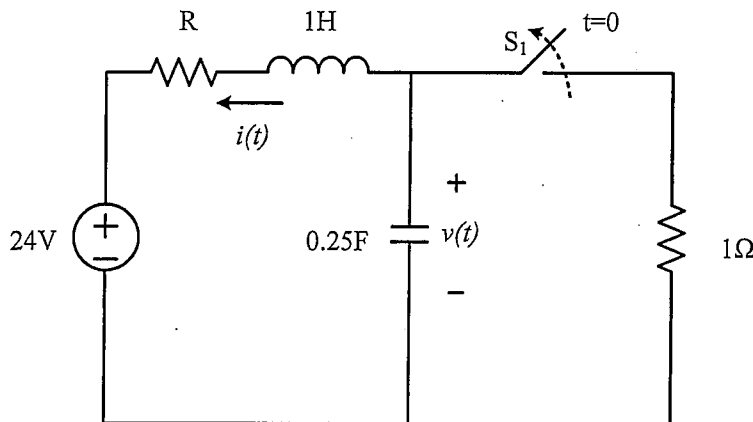


Fig. 2

## 國立中山大學100學年度碩士班招生考試試題

科目：電路學【電機系碩士班丁組】

- 6.(20pt) Calculate average power on all resistors and reactive power on all reactive components in the circuit of Fig. 3.

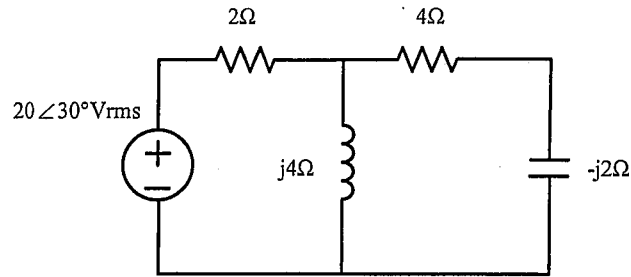


Fig. 3

- 7.(10pt) In Fig. 4, the turn ratio of the ideal transformer is 1:2. Find  $V_o$  and complex power supplied by the source.

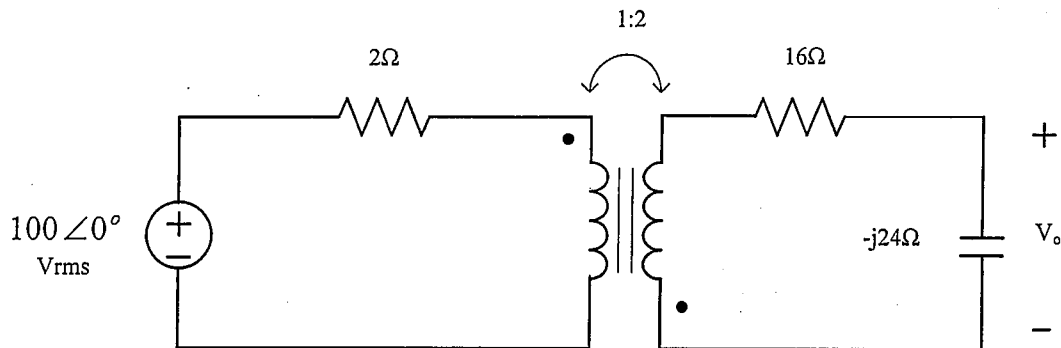


Fig. 4

- 8.(10pt) Solar energy is becoming increasingly popular recently. Generally, variable power with low dc voltage is produced by the solar panel. So, please describe how to use power electronics converters to deliver the generated power to the utility grid.