
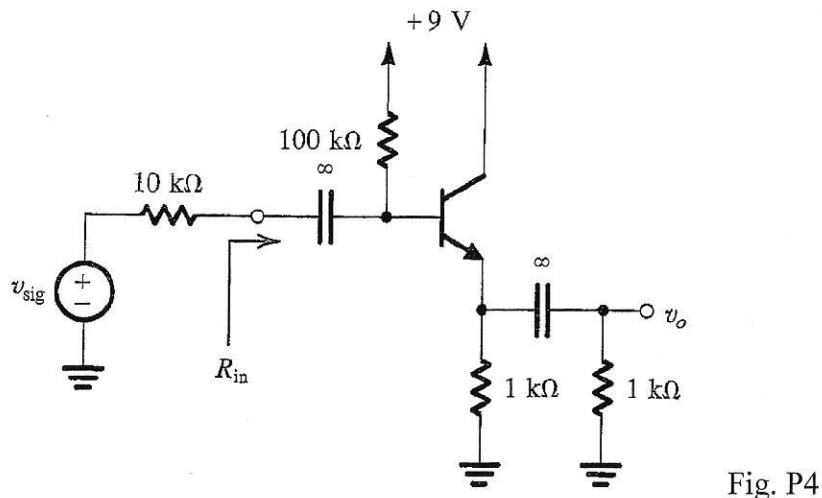
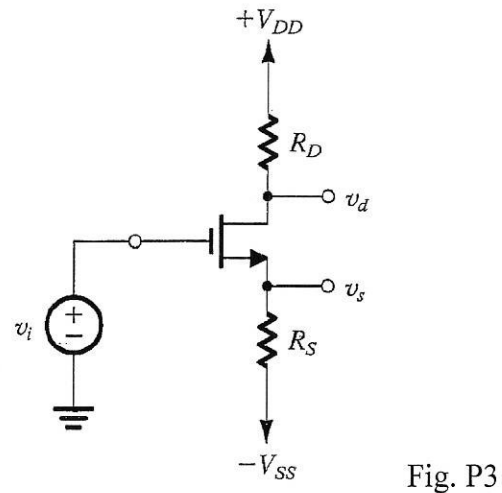


招生學年度	105	招生類別	碩士班
系所班別	電機工程學系碩士班		
科目名稱	電子學		
注意事項	本考科可使用掌上型計算機		

- (10 分) Electrons are being steadily injected into a region of p -type silicon. In the steady state, the excess electron concentration profile shown in Fig. P1 is established in the p -type silicon region. If $N_A = 10^{16} \text{ cm}^{-3}$, $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, and $W = 5 \mu\text{m}$, find the current density that will flow in the x direction. Hint: $D_n = 34 \text{ cm}^2/\text{s}$ and $D_p = 12 \text{ cm}^2/\text{s}$.
- (10 分) Sketch the physical structure of a NMOS transistor. Indicate the source, drain, gate, oxide, body, and channel while the transistor is turned-on.
- (15 分) For the NMOS amplifier in Fig. P3, replace the transistor with its T equivalent circuit. Derive expressions for the voltage gains v_s/v_i and v_d/v_i . Hint: Neglect the Early effect.
- (15 分) For the emitter-follower circuit shown in Fig. P4, the BJT has $\beta = 100$. Assume $V_{BE} = 0.7 \text{ V}$. Find (a) I_E , V_E , and V_B , (b) the input resistance R_{in} , and (c) the voltage gain v_o/v_{sig} .

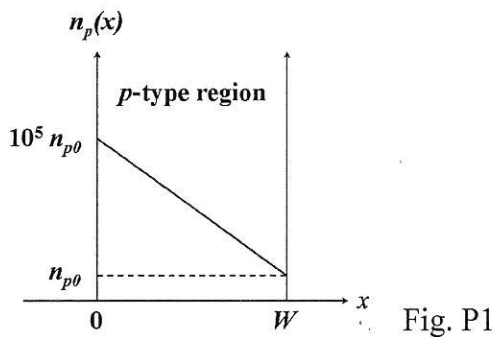

招生學年度	105	招生類別	碩士班
系所班別	電機工程學系碩士班		
科目名稱	電子學		
注意事項	本考科可使用掌上型計算機		

- (20 分) Estimate the G_m and voltage gain of the differential amplifier as shown in Fig. P5. Notice that $V_{DD}=3V$, $I_B=50\mu A$, $V_t=1V$, $(W/L)_{N1}=(W/L)_{N2}=100$ $(W/L)_{P1}=(W/L)_{P2}=200$, $\mu_n C_{ox}=200\mu A/V^2$, $\mu_p C_{ox}=100\mu A/V^2$, $V_{AN}=|V_{AP}|=20V$.
- (20 分) Two amplifiers are connected in series and with midband gain of A_1 and A_2 (Fig. P6). Their high-frequency dominant poles are ω_1 and ω_2 , respectively. Answer the following questions.
 - Find the high frequency response for $H(s)=V_o(s)/V_i(s)$ of the system.
 - If $\omega_1 \ll \omega_2$, please depict the Bode plot of $H(s)$ for ω in the range of $0.1\omega_1 < \omega < 10\omega_2$.
- (10 分) Fig. P7 shows a feedback amplifier with three BJTs, Q_1, Q_2, Q_3 . Notice that currents on BJTs are $I_{C1}=0.5mA$, $I_{C2}=1mA$ and $I_{C3}=5mA$. Also β is assumed 100 and $r_o=\infty$. Please calculate the closed-loop voltage gain which is defined as $A_f \equiv V_o/V_i$.

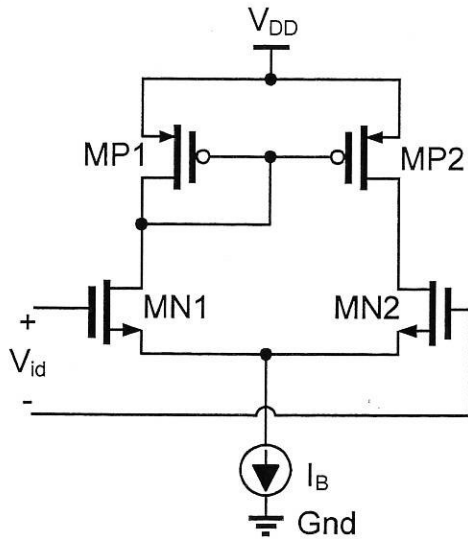


Fig. P5 Differential amplifier with active load.

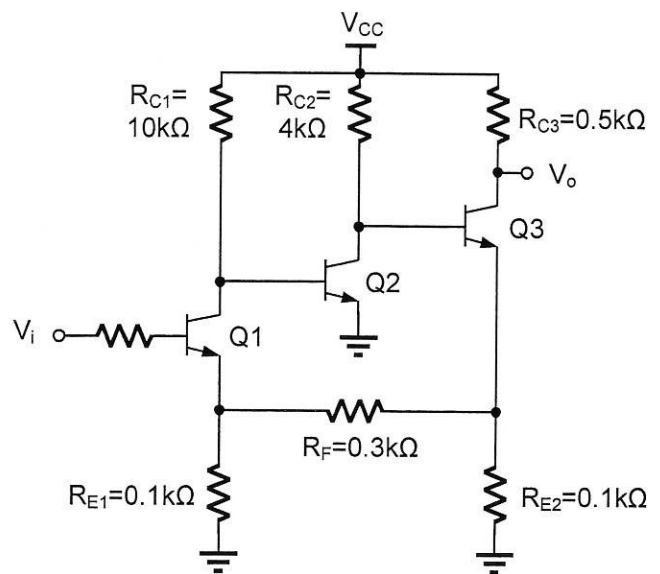


Fig. P7 Feedback amplifier.

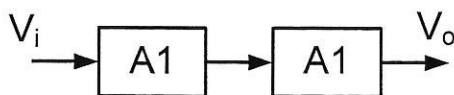


Fig. P6