

國立高雄應用科技大學  
106 學年度研究所碩士班招生考試  
電機工程系碩士班  
電路學(甲組)

試題 共 2 頁，第 1 頁

注意：a. 本試題共五題，每題 20 分，共 100 分

b. 作答時不必抄題

c. 考生作答前請詳閱答案卷之考生注意事項

1. The current  $i_a$  in the circuit shown in Fig. 1 is 2A, find (a) the value of voltage source  $v_s$  (b) the power delivered by the controlled current source.

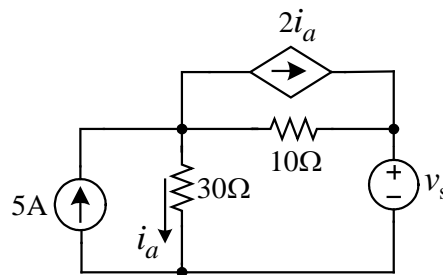


Fig. 1

2. The circuit in Fig.2 has initial inductor current  $i_L(0) = -45\text{mA}$ , and initial capacitor voltage  $v(0) = 15\text{V}$ . Find  $v(t)$  for  $t \geq 0$ .

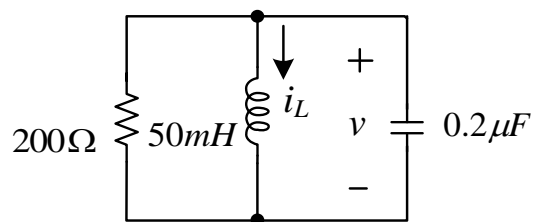


Fig.2

【背面尚有試題】

3. For the circuit in Fig.3, if  $i_g$  is the input signal and  $v_o$  is the output signal.
- Find the numerical expression of the transfer function in s-domain.
  - Give the numerical value of each pole and zero of the transfer function.

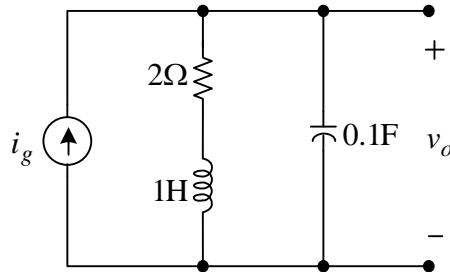


Fig. 3

4. The voltage source in the phasor-domain circuit shown in Fig.4 is  $\mathbf{V}_g = 240\angle 0^\circ \text{ V(rms)}$ . Find the average power and reactive power delivered from the voltage source.

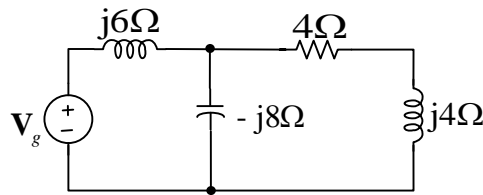


Fig. 4

5. Find  $I_1$  and  $I_2$  if the transmission parameters for the two-port circuit in Fig. 5 are

$$\begin{bmatrix} 5 & 10\Omega \\ 0.4\text{S} & 1 \end{bmatrix}$$

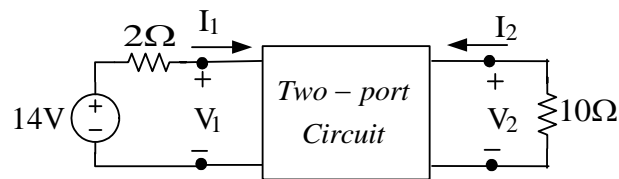


Fig. 5