

# 國立臺北大學 106 學年度碩士班一般入學考試試題

系（所）組別：電機工程學系甲組（晶片設計組）

科目：電子學 B

第 1 頁 共 2 頁

☐可 ☒不可使用計算機

- For **Fig. 1**, determine (a) common-mode voltage gain, (b) different mode gain, and (c) CMRR ratio, assuming  $g_{mn}=g_{mp}=g_m$  and  $r_{on}=r_{op}=r_o$  (15%)
- Fig. 2** shows the high-frequency model of a common-source amplifier.
  - Derive dc gain  $A_M=V_o/V_i$  of this circuit shown in **Fig. 2(a)**. (5%)
  - Apply Miller's theorem to  $C_{gd}$ , find  $C_{gd1}$  and  $C_{gd2}$  as shown in **Fig. 2(b)**. (10%)
  - Calculate its 3-dB high-frequency of  $f_H$ . (5%)
- Compute the closed-loop gain ( $A_V=V_{out}/V_{in}$ ) of the amplifier shown in **Fig. 3**.
  - Assuming the open-loop amplifier gain  $A_0$  is 20,  $R_1=1k\Omega$ ,  $R_2=100k\Omega$ . (5%)
  - Assuming the open-loop amplifier gain  $A_0$  is infinite,  $R_1=1k\Omega$ ,  $R_2=100k\Omega$ . (5%)
- Derive dc gain of the circuit shown in **Fig. 4**, ignoring body effect but including channel length modulation? (5%)
- The common-source stage of **Fig. 5** must provide a voltage gain of 10V/V with a bias current of 0.5mA, assuming  $\lambda_1=\lambda_2=0.1V^{-1}$ ,  $|V_{tp}|=|V_{tn}|=0.4V$ ,  $\mu_n C_{ox}=200\mu A/V^2$ , and  $\mu_p C_{ox}=100\mu A/V^2$ .
  - Compute the required value of  $(W/L)_1$ . (5%)
  - If  $(W/L)_2=10$  and  $V_{DD}=1.8V$ , calculate the required value of  $V_b$ . (5%)
- Fig. 6** shows the Common-emitter (CE) stage amplifier without considering the Early effect of  $Q_1$ .
  - Draw the small-signal model. (5%)
  - Find voltage gain of ( $A_V=V_{out}/V_{in}$ ) and input impedance ( $R_{in}$ ). (10%)
  - Explain the reasons to have capacitor  $C_1$ . (5%)
- The open-loop amplifier gain  $A_0$  is infinite, compute the output voltage  $V_{out}$  of the circuit shown in **Fig. 7**. (5%)
- An amplifier with the low-frequency response of  $L(s)=\frac{s(s+10)}{(s+100)(s+14)}$ 
  - Find each location of poles ( $\omega_{p1}$ ,  $\omega_{p2}$ ) and zeros ( $\omega_{z1}$ ,  $\omega_{z2}$ ). (10%)
  - Find the 3-dB low-frequency  $\omega_L$  of the amplifier. (5%)

# 國立臺北大學 106 學年度碩士班一般入學考試試題

系（所）組別：電機工程學系甲組(晶片設計組)

科 目：電子學 B

第 2 頁 共 2 頁

☐ 可 ☒ 不可使用計算機



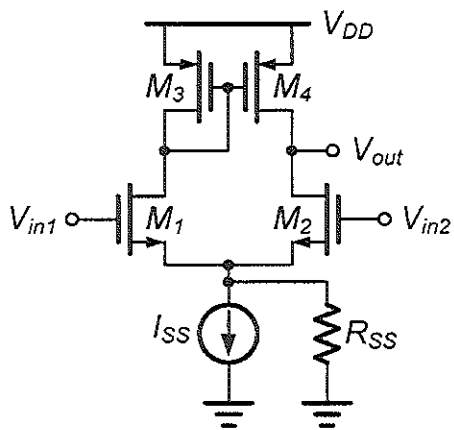


Fig. 1

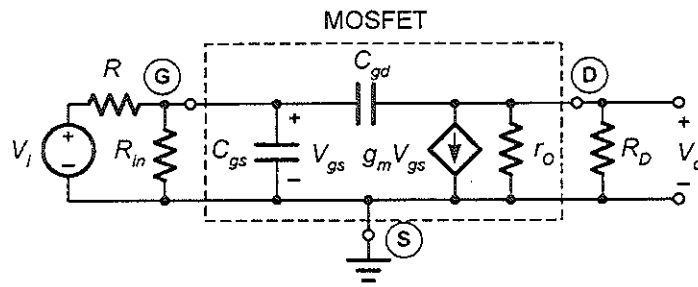

(a)

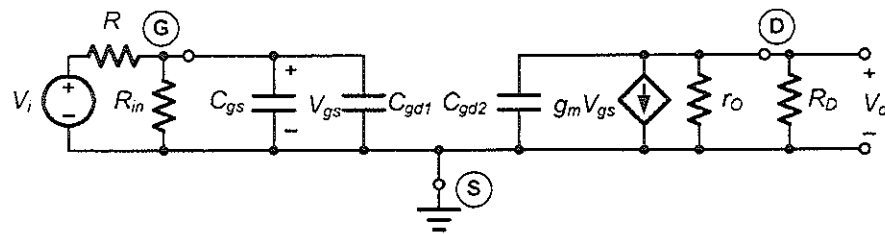

(b)

Fig. 2

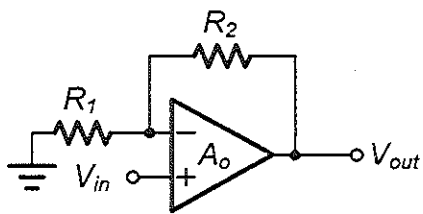


Fig. 3

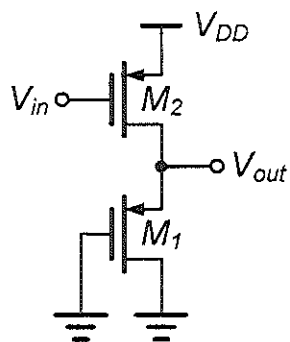


Fig. 4

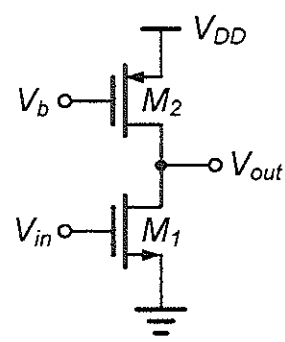


Fig. 5

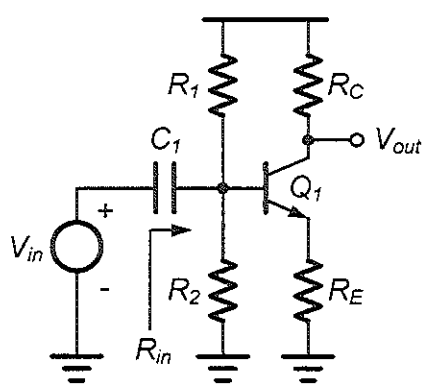


Fig. 6

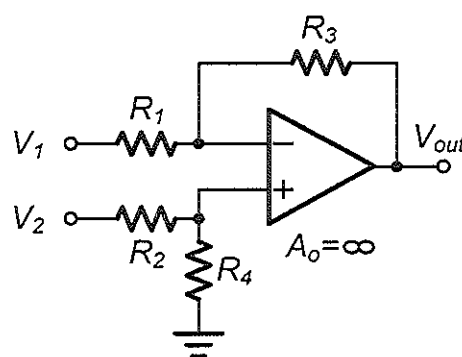


Fig. 7

試題隨卷繳交