

科目：電子學二(電路)

適用：電機系


考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。


本試題
共 3 頁
第 1 頁

編號：352

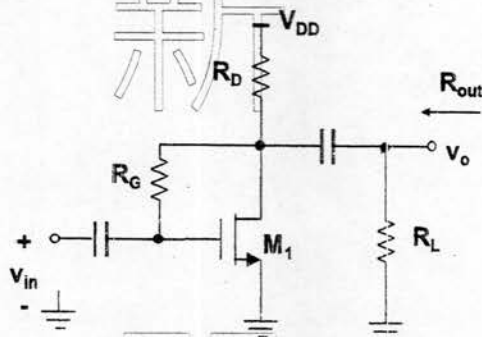
1. Assume the capacitors in the circuit shown below are sufficiently large so as to act as short circuits at the signal frequencies of interest. $V_{DD} = 1.5V$, $R_G = 1M\Omega$, $R_D = 4K\Omega$, $R_L = 4K\Omega$. M_1 has $V_{tn} = 0.5V$, $\mu_n C_{ox}(W/L)_1 = 0.4mA/V^2$, and $\lambda = 0.5V^{-1}$.
 - (a) Find the DC operating point (I_{DS} , V_{DS}). [5%]
 - (b) Draw the small-signal equivalent circuit. [5%]
 - (c) Determine the voltage gain $A_v = v_o/v_{in}$. [5%]
 - (d) Determine the output resistance R_{out} . [5%]



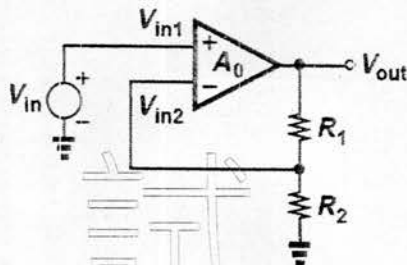2. For the non-inverting amplifier shown below,
 - (a) Derive its voltage gain, $A_v = V_{out}/V_{in}$, if $A_0 = \infty$. [5%]
 - (b) Derive its voltage gain, $A_v = V_{out}/V_{in}$, if $A_0 \neq \infty$. [5%]
 - (c) What is its gain error if $R_1/R_2 = 4$, and $A_0 = 1000$. [5%]



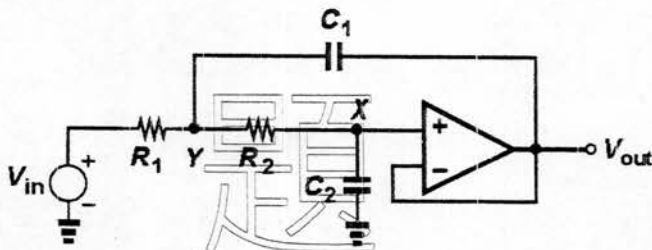3. Assume the open-loop gain of the op-amp in the circuit below is infinite.
 - (a) Derive the transfer function, $H(s) = V_{out}(s)/V_{in}(s)$. [5%]
 - (b) Assume the second pole is much smaller than the first one. What are these poles? [5%]



科目：電子學二(電路)

適用：電機系

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。


本 試 題
共 3 頁
第 2 頁

編號：352


4. A CMOS inverter amplifier and small-signal equivalent circuit model of NMOS are shown below. Assume M_1 and M_2 have been properly biased at saturation region.

(a) Draw the small-signal equivalent circuit for the inverter amplifier. [5%]

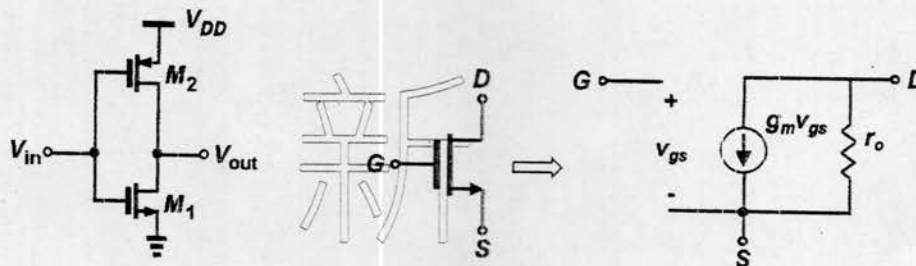(b) Derive the voltage gain, $A_v = V_{out}/V_{in}$. [5%]



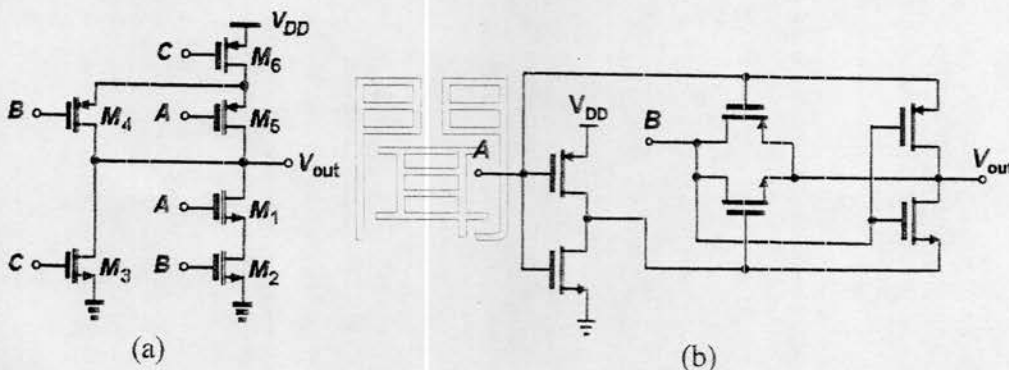
5. Assume all MOSs in the following two circuits are ideal switches. Determine their logic functions. [10%]



6. A current mirror application is shown below, where (W/L) is the ratio of width to length of MOS's. The drain-source voltage of MOS, $|V_{DS}|$, must be larger than 0.2V for good mirroring in the application.

(a) Determine the voltage values of V_1 and V_2 . [5%]

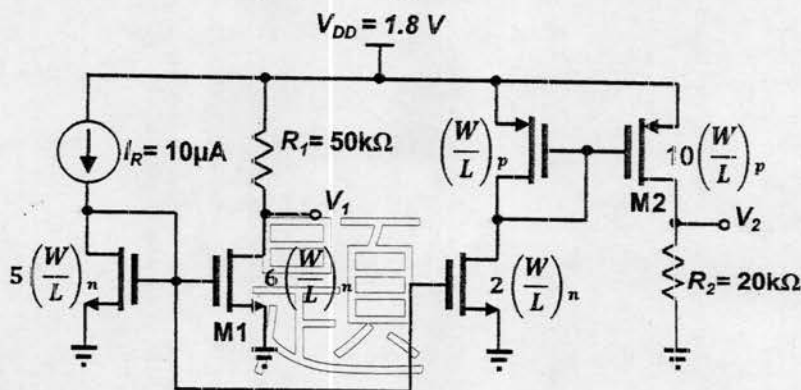(b) Find the maximum I_R that keeps both M1 and M2 saturation for good mirroring. [5%]



科目：電子學二(電路)

適用：電機系



考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。


本 試 題
共 3 頁
第 3 頁

編號：352

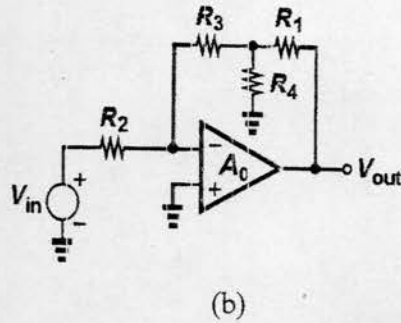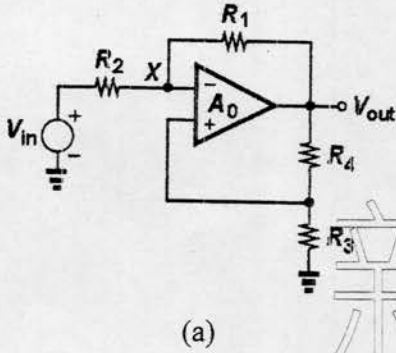7. Determine the closed-loop gain of the following two circuits if $A_0 = \infty$. [10%]




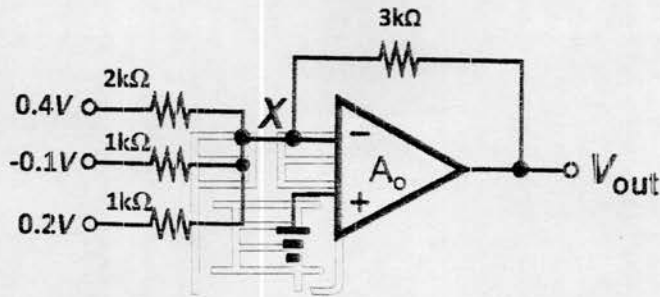8. Find V_{out} for the circuit shown below if $A_0 = \infty$. [5%]



9. (a) Determine the input impedance, Z_{in} , for the circuit shown below. Assume $\lambda = 0$ [5%]

(b) At what condition $|Z_{in}|$ behaves as an inductance? [5%]

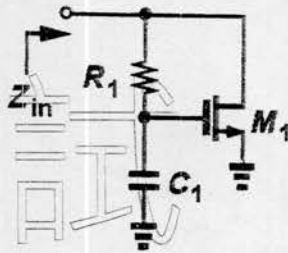

題