

# 元智大學 100 學年度研究所 碩士班 招生試題卷

系(所)別： 通訊工程學系碩  
士班


組別： 微波組

科目： 電子學


用紙第 / 頁共 > 頁

● 不可使用電子計算機

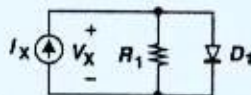1. Sketch  $V_x$  as a function of  $I_x$  for the following circuit. Assume a constant-voltage model. ( $D_{on} = 0.8 V$ ) ( $I_S = 8 \times 10^{-16} A$ ,  $V_T = 26 mV$ ,  $R_1 = 1 K\Omega$ ). 15%  
(15%)



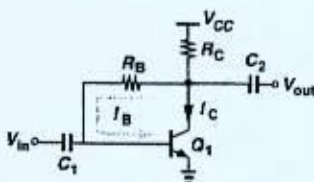
2. Design a self-biased common-emitter amplifier for voltage gain  $A_v = 36.5$ . Assume  $V_{CC} = 1.8 V$ ,  $I_C = 2 mA$ ,  $I_S = 5 \times 10^{-16} A$ ,  $\beta = 100$ ,  $V_A = \infty$  and blocking capacitors are large. (a) Determine the required value of  $R_C$  and  $R_B$ . (b) Calculate the  $V_{CE}$ ,  $V_{BE}$  and  $I_B$ . (c) Plot the small signal equivalent circuit that neglects  $R_B$ . (Hint.  $V_{BE} = V_T \ln(I_C / I_S)$  and  $V_T = 26 mV$ ) 20%  
(20%)



註 1 :  $\ln(2) = 0.693$

註 2 : 三小題配分，分別為 (a)7% ; (b)7% ; (c)6%

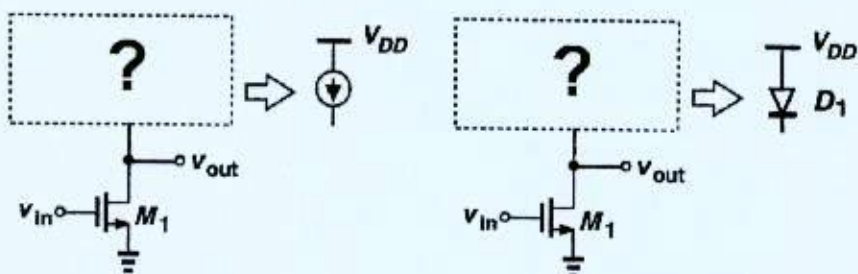3. Plot the schematic circuit of a NMOS common-source amplifier with (a) current-source load that uses PMOS device and (b) diode-connected load that uses NMOS device. These are CMOS CS amplifiers and explain the advantages of these circuits. 15% 註：(a)8% ; (b)7% .  
(15%)



# 元智大學 100 學年度研究所 碩士班 招生試題卷

系(所)別： 通訊工程學系碩士班

組別： 微波組

科目： 電子學

用紙第 2 頁共 2 頁

● 不可使用電子計算機

4. The CMOS operational amplifier shown in Fig. 1 has the following device geometries (in  $\mu\text{m}$ ). (20%)

Transistor	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	$Q_8$
$W/L$	20/0.8	20/0.8	5/0.8	5/0.8	40/0.8	10/0.8	40/0.8	40/0.8

Assume  $I_{REF} = 90\mu\text{A}$ ,  $V_m = 0.7\text{V}$ ,  $V_{tp} = -0.8\text{V}$ ,  $\mu_n C_{ox} = 160\mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 40\mu\text{A}/\text{V}^2$ ,  $V_{DD} = V_{SS} = 2.5\text{V}$ ,  $|V_A| = 10\text{V}$  for all devices. Find  $I_D$ ,  $|V_{OV}|$ ,  $g_m$  and  $r_o$  for all devices (12%). Also find the open-loop voltage gain in dB scale (8%).

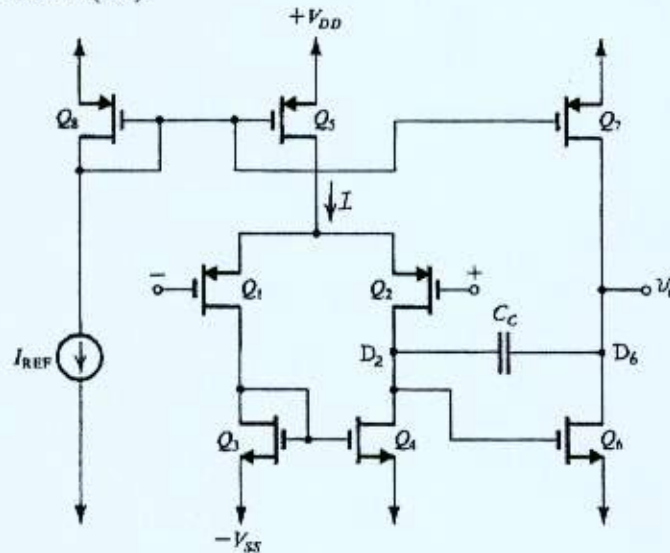


Fig. 1

5. Sketch Bode plots for the magnitude and phase of the transfer function (10%)

$$T(s) = \frac{10^2(1+s/10^5)}{(1+s/10^3)(1+s/10^4)}$$

Determine the approximated values for magnitude and phase at  $\omega = 10^6$  rad/s. (10%)

6. A shunt-shunt feedback amplifier is shown in Fig. 2, where the parameters are given as follows:  $R_s = 1\text{K}$ ,  $R_{id} = 10\text{K}$ ,  $R_{os} = 10\Omega$ ,  $A_v = -10000$ ,  $R_f = 10\text{K}$ , and  $R_L = 10\text{K}$ . (a) Find the basic amplifier gain  $A$  and the feedback factor  $\beta$ . (10%) (b) Find the feedback gain  $A_f$  and the voltage gain  $V_o/V_s$ . (10%)

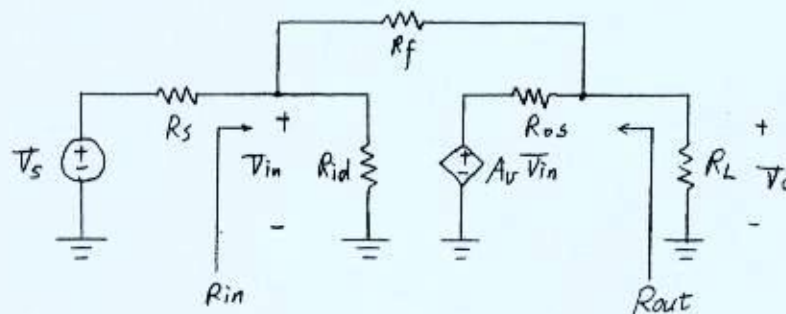


Fig. 2