

科目	數位電路(含邏輯設計)	適用系所組	電子工程學系電路與系統	時間	100分鐘
----	-------------	-------	-------------	----	-------

※請務必在答案卷作答區內作答。 共 3 頁第 1 頁

The “ $V_{OUT}$  vs.  $V_{IN}$  VTC curve” analysis is very important for the discussion of the static performance of a digital circuit. Let us make a test of this fundamental skill by means of the following two basic inverter-modules of both the BJT and the CMOS technologies.

- 1、The current gain of the transistor in Fig.1 is  $\beta = 100$ ,  $V_{BE(ACT)} = 0.7$  V,  $V_{BE(SAT)} = 0.8$  V, and  $V_{CE(SAT)} = 0.2$  V. Plot the  $V_{OUT}$  vs.  $V_{IN}$  VTC curve of this circuit. Note : You have to indicate the breakpoints and to annotate the slopes of the curve. (10 pt.s)


 


Fig. 1

 - 2、A CMOS inverter shown in Fig.2(A) with NMOS-FET  $Q_N$  parameters ( $K_N$ ,  $(W/L)_N$ , and  $V_{TN}$ ) and PMOS-FET  $Q_P$  parameters ( $K_P$ ,  $(W/L)_P$ , and  $V_{TP}$ ) is a basic structure for the CMOS digital circuit. Neglecting the effect of the channel-length modulation of both MOSFETs ( $Q_N$  and  $Q_P$ ), the  $V_{OUT}$  vs.  $V_{IN}$  VTC curve of this inverter is shown in Fig.2(B). Please answer the following questions.



$Q_N$  : ( $K_N$ ,  $(W/L)_N$ , and  $V_{TN}$ )  
 $Q_P$  : ( $K_P$ ,  $(W/L)_P$ , and  $V_{TP}$ )

Fig. 2(A)

 


Fig. 2(B)

- (1) Indicate the operation regions of both MOSFET using annotations ( OFF , SAT, and  $\Omega$  regions) within each field labeled by the ( I , II , III, IV, V) characters. (5 pt.s)

	I	II	III	IV	V
$Q_N$					
$Q_P$					

- (2) Analyze and express the breakpoints  $B(V_{IB}, V_{OB})$ ,  $C(V_{IC}, V_{OC})$  of the VTC curve using the parameters of  $Q_N$  and  $Q_P$ . (10 pt.s)
- (3) The noise margins  $NM_H$  and  $NM_L$  are defined by  $NM_H \equiv V_{OH} - V_{IH}$ , and  $NM_L \equiv V_{IL} - V_{OL}$ . As we know that the  $V_{OH} = V_{DD}$  and  $V_{OL} = 0$  V .Describe briefly (don't need to calculate) how to analyze the  $V_{IL}$ , and  $V_{IH}$  of this CMOS inverter. (5 pt.s)
- (4) What is the meaning of “a symmetric-design”, and explain how to deal with it. (5 pt.s)
- (5) Changing the relative ratio ( $K_N / K_P$ ) of the aspect-ratio of the MOSFETs  $Q_N$  and  $Q_P$ , what will be happened on the VTC curve, and explain the reasons why. (5 pt.s)
- (6) Using this inverter circuit, explain “the dynamic power dissipation ;  $P_{D(dynamic)}$ ” and “the short-circuit current;  $I_{SC}$ ” of a CMOS digital circuit. (5 pt.s)
- (7) For a correct inverter-operation , what is the necessary condition of the supply voltage  $V_{DD}$ . How comes ? (5 pt.s)

3. 5% Please minimize the following expression:

$$\overline{BCD} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}} + \overline{ABC\overline{D}}$$


4. 5% Please design and make the logic circuit as simple as possible of  $Y(A, B, C, D) = \Sigma m(7, 9, 10, 11, 12, 13, 14, 15)$ .

5. 5% Please design a logic gate circuit can implement the function of a 4-1 Multiplexer.


6. 5% Please design a logic gate circuit can implement the function of a 4-2 Encoder.

7. 10% Please draw the output waveforms for the follows logic device

(1) D-type Flip-Flop

 

(2) D-type Latch

 

8. 10% Please use the D-FF to design a **Synchronous counter** with the counting sequence of 0->1->3->5->7->0.

9. 10% Please use the JK-FF to design a **Asynchronous counter** with the counting sequence of 0->7->6->5->4->3->2->1->0