

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (10%) Design one CCM Buck converter with ideal components for the following specifications and list the parameters of the employed inductor and capacitor.
 - (1) Input DC voltage: 20V,
 - (2) Output DC voltage: 10V
 - (3) Output power: 10W
 - (4) Switching frequency: 100kHz
 - (5) Inductor current ripple: 1%
 - (6) Output voltage ripple ratio: 1%
2. (10%) Design one CCM Flyback converter with ideal components for the following specifications and list the parameters of the employed transformer and capacitor.
 - (1) Input DC voltage: 200V,
 - (2) Output DC voltage: 10V
 - (3) Output power: 10W
 - (4) Switching frequency: 100kHz
 - (5) Inductor current ripple: 1%
 - (6) Output voltage ripple ratio: 1%
3. (10%) Design and plot the P-I compensator using one ideal operational amplifier, one capacitor, and two resistors for the zero at $\omega=10$ rad/s and the 10dB gain at $\omega=1$ rad/s.
4. (10%) Plot the semiconductor structure and the equivalent circuit model of the power N-MOSFET, including three parasitic capacitors and one parasitic transistor.
5. (8%) Draw the physical structure and the equivalent circuit of a transformer with two isolated windings, including one leakage inductor, one magnetizing inductor, one copper-loss resistor, one core-loss resistor, one ideal transformer, and three parasitic capacitors.
6. (a) (4%) Draw the circuit diagram of a DC shunt generator with generated armature voltage E_A , armature resistor, shunt field resistor and shunt inductor L_F .
(b) (4%) List two methods for the voltage control of a DC shunt generator.
(c) (4%) Assume the field current is very small and ignorable at open circuit, write down voltage regulation (VR) when the generator is operating at full-load armature current I_A with the parameters shown in the circuit diagram of (a).
7. (20%) A three-phase transformer rated 20MVA, 22kV/11kV has per-phase series impedance of $(0.04 + j0.08)$ per unit. The transformer is connected to a short distribution line which can be represented by a series impedance per phase of $0.5+j2 \Omega$. The line supplies a balanced three-phase load rated 10MVA, 11kV, with lagging power factor 0.8.
 - (a) (10%) Draw an equivalent circuit of the system indicating all impedances in per unit. Choose 10MVA, 11kV as the base.
 - (b) (5%) Find the line current in real unit at the 22kV side of the transformer.

- (c) (5%) With the voltage at the primary side of the transformer held constant at 22 kV, the load at the receiving end of the line is disconnected. Find the **voltage regulation** at the load.
8. (20%) **Continue on problem 7** for using the same common base. Assume a 20MVA, 22kV synchronous generator has subtransient reactance of 20% is connected to the primary side of the transformer. The load side is connected with a 10MVA, 11kV synchronous motor with a 20% subtransient reactance. The motor is drawing 8MVA at a leading power factor of 0.8 when a symmetrical three phase fault occurs at the secondary side of the transformer. Find the **subtransient currents in per unit** from the generator, the motor, and at the fault point.