

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (20%) Fig. 1 shows the circuit of the analog-to-digital converter (ADC) in a stepper-type digital voltmeter, where the frequency of clock pulses is 1 MHz, the resolution of the digital-to-analog converter (DAC) is 10-bit, and the input voltage range of  $E_{in}$  is 0-5V. (a) Please calculate the fastest sampling rate when using this ADC. (10%) (b) For  $E_{in}=0$ , the output digital code is 0000000000 by using this ADC. Please calculate the corresponding value of  $E_{in}$  when the output digital code is 0100100100. (10%)

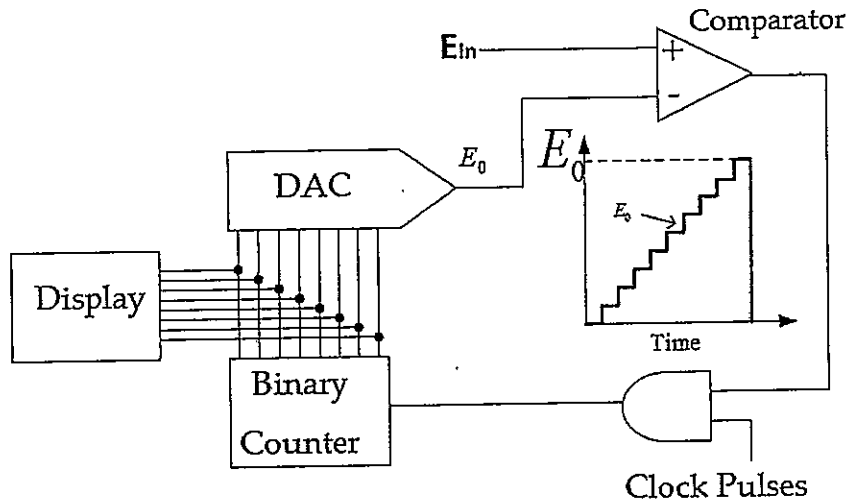


Fig. 1

2. (12%) In a decimal counting unit (DCU), the rolling effect may happen if the circuit is not appropriately designed. Please explain what the rolling effect is, and describe how to eliminate this phenomenon.
3. (18%) As shown in Fig. 2, a Zener diode is used to regulate the output voltage ( $V_{out}$ ), where  $V_{in}$  is 8V,  $R$  is  $50\Omega$ , and the breakdown voltage  $V_{Z0}$  and dynamic impedance  $r_z$  (i.e., the equivalent resistance in the breakdown region) of the Zener diode is 5 V and  $2\Omega$ , respectively. The desired output voltage ( $V_{O\_goal}$ ) of this circuit is 5V. (a) Please calculate the actual value of  $V_{out}$  when the equivalent load resistance ( $R_L$ ) is  $100\Omega$ . (8%) (b) Please recalculate the actual value of  $V_{out}$  when  $R_L$  is  $1\text{ k}\Omega$ . (4%) (c) According to the results in (a) and (b), please calculate the load regulation of this circuit. (6%)

$$[\text{Load regulation} = \frac{\Delta V_{out}}{V_{O\_goal}} \times \frac{1}{\Delta I_L} \times 100\%, \text{ Unit: \% / A}]$$

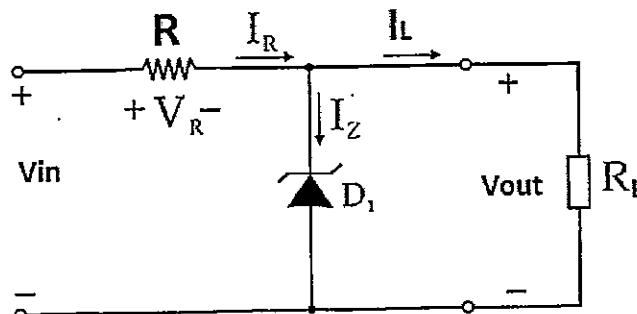


Fig. 2

4. (10%) What value of a multiplier resistor will make a 0-to-100  $\mu\text{A}$  meter with an internal resistance of 1.5  $\text{k}\Omega$  read (a) 0 to 5V? (5%) (b) 0 to 20V? (5%)
5. (12%) Given  $A = 6 \pm 0.2$ ,  $B = 3 \pm 0.3$ ,  $C = 1 \pm 10\%$ , and  $D = 3 \pm 5\%$ . Please estimate the value of  $A*B / (C+D)$  with absolute errors in expression.
6. (16%) Given the meter used is accurate to  $\pm 2\%$ . (a) **Prove** that the accuracies (i.e., errors of measured resistance) of a series-type ohmmeter (refer to the ohmmeter in Fig. 3) at  $x$  full-scale deflection (FSD) and  $(1-x)$  FSD are exactly the same ( $x$  ranges from  $0\% \sim 100\%$ ). (Hint: you need to express the measured  $R_x$  error in function of  $x$ ). (8%) (b) Determine the errors of unknown resistance  $R_x$  at 80% FSD. (8%)

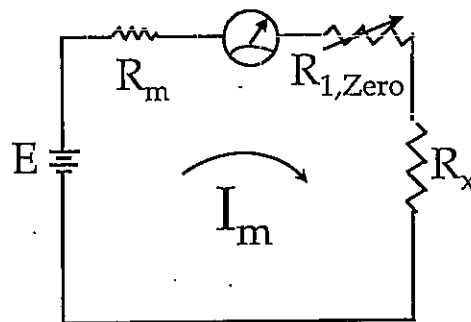


Fig. 3

7. (12%) Please refer to Fig. 4. Assume transmission line  $Z_0 = 50 \Omega$ ; discontinuity occurs and is measured at  $t_0=0$ ;  $E_i = 2 \text{ V}$ . For the circuit terminated with a series R-L ( $R=25 \Omega$ ;  $L=300 \text{ mH}$ ) circuit, (a) draw the response of Time-Domain Reflectometer (TDR) measurement results. (4%) (b) Calculate the reflection coefficient at time  $t_0=0^+$ . (4%) (c) Please evaluate the time (w.r.t.  $t_0$ ) when the total received voltage ( $E_i+E_r$ ) is 2.5 V. (4%)

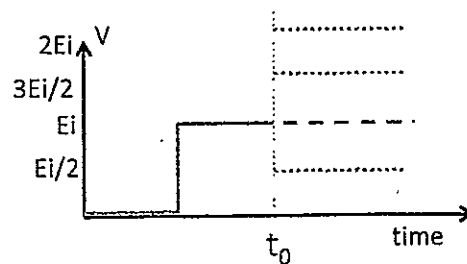


Fig. 4