

國立宜蘭大學

107 學年度研究所碩士班考試入學

電子學 試題

(範圍相當於 Sedra/Smith 微電子學前七章)

(電子工程學系碩士班)

准考證號碼：

《作答注意事項》

- 1.請先檢查准考證號碼、座位號碼及答案卷號碼是否相符。
- 2.考試時間：100 分鐘。
- 3.本試卷共有 6 題，第 1 題為 10 個單選題，每題 4 分，小計 40 分，第 2~6 題為非選擇題，小計 60 分，合計 100 分。
- 4.請將答案寫在答案卷上。
- 5.考試中禁止使用手機或其他通信設備。
- 6.考試後，請將試題卷及答案卷一併繳交。
- 7.本試卷採雙面影印，請勿漏答。
- 8.本考科可使用非程式型（不具備儲存程式功能）之電子計算機。

1. Choose the correct answer for the following questions. (40%)

- (1) Consider the amplifier shown in Fig. 1.(1) with ideal op amps and $R_1 = 1 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, $R_L = 1 \text{ k}\Omega$. If $v_I = 1 \text{ V}$. Then current $i_2 = ?$ (A) 0.5 mA (B) 1 mA (C) 1.5 mA (D) 2 mA
- (2) Continuing the above problem, current $i_L = ?$
 (A) 1 mA (B) 2 mA (C) 3 mA (D) 4 mA
- (3) If the circuit shown in Fig. 1.(3) is an ideal diode circuit, which is the correct transfer characteristic? In the figures, m is the slope.

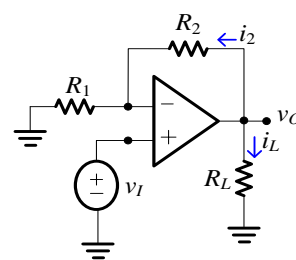


Fig. 1.(1)


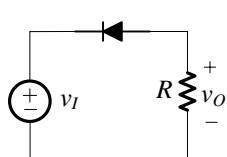


Fig. 1.(3)

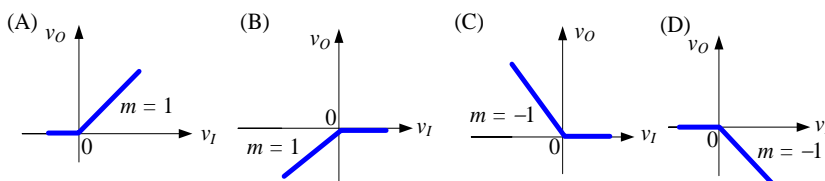

- (4) For BJT, the h_{FE} is defined as (A) $\frac{I_C}{I_B}$ (B) $\frac{\Delta I_C}{\Delta I_B}$ (C) $\frac{I_C}{I_E}$ (D) $\frac{\Delta I_C}{\Delta I_E}$
- (5) The BJT's finite output resistance in active region, r_o , results from
 (A) Early effect (B) Avalanche effect (C) Temperature effect (D) Zener Effect.
- (6) The symbol shown in Fig. 1.(6) stands for
 (A) enhancement-type NMOS (B) enhancement-type PMOS
 (C) depletion-type NMOS (D) depletion-type PMOS.
- (7) An enhancement-type NMOS FET, with $V_t = 1 \text{ V}$ and $k_n' = 25 \mu\text{A}/\text{V}^2$, has its source terminal voltage = 0.5 V and a 2.5 V dc applied to the gate. What region does the device operate for $V_D = 1 \text{ V}$?
 (A) Saturation (B) Cutoff (C) Triode (D) Active region.
- (8) If a depletion-type NMOS FET is in saturation region, and its current is

$$i_D = \frac{1}{2} k_n (v_{GS} - V_t)^2 \cdot (1 + \lambda v_{DS}). \text{ Which is correct?}$$

- (A) $V_t > 0$ (B) k_n is in proportion to L/W
 (C) λ is related to the Miller effect (D) $v_{GS} > V_t$
- (9) In Fig. 1.(9), if $R_s = r_o = 10 \text{ k}\Omega$, $g_m = 2 \text{ mA}/\text{V}$, then $R_{out} = ?$
 (A) 2 k Ω (B) 20 k Ω (C) 200 k Ω (D) 400 k Ω
- (10) Which is correct about CB (Common Base) amplifier?
 (A) large input resistance (B) bad high frequency response
 (C) high voltage gain (D) used as voltage buffer

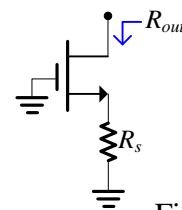


Fig. 1.(9)

2. If the circuit shown in Fig.2 has $R_a = 2 \text{ k}\Omega$, $R_b = 50 \text{ k}\Omega$, and $C = 2 \text{ nF}$.

(a) What is the circuit?
 (b) Find its transfer function $V_o(s)/V_i(s)$.

(10%)

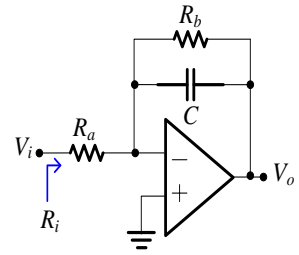


Fig.2

3. Consider a peak rectifier, shown in Fig.3, fed by a 60 Hz sinusoid v_I having a rms value $V_{\text{rms}} = 24 \text{ V}$. Let the load resistance $R = 10 \text{ k}\Omega$.

(a) Find the capacitance C that will result in a peak-to-peak ripple of 2 V.

(b) Find the peak value of the diode current $i_{D,\text{max}}$.

(10%)

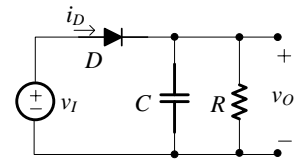


Fig.3

4. For the circuit shown in Fig.4 has that $V_{CC} = +9 \text{ V}$, $R_B = 100 \text{ k}\Omega$. If the β of transistor is specified the range of 50 to 200,

(a) find the maximum value of R_C so that the circuit is in the active mode. (b) Continuing the above problem, what is the range of collector voltage V_C ?

(10%)

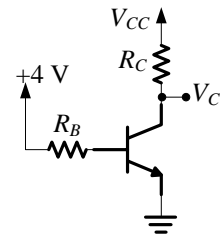


Fig.4

5. For the circuit shown in Fig.5, let $V_{DD} = 5 \text{ V}$. The FET operates in saturation with $I_D = 0.25 \text{ mA}$, and has $V_{tp} = -1 \text{ V}$, $\mu_p C_{ox}(W/L) = 1 \text{ mA/V}^2$. Find

(a) $|V_{GS}|$.
 (b) What is the largest value that R_D can have while maintaining saturation region operation?

(10%)

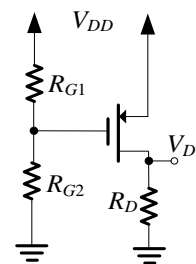


Fig.5

6. (a) Design the CE amplifier, shown in Fig.6, to obtain DC current $I_E = 0.5 \text{ mA}$ for $V_{CC} = +10 \text{ V}$, $V_C = 6 \text{ V}$, $V_B = 3 \text{ V}$, $\beta = 100$, and current through R_{B2} of $50 \mu\text{A}$.

(b) What is the function of C_1 and C_2 ?
 (c) Find input resistance R_{in} .
 (d) If $R_L = 20 \text{ k}\Omega$, find $A_v = v_o/v_i$.

(20%)

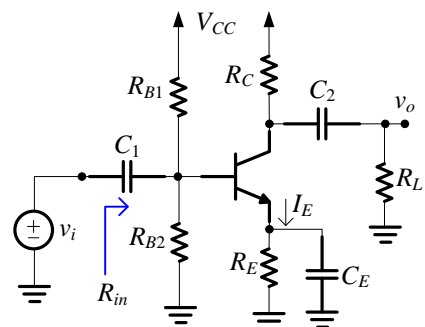


Fig.6