

元智大學 107 學年度 碩士班 招生試題卷

系(所)別：電機工程學系碩士班 組別：甲組

科目：電子學

用紙第 1 頁共 2 頁

● 不可使用電子計算機

Problem 1: (18%) For the bridge rectifier circuit shown in Fig. 1, V_{in} is a 100-Hz 5-V peak sine wave with zero offset, $D_1 \sim D_4$ are diodes with a constant voltage drop $V_D = 0.7$ V. Use the constant-voltage-drop diode model to find the following:

- Draw waveforms V_{in} and V_{out} versus time with their maximum amplitudes. (6%)
- Remove D_1 , make terminals a and b open circuit, and please draw waveforms V_{in} and V_{out} versus time with their maximum amplitudes. (6%)
- Make terminals a and b short circuit, and please draw waveforms V_{in} and V_{out} versus time with their maximum amplitudes. (6%)

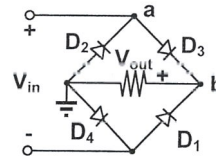


Fig. 1

Problem 2: (15%) For a CMOS inverter with matched MOSFETs having $V_{th} = 0.7$ V, if $V_{DD} = 3.3$ V, find (a) input low level, V_{IL} , (b) input high level, V_{IH} , and (c) noise margins.

Problem 3: (17%) (a) Sketch a static CMOS logic circuit that realizes the function $\overline{A(B + CD)}$. (9%) (b) Provide the W/L ratios for nMOS and pMOS transistors. Assume that for the basic CMOS inverter $(W/L)_n = 2$ and $(W/L)_p = 5$. (8%)

元智大學 107 學年度 碩士班 招生試題卷

系(所)別：電機工程學系碩 士班 組別：甲組

科目：電子學

用紙第 2 頁共 2 頁

● 不可使用電子計算機

Problem 4: (25%) Consider a typical Opamp with two amplification stages (A_{v1} and A_{v2}). The input and output impedance of each stage is denoted as R_{in1} , R_{out1} , R_{in2} , and R_{out2} . A compensation capacitance C_c is placed across A_{v2} .

- (a) Determine the bandwidth of the Opamp by Miller Effect. (10%)
- (b) Redo (a) without using Miller Effect. (5%)
- (c) Under what condition will the results of (a) and (b) become identical? (10%)

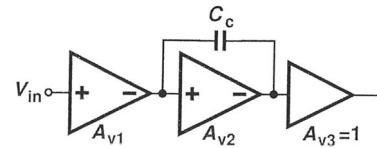


Fig. 2

Problem 5: (25%) A fully differential telescopic Opamp is shown below with the parameters: $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\lambda_n = \lambda_p = 0.2 \text{V}^{-1}$, $\gamma = 0$, $V_{THN} = |V_{THP}| = 0.7 \text{V}$, $V_{DD} = 3 \text{V}$, $I_{M9} = 1 \text{mA}$, $V_{OD9} = V_{GS9} - V_{TH9} = 0.4 \text{V}$. $M_{1,4}$: $(W/L) = 1000$, $M_{5,8}$: $(W/L) = 2000$.

- (a) Calculate the dc gain. (10%)
- (b) Determine the maximum differential output swing. (5%)
- (c) Using resistive feedback with the Opamp to construct a voltage amplifier with typical dc gain of 10dB. Draw the circuit with the calculated resistance and calculate the gain error. (10%)

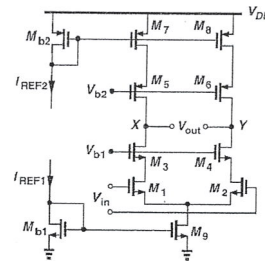


Fig. 3.