

國立中山大學 107 學年度碩士暨碩士專班招生考試試題

科目名稱：電子學【電波領域聯合】

題號：482003

※本科目依簡章規定「可以」使用計算機（廠牌、功能不拘）

共 1 頁第 1 頁

1. (30%) Figure 1 shows an amplifier made of a single MOSFET that is biased with $I_D = 0.5$ mA. Assume that all capacitors C_1 , C_2 and C_3 are large enough to act like shorted in the frequency band of interest, and the parasitic capacitances of the MOSFET Q and the series gate resistance are negligible. The transistor Q has the device parameters: $W/L = 80$, $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.7$ V, $\lambda = 0.1$. (a)(20%) Draw the ac equivalent circuit. Determine the frequency (in rad/s) at which the amplifier achieves the peak gain, and determine this maximum gain. (b) (10%) Find the bandwidth of the amplifier (in rad/s). Note: $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$ for Q in saturation.

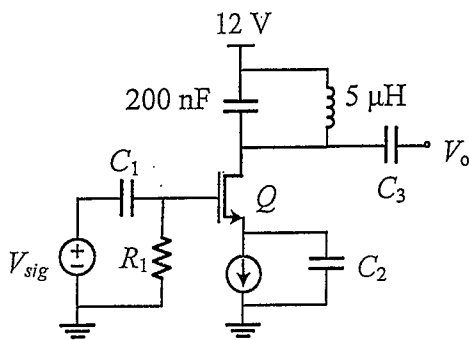


Fig. 1

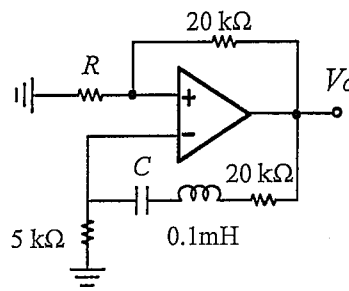


Fig. 2

2. (20%) Use the Barkhausen criterion to determine the values of R and C so that the Wien-bridge circuit in Fig. 2 oscillates at 100 kHz.
3. (30%) (a) (20%) Determine the values of R and C in Fig. 3 so that the average power dissipation on resistor R is maximized. (b) (10%) Calculate this maximum power.

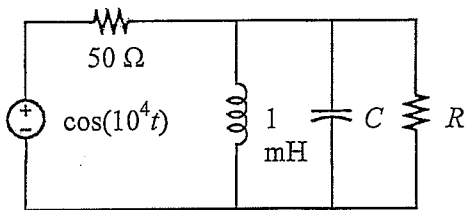


Fig. 3

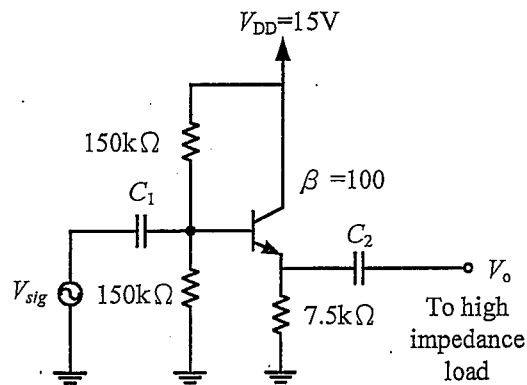


Fig. 4

4. (20%) An emitter follower in Fig. 4 is used to drive a very high impedance. C_1 forms a high-pass filter with the divider resistances and the resistance looking into the base. Choose the value of C_1 so that the resulting cutoff frequency is 1 kHz.