

國立高雄應用科技大學
100 學年度碩士班招生考試
電機工程系 (甲組)

准考證號碼 (考生必須填寫)

電路學

試題 共 3 頁，第 1 頁

- 注意：a. 本試題共 6 題，第 1~2 題每題 10 分，第 3~6 題每題 20 分，共 100 分。
 b. 作答時不必抄題。
 c. 考生作答前請詳閱答案卷之考生注意事項。

1. Calculate the power delivered by the dependent voltage source in the circuit shown in Fig.1. (10%)

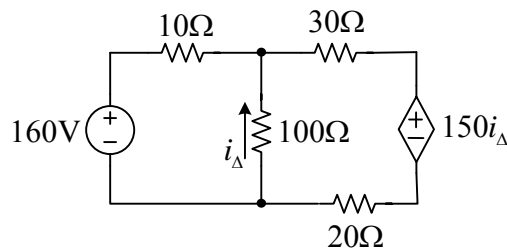


Fig.1

2. The sinusoidal voltage source in the circuit in Fig.2 is $v_g = 20 \cos(2000t - 30^\circ) \text{V}$, find the steady-state expression of v_o . (10%)

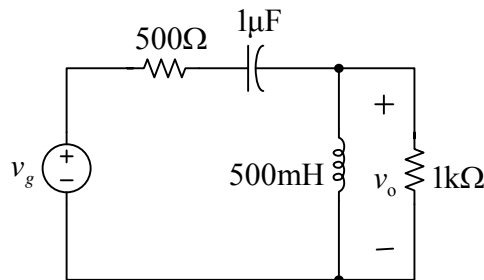


Fig.2

3. In the circuit in Fig.3, switches 1 and 2 are synchronized. When switch 1 is opened, switch 2 closes and vice versa. Switch 1 has been opened for a long time before closing at $t = 0$.
- (a) What type of damping will the circuit produce? (overdamped, underdamped, critically damped, or none of the above) (5%)
- (b) Find $i_L(t)$ for $t \geq 0$. (15%)

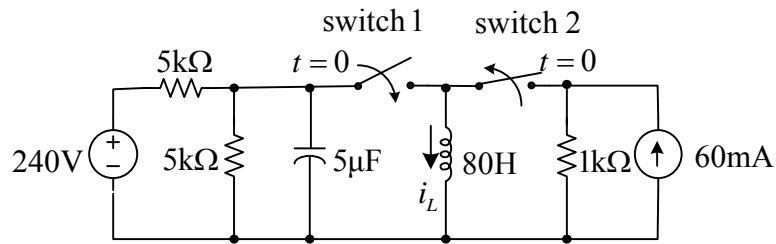


Fig.3

4. The coupling coefficient of the two coils in the circuit in Fig.4 is $k = 0.75$, and the load resistor R_L is adjustable. If $v_g = 54\sqrt{2} \cos 1000t$ V.
- (a) If the value of R_L is ∞ (open circuit), find v_o . (10%)
- (b) What value of R_L will result in the maximum average power being transferred to R_L ? (10%)

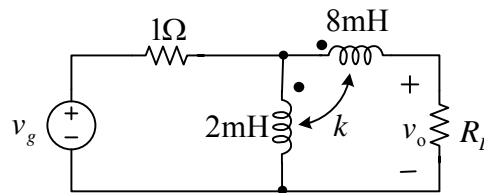


Fig. 4

5. The op amp in the circuit in Fig.5 is ideal, and there is no energy stored in the capacitors at the time the circuit is energized.
- (a) Find the transfer function of the circuit. (10%)
- (b) If $v_g = 0.5u(t)$ V, How many milliseconds elapse before the op amp saturate? (10%)

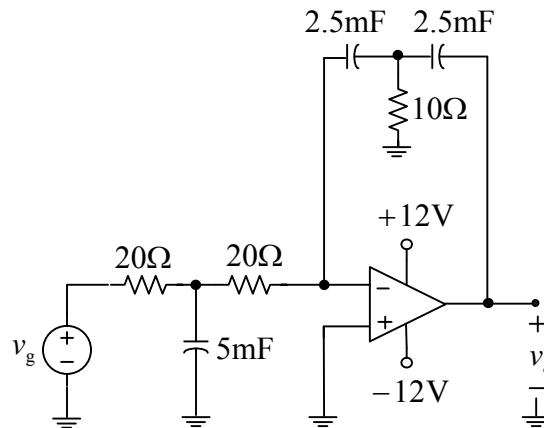


Fig.5

6. Explain the following glossaries: (20%)
- (a) susceptance
- (b) apparent power
- (c) unit impulse response
- (d) third-order harmonic
- (e) root-mean-square value