



本試題共五題，每題得分如各題中所示，共計 100 分，請依題號作答並將答案寫在答案卷上，違者不予計分。

- From the Voltage Transfer Characteristic (VTC), we can find four parameters of the VTC (V_{OH} , V_{OL} , V_{IL} , and V_{IH}). Determine the noise margins:
 - (5 分) NM_H and
 - (5 分) NM_L

- For the instrumentation amplifier of Fig. P2:

- (10 分) find the voltage v_1 and v_2 .
- (10 分) find the voltage v_3 and v_4 .
- (5 分) find the voltage v_o .

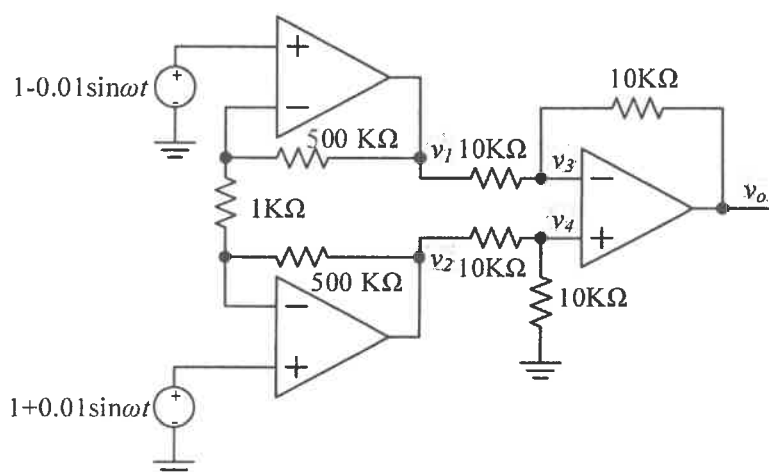


Fig. P2

- Assume the forward voltage of the diode which shown in Fig. 3(a)(b)and(c) is 0.1V with no leakage current.

- (5 分) Find the values of I_1 and V_1 in the circuits shown in Fig. P3(a).
- (5 分) Find the values of I_2 and V_2 in the circuits shown in Fig. P3(b).
- (5 分) Find the values of I_3 and V_3 in the circuits shown in Fig. P3(c).

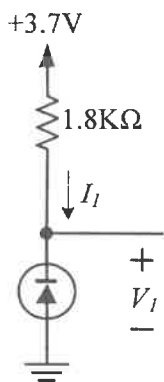


Fig. P3(a)

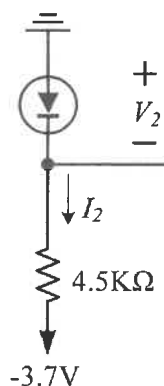


Fig. P3(b)

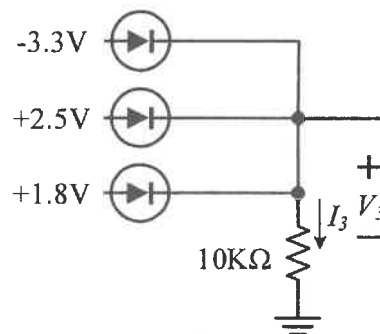


Fig. P3(c)



4. (20 分) The operational amplifiers are ideal. Please (a) calculate the voltage gains of the circuits shown in Fig. P4(a), where $R_1=10k\Omega$ and $R_2=100\Omega$. (b) Write down V_{out} in terms of $V_A, V_B, R_A, R_B,$ and $R_C,$ as shown in Fig. P4(b).

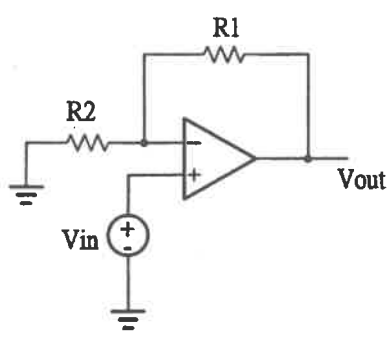


Fig. P4(a)

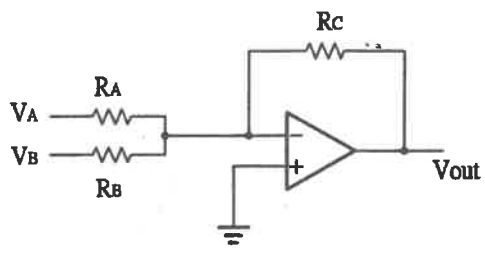


Fig. P4(b)

5. (30 分) All MOS transistors are biased in the saturation region. Neglect the body-effect of the NMOS transistors. Calculate (a) open-loop gain, (b) loop gain, and (c) closed-loop gain of the feedback amplifier shown in Fig. P5. $\lambda_N = \lambda_P = 0.1V^{-1}$. $g_{mN} = 10 \times 10^{-3} A/V$. $g_{mP} = 2.5 \times 10^{-3} A/V$. $I_{SS} = 2mA$. $R_1=100k\Omega$. $R_2=100k\Omega$.

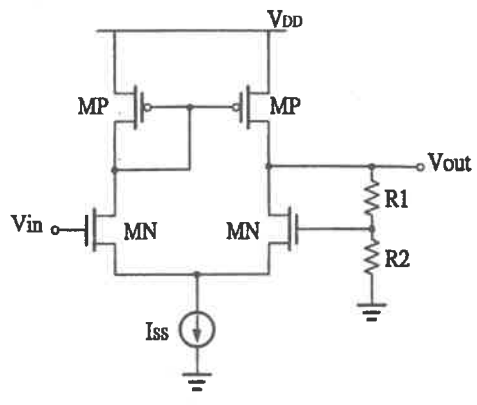


Fig. P5