

國立臺北科技大學 100 學年度碩士班招生考試

系所組別：2230 電腦與通訊研究所丙組

第二節 電子學 試題

第一頁 共一頁

注意事項：

1. 本試題共五題，配分共 100 分。
2. 請標明大題、子題編號作答，不必抄題。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。

1. Assume M_1 is in saturation with a transconductance g_{m1} as shown in Fig. 1. Please calculate
- (a) the input impedance (Z_{in}) including gate-to-source capacitance (C_{gs1}) and gate resistance (r_{g1}). (10%)
 - (b) the frequency that Z_{in} is purely inductive or capacitive. (5%)

 


Fig. 1

 


Fig. 2

2. Figure 2 shows a layout of a CMOS logic circuit.

- (a) Sketch the schematic of Fig. 2, where a, b, c, and d are the four inputs, and out is the output (10%)
- (b) What is the logic function in Fig. 2? (5%)
- (c) Why NAND gate is preferably used in CMOS logic circuits as compared with NOR gate for the consideration of package density? (10%)

3. In the amplifier circuit as shown in Fig. 3, JFET parameters are: $I_{DSS}=10\text{mA}$, $V_p=-1\text{V}$, $\lambda=0$, $C_{gs}=C_{gd}=0.5\text{pF}$. Capacitors C_1 and C_2 are very large. The drain voltage should be biased at $V_D=5.1\text{V}$.

- (a) Find the value of R_s . (6%)
- (b) Find the g_m value and mid-band voltage gain V_o/V_i . (6%)
- (c) Find the Miller's capacitance C_M . (4%)
- (d) Find the upper 3-dB frequency f_H . (4%)

 


Fig. 3

 


Fig. 4

4. For the circuit shown in Fig.4, let $V_{BE(on)}=0.7\text{V}$, $\beta=100$, and $V_{CE(sat)}=0.2\text{V}$.

- (a) Determine the Q -point of the circuit. (10%)
- (b) Plot the load line and indicate the Q -point on the collector current-voltage characteristic plot. Indicate important data and the associated units on the plot. (10%)

5. In the Fig. 5, the op-amp circuit has three internal critical frequencies as follow: 1.2KHz, 50KHz, and 250KHz. If the midrange open-loop gain is 100dB, is the amplifier configuration stable, marginally stable, or unstable? (20%)

 


Fig. 5