

科目：電子學甲 適用：電機所電子組

編號：452

考生注意：  
 1. 依次序作答，只要標明題號，不必抄題。  
 2. 答案必須寫在答案卷上，否則不予計分。  
 3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題  
 共 2 頁  
 第 1 頁

1. (a) Calculate the bias current ( $I_D$ ) of  $M_1$  in Fig. 1. Assume  $\mu_n C_{ox} = 100 \mu A/V^2$  and  $V_{TH} = 0.4 V$ . (10 points)

- (b) If the gate voltage of  $M_1$  increases by  $10 mV$ , what is the change in its drain voltage? (10 points)

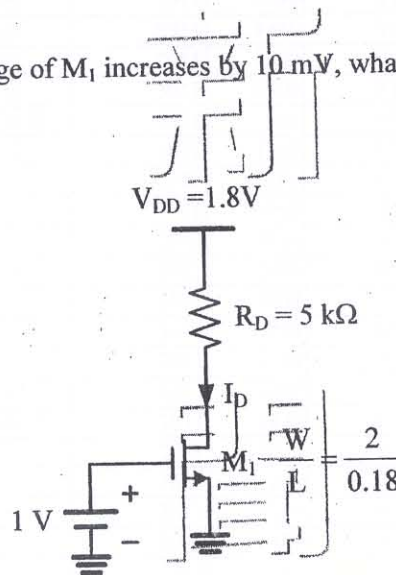


Fig. 1

2. Calculate the CMRR (common-mode rejection ratio) of the circuit shown in Fig. 2. (15 points)

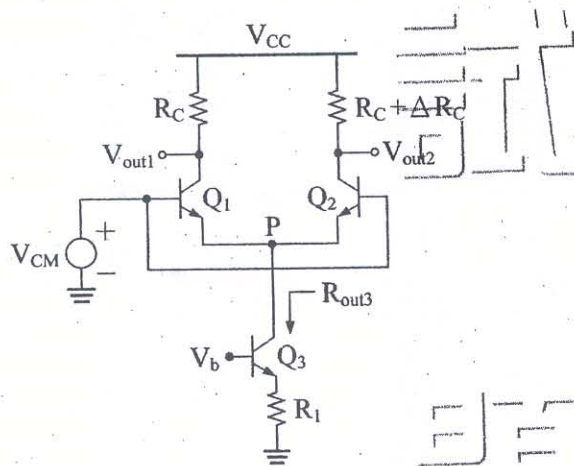


Fig. 2

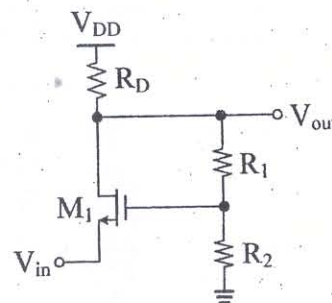


Fig. 3



3. Calculate the voltage gain, input impedance, and output impedance of the amplifier depicted in Fig. 3. Suppose  $R_1 + R_2$  is not much less than  $R_D$ . (15 points)

科目：電子學甲 適用：電機所電子組  
 編號：452

考生注意：  
 1. 依次序作答，只要標明題號，不必抄題。  
 2. 答案必須寫在答案卷上，否則不予計分。  
 3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題  
 共 2 頁  
 第 2 頁

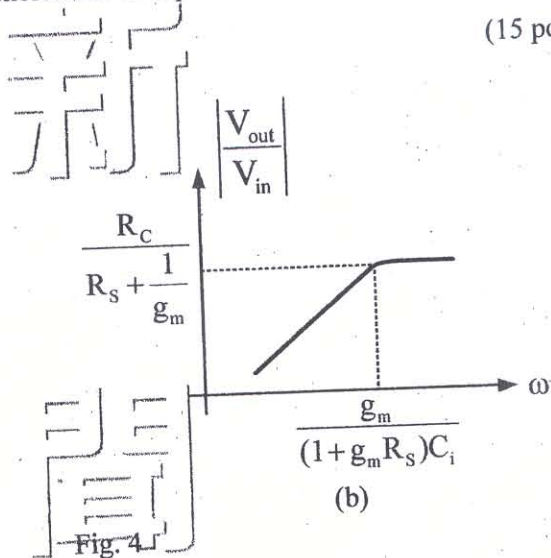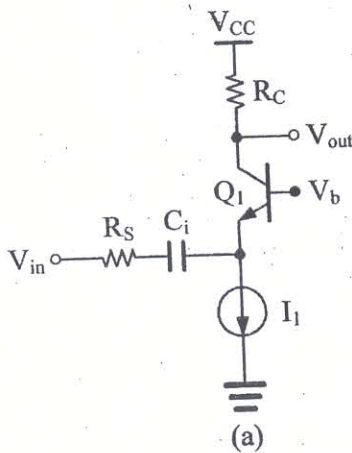4. Fig. 4(a) shows a common-base stage with input capacitor coupling. Prove its frequency response at low frequencies can be represented as that in Fig. 4(b). (15 points)



5. Estimate the poles of the circuit shown in Fig. 5. Assume  $\lambda = 0$ . (15 points)

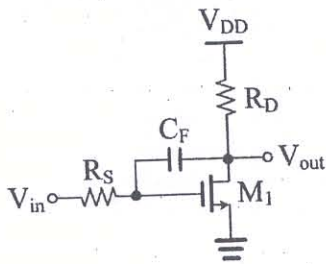


Fig. 5

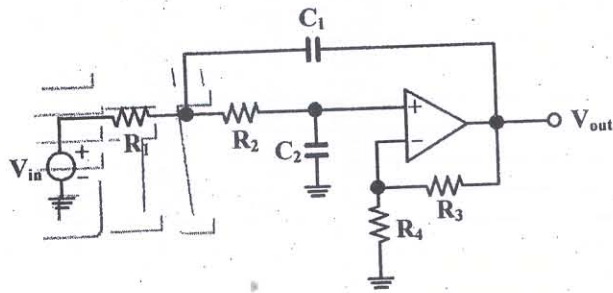


Fig. 6

6. Fig. 6 shows the Sallen and Key filter with in-band gain. Assuming an ideal op amp, determine the transfer function of the circuit. (20 points)