

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. The circuit of Fig. 1 is used to create an ac-coupled noninverting amplifier with a gain of 100 V/V using resistor  $R_2$  of 100 k $\Omega$ .

(a) What values of  $R_1$  and  $R_3$  should be used ? (4%)

(b) For break frequency due to  $C_1$  at 100 Hz, and that due to  $C_2$  at 10 Hz, what values of  $C_1$  and  $C_2$  are needed ?(8%)

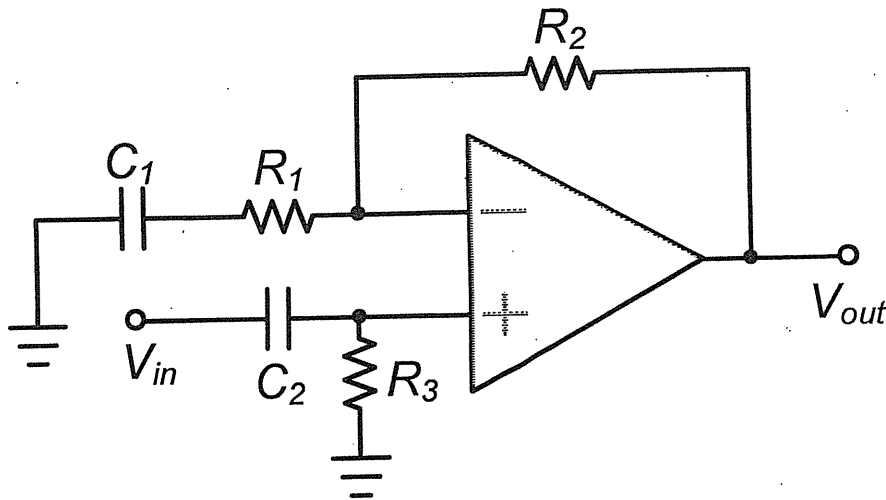


Fig. 1.

2. Consider an operational rectifier as shown in Fig. 2 with  $R=1$  k $\Omega$ . Assume that the op amp is ideal and that its output saturates at  $\pm 12$  V. The diode has a 0.7-V drop at 1-mA current. Find the voltages ( $V_A$  and  $V_O$ ) that result at the rectifier output ( $V_O$ ) and at the opamp output ( $V_A$ ) under the conditions:

(a)  $V_i=10$ mV (4%)

(b)  $V_i=1$ V (4%)

(c)  $V_i=-1$ V (4%)

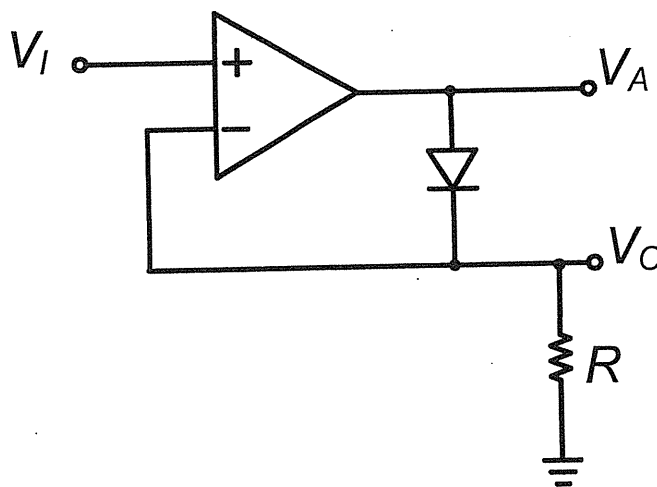


Fig. 2



5. Explanatory questions:

- (a) Draw and explain the circuit diagram of a basic Wien-bridge oscillator. (5%)
- (b) A student mistakenly configures a Sallen and Key filter as shown in Fig. 5. Explain why this is not a useful circuit. (5%)

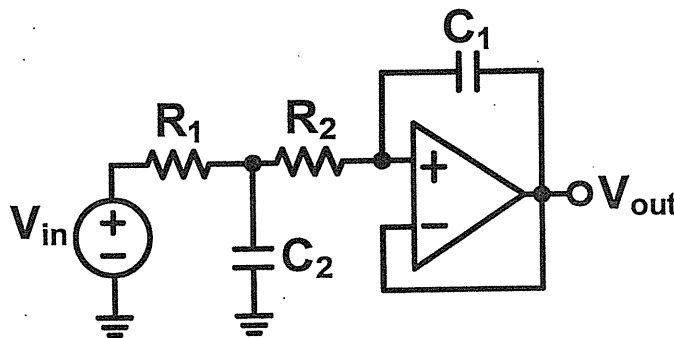


Fig. 5

6. Consider a three-pole feedback amplifier with a loop gain function given by

$$T(f) = \frac{1000}{(1 + j \frac{f}{10^4})(1 + j \frac{f}{10^6})(1 + j \frac{f}{10^8})}$$

- (a) Please draw the Bode plot of this amplifier. (5%)
  - (b) Insert an additional dominant pole (assuming all original poles do not change) such that the resulting phase margin is at least 45 degrees. (5%)
7. Consider the circuit shown in Fig. 6. Assume the saturated output voltages of op-amp are  $\pm 10V$ .
- (a) Find  $R_x$  such that the frequency of oscillation is 500 Hz when the potentiometer is connected to point A. (5%)
  - (b) Using the result of (a), determine the oscillator frequency when the potentiometer is connected to point B. (5%)

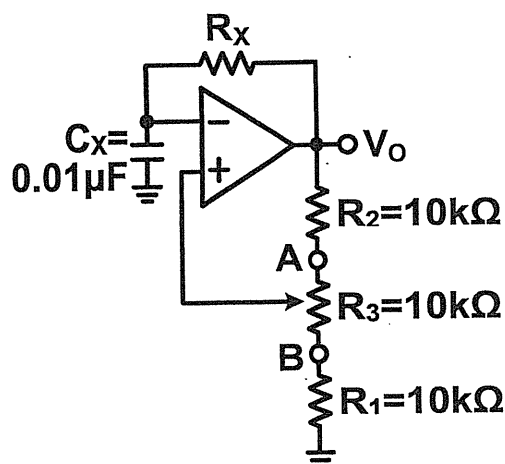


Fig. 6

