

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. Find the Thevenin equivalent of the circuit in Fig. 1 at terminals $a-b$. (10%)
2. A resistance array is connected to a load resistor R_L and a 9-V battery as shown in Fig. 2.
 - (a) Find the value of R_L such that $V_o = 1.8$ V. (15%)
 - (b) Calculate the value of R_L that will draw the maximum current. What is the maximum current? (5%)
3. In the op amp circuit of Fig. 3, let $v_i(t) = u(t)$ V, $R_1 = R_2 = 10$ k Ω , and $C_1 = C_2 = 100$ μ F.
 - (a) What are the value of $v_o(0)$ and $v_o(\infty)$, respectively? (4%)
 - (b) Determine $v_o(t)$ for $t > 0$ s. (16%)

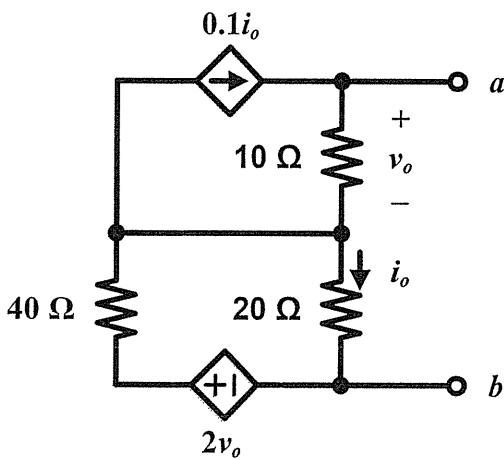


Fig. 1

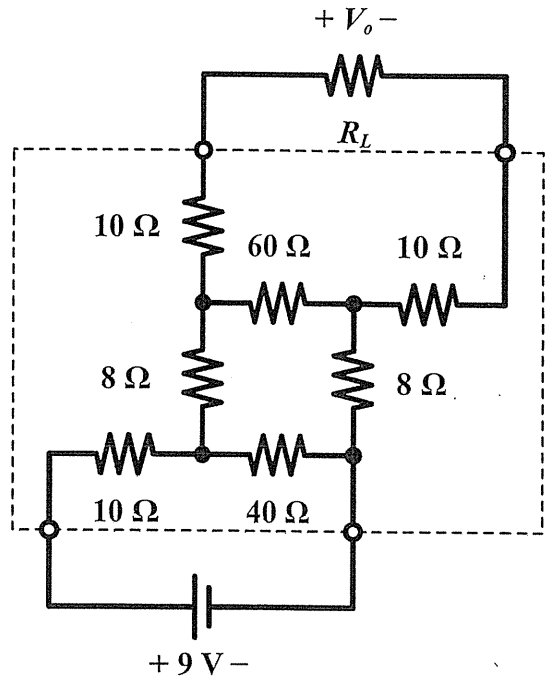


Fig. 2

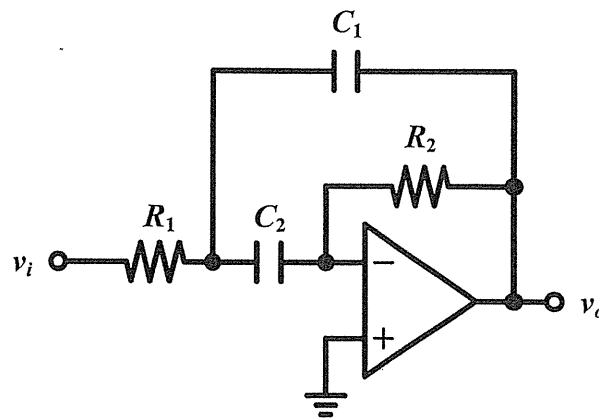


Fig. 3

4. The circuit shown in Fig. 4 contains four passive elements and an ideal transformer with turns ratio of 2:1. Please derive the admittance parameters or y parameters as a function of s . (20%)

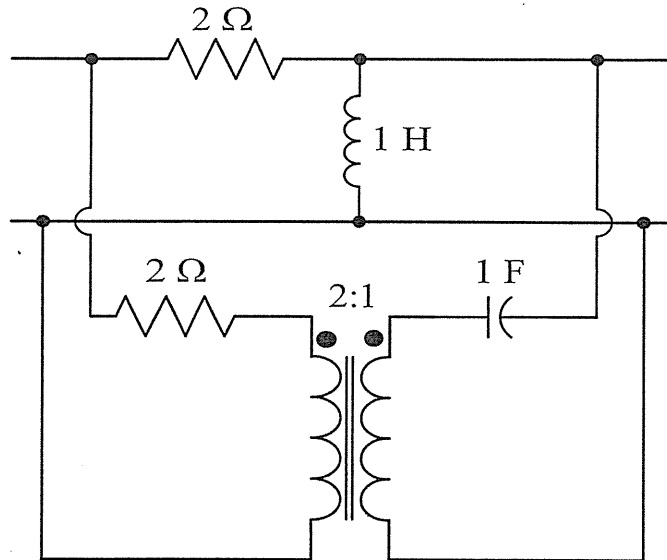


Fig. 4

5. A three-phase Y-connected induction-motor load with per-phase impedance of $80 + j60 \Omega$ is properly connected to a balanced three-phase power source of 208 V, 60 Hz, negative sequence. Two wattmeters are properly connected to measure the absorbed power of the load.
- Please find the readings of the two wattmeters (5%).
 - Please determine the line-current magnitude, total active power, and total reactive power absorbed by the induction-motor load. (15%)
6. For the circuit shown in Fig. 6, $i(t) = 20 + 16\cos(10t + 45^\circ) + 12\cos(20t - 60^\circ)$ mA.
- Please solve for the voltage $v(t)$. (5%)
 - Please calculate the average power dissipated in the resistor of 2 k Ω . (5%)

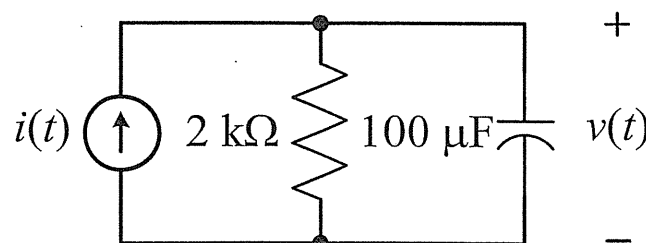


Fig. 6