

1. (20%) Consider a rectifier circuit shown in Fig. 1, where the diode is assumed to be ideal.

(a) (10%) Please plot the waveform of the load voltage  $v_L(t)$ .

(b) (10%) Suppose now that the diode  $D_1$  is broken, i.e., always open. Please plot the waveform of the load voltage  $v_L(t)$ .

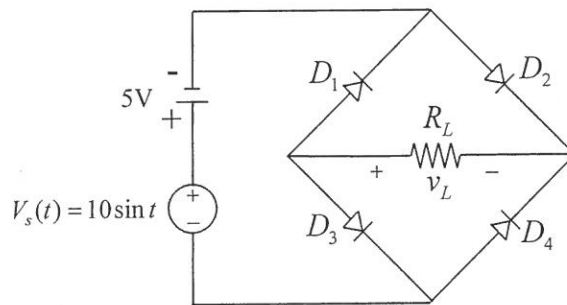


Fig. 1

2. (30%) Consider the circuit shown in Fig. 2.

(a) (10%) Please reduce the circuit (viewed from the terminals a and b) to a Thevenin equivalent circuit.

(b) (10%) Please reduce the circuit (viewed from the terminals a and b) to a Norton equivalent circuit.

(c) (10%) Suppose now we attach a  $1\ \Omega$  resistor to the terminals a and b. Please find the current passing through this resistor using (i) Thevenin equivalent circuit and (ii) Norton equivalent circuit.

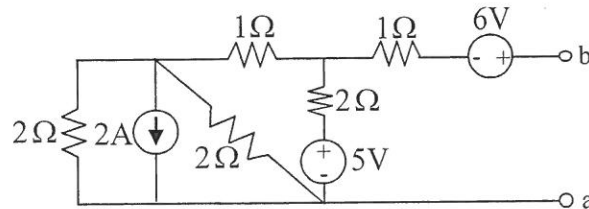


Fig. 2

3. (25%) Fig. 3 shows a RLC circuit wherein  $R = 1\Omega$ ,  $L = 1mH$ , and  $C = 1mF$ .

(a) (10%) What is the transfer function from the input voltage  $u$  to the output voltage  $y$ ?

(b) (5%) What is the governing equation of the circuit in terms of the input voltage  $u$  and the output voltage  $y$ ?

(c) (5%) Sketch the Bode plot of the transfer function found above in (a).

(b) (5%) Sketch the step response of the transfer function found above in (a). Estimate its steady-state error, rising time, overshoot, and settling time.

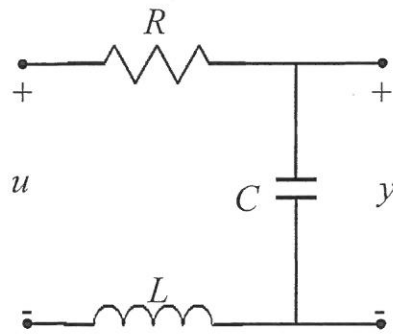


Fig. 3

4. (25%) Fig. 4 shows a schematic circuit comprising Operational Amplifiers, which will function as a feedback compensator. Therein,  $C = 1\mu F$ ,  $R_1 = 100k\Omega$ ,  $R_2 = 10k\Omega$ ,  $R_3 = 1k\Omega$ , and  $R_4 = 100\Omega$ .

(a) (15%) What is the transfer function from the input voltage  $e$  to the output voltage  $u$ ?

(b) (10%) Sketch the Bode plot of the transfer function found above in (a).

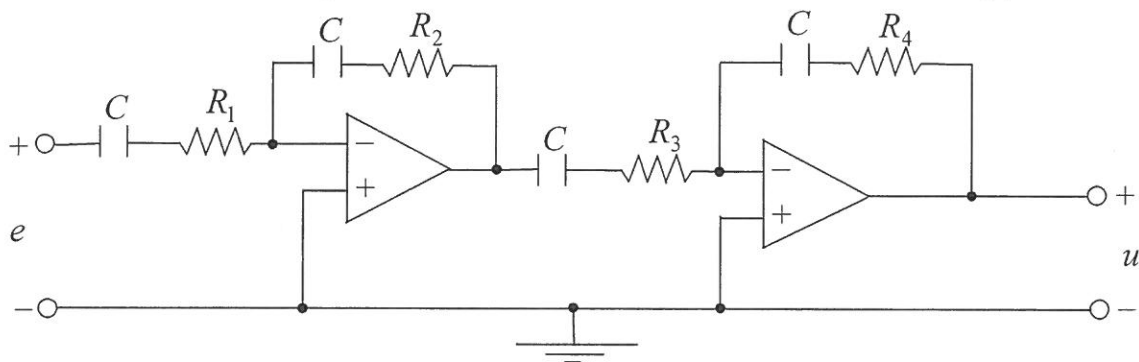


Fig. 4