

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (10%) Fig. 1 shows a rectifier ammeter, which has the following components: PMMC instrument with FSD = 100 μA and $R_m = 0.5 \text{ k}\Omega$; current transformer with $N_s = 400$ and $N_p = 5$; diodes with $V_F \sim 0.6\text{V}$; meter series resistance $R_s = 160 \text{ k}\Omega$; transformer shunt secondary resistance $R_L = 80 \text{ k}\Omega$. (a) Calculate the level of transformer primary current for instrument FSD (in rms). (b) If we want to measure $I_{ac} (\text{rms}) = 1.6\text{A}$, please calculate the value of R_L .

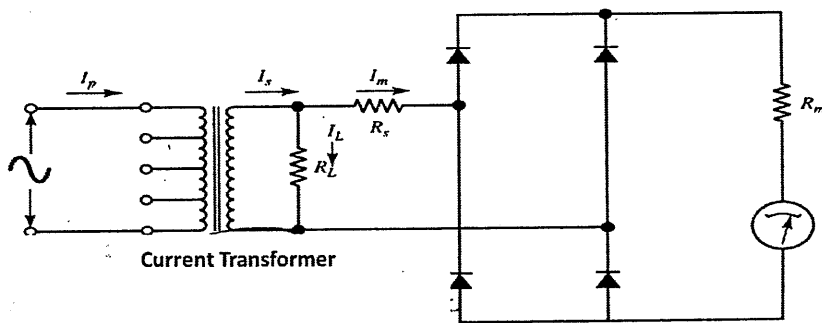


Fig. 1

2. (10%) Explain the terminologies or the difference of the following terms:
 (a) Null measurement; (b) Difference between accuracy and precision; (c) Theoretical errors; (d) What is the difference between Reliability and Repeatability?
3. (20%) A Wheatstone bridge which serves as an ohmmeter is shown in Fig. 2.
 (a) Fig. 3 shows the Thevenin equivalent circuit. Express I_G with V_{RS} , R_m , P , Q , R , and S ($I_G = ?$)
 (b) The relative error of resistor P , Q , and S is 1%, 0.5%, and 1.25%, respectively. What is the relative error of the ohmmeter?
 (c) If the minimal adjustable resistance of resistor S is ΔS , what is the sensitivity defined by resistor S (ΔR_1)?
 (d) Prove that sensitivity ΔR_2 caused by the minimum current of galvanometer could be represent as

$$\Delta R_2 = \frac{\Delta V_{RS}(P + R)^2}{PE - \Delta V_{RS}(P + R)}$$

 (e) What is the sensitivity of this ohmmeter? If E decreases, how will the sensitivity change?

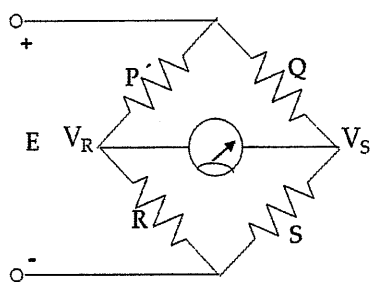


Fig. 2


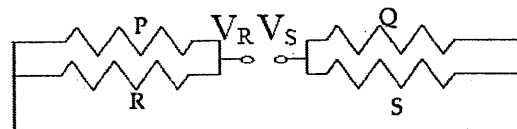
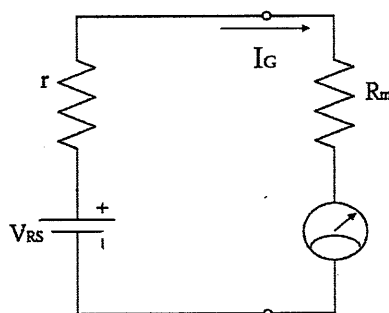


Fig. 3

4. (10%) Derive the equation below for Series-Parallel ohmmeter (with voltage meter) in Fig. 4. The resistance (R_2) is in series with the battery (E) and is parallel connection with the unknown resistance (R_x): (assume $R_2 \ll R_m + R_1$)

Voltage meter

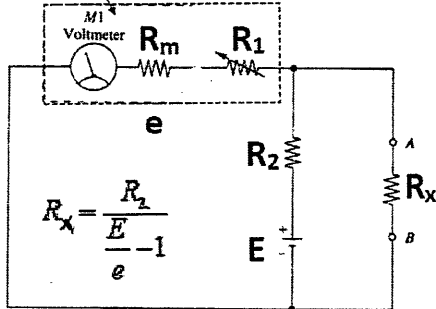

$$R_x = \frac{R_2}{\frac{E}{e} - 1}$$

Fig. 4

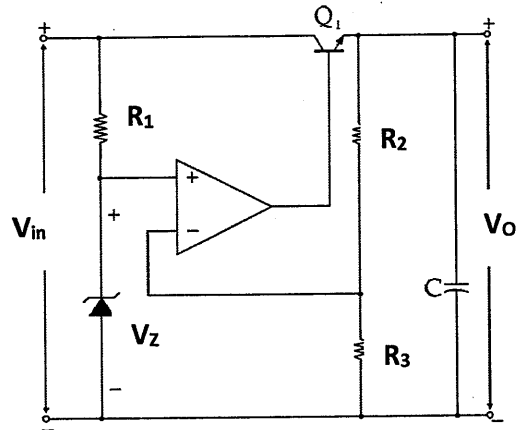


Fig. 5

5. (20%) Fig. 5 shows a voltage regulator, where the input voltage (V_{in}) is 20 V. The breakdown voltage of the Zener diode (V_z) is 4 V when its current is 10 mA, and V_z increases to 4.05 V when its current increases to 20 mA. In addition, $R_2 = 8 \text{ k}\Omega$ and $R_3 = 4 \text{ k}\Omega$.
- (a)(6%) Please calculate the dynamic resistance of the Zener diode (i.e., its equivalent resistance at its quiescent operating point).
- (b)(7%) Please calculate its output voltage (V_o) when the current of the Zener diode is 10 mA.
- (c)(7%) Please calculate the value of R_1 to make $V_z = 4 \text{ V}$.
6. (10%) Fig. 6 shows the block diagram of a Decimal Counting Unit (DCU), and a basic Decimal Counting Assembly (DCA) consists of three DCU elements. Hence, a DCA is 3-bit, and the maximal number that a 3-bit DCA can show is 999. Then, if a digital meter is said to have $3\frac{1}{2}$ bit, what is the maximal number that it can show?
7. (20%) Fig. 7 shows the circuit of an electronic voltage meter, whose input voltage range is 0-5 V. (a) Please describe how to modify it for increasing the input voltage range to 0-10 V. (b) Please describe how to modify it to become an ohmmeter with its reading linearly proportional to the value of measured resistor.

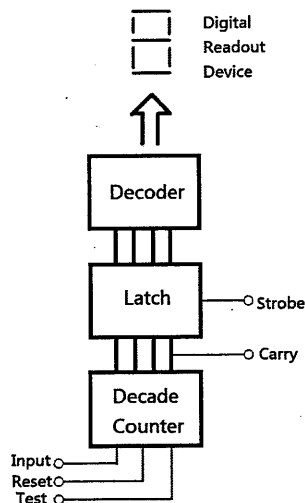


Fig. 6

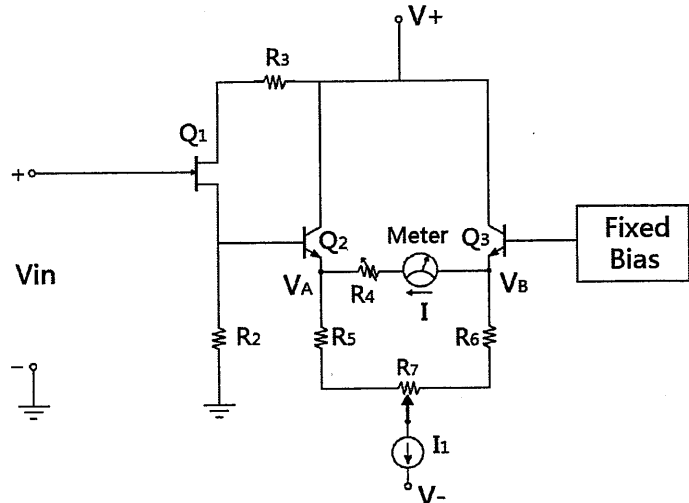


Fig. 7