

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. Consider the folded-cascode amplifier of Fig. 1 for the following case:  $V_{DD}=1.8\text{ V}$ ,  $\mu_p C_{ox}=1/4\mu_n C_{ox}$ , and  $V_{tn}=V_{tp}=0.5\text{ V}$ . To operate  $Q_1$  and  $Q_2$  at equal bias currents  $I$ ,  $I_1=2I$  and  $I_2=I$ . While current source  $I_1$  is implemented using the simple circuit and current source  $I_2$  is realized using a cascoded circuit. The transistor  $W/L$  ratios are selected so that each operates at an overdrive voltage of  $0.2\text{ V}$ . (20%)

- (a) What must the relationship of  $(W/L)_2$  to  $(W/L)_1$  be? (4%)
- (b) What is the minimum dc voltage required across current source  $I_1$  for proper operation? If a  $0.1\text{-V}$  peak-to-peak signal swing is to be allowed at the drain of  $Q_1$ , what is the highest dc bias voltage that can be used at that node? (4%)
- (c) What is the value of  $V_{SG}$  of  $Q_2$ , and hence what is the largest value to which  $V_{G2}$  can be set? (4%)
- (d) What is the minimum dc voltage required across current-source  $I_2$  for proper operation? (4%)
- (e) Given the results of (c) and (d), what is the allowable range of signal swing at the output? (4%)

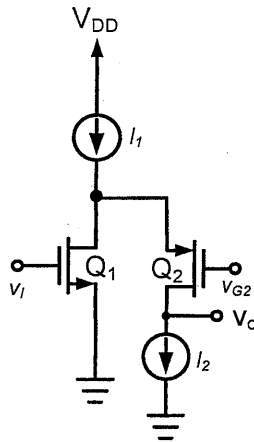


Fig. 1

2. Consider the integrated-circuit CS amplifier in Fig. 2 for the case  $I_{BIAS}=100\ \mu\text{A}$ ,  $Q_2$  and  $Q_3$  are matched, and  $R_{sig}=200\ \text{k}\Omega$ . For  $Q_1$ :  $\mu_n C_{ox}=90\ \mu\text{A}/\text{V}^2$ ,  $|V_A|=12.8\ \text{V}$ ,  $W/L=100\ \mu\text{m}/1.0\ \mu\text{m}$ ,  $C_{gs}=0.2\ \text{pF}$ ,  $C_{gd}=0.015\ \text{pF}$ . For  $Q_2$ :  $|V_A|=19.2\ \text{V}$ . Neglecting the effect of the capacitance inevitably present at the output node. (14%)

- (a) Find the low-frequency gain (5%)
- (b) Find the 3-dB frequency  $f_H$  (5%)
- (c) Find the frequency of the zero  $f_z$  (4%)

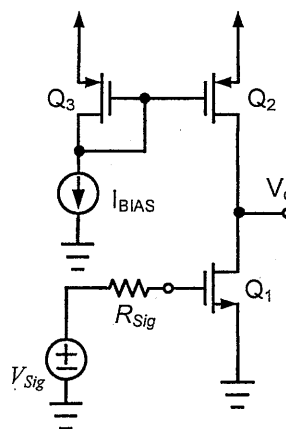


Fig. 2

3. Fig. 3 shows the feedback circuit with the case  $g_{m1}=g_{m2}=2 \text{ mA/V}$ ,  $R_{sig}=200 \text{ k}\Omega$ ,  $R_{D1}=R_{D2}=10 \text{ k}\Omega$ ,  $R_1=1 \text{ k}\Omega$ , and  $R_2=9 \text{ k}\Omega$ . For simplicity, neglect  $r_o$  of each of  $Q_1$  and  $Q_2$ . (16%)

- (a) Find the loop gain  $\beta A$  (4%)
- (b) Find the voltage gain  $V_o/V_s$  (4%)
- (c) Find the input resistance  $R_{in}$  (4%)
- (d) Find the output resistance  $R_{out}$ . (4%)

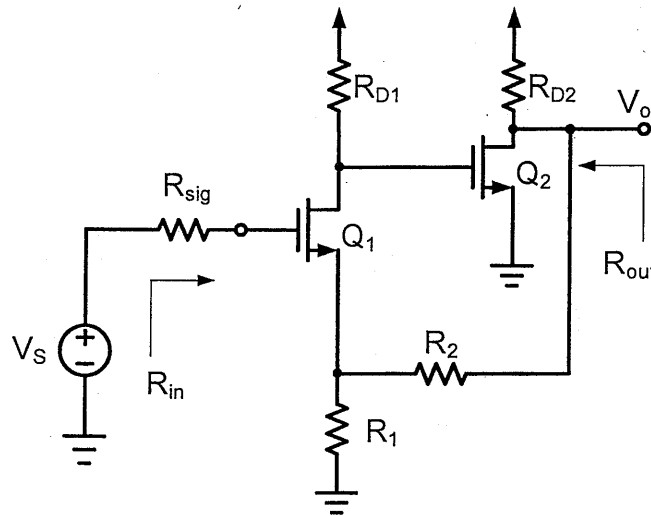


Fig. 3

4. For the Class AB output stage shown in Fig. 4, we know that  $Q_3$  and  $Q_4$  are the major power BJTs which deliver current to load resistance  $R_L$ . Please give your answer and brief explanation for the following questions: (15%)

- (a) In addition to provide two  $V_{BE}$  voltage drop for biasing the  $Q_3$  and  $Q_4$  like the conventional diode-connected biasing circuit does, what is the major advantage of the input stage which consists of  $Q_1$ ,  $Q_2$ ,  $R_1$  and  $R_2$ ? (5%)
- (b) What is the major purpose of the last stage which consists of  $Q_5$ ,  $Q_6$ ,  $R_3$  and  $R_4$ ? (5%)
- (c) What is the major purpose of the resistors  $R_5$  and  $R_6$ ? (5%)

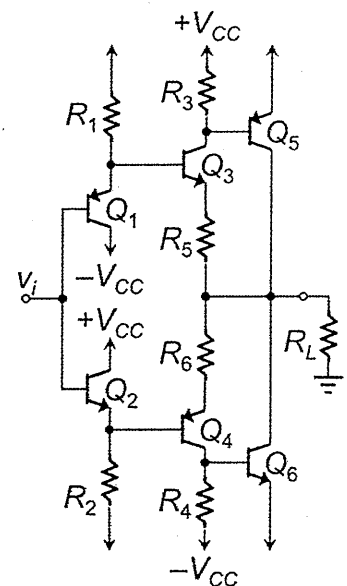


Fig. 4

5. Fig. 5 shows a three-stage feedback amplifier: (20%)

$A_1$  has an 82-k $\Omega$  differential input resistance, a 20-V/V open-circuit differential voltage gain, and a 3.2-k $\Omega$  output resistance.

$A_2$  has a 5-k $\Omega$  input resistance, a 20-mA/V short-circuit transconductance, and a 20-k $\Omega$  output resistance.

$A_3$  has an 20-k $\Omega$  input resistance, unity open-circuit voltage gain, and a 1-k $\Omega$  output resistance.

The feedback amplifier feeds a 1-k $\Omega$  load resistance and is fed by a signal source with a 9-k $\Omega$  resistance.

- (a) If  $R_1 = 20$  k $\Omega$ , find the value of  $R_2$  that results in a closed-loop gain  $V_o/V_s$  that is ideally 5V/V. (4%)
- (b) Find the feedback amplifier's input resistance  $R_{in}$ . (4%)
- (c) Find the feedback amplifier's output resistance  $R_{out}$ . (4%)
- (d) If the high-frequency response of the open-loop gain  $A$  is dominated by a pole at 100Hz, what is the upper 3-dB frequency of the closed-loop gain? (4%)
- (e) If for some reason,  $A_1$  drops to half its nominal value, what is the percentage change in the closed-loop gain  $A_f$ ? (4%)

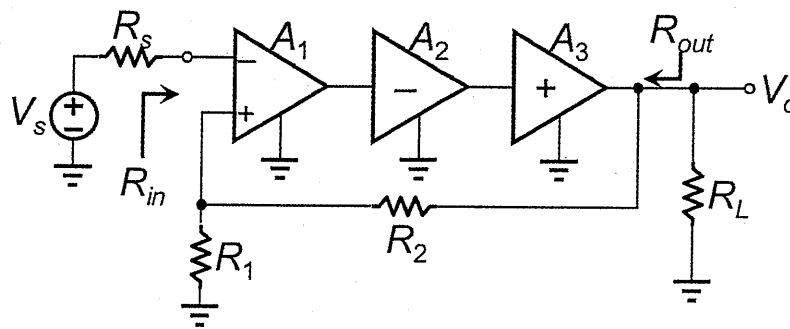


Fig. 5

6. Please analysis and design an oscillator which uses a bistable circuit. (15%)

- (a) Fig. 6. shows a square waveform generator. The positive and negative saturation levels of the op-amp used in the bistable circuit are  $L_+$  and  $L_-$ , respectively. The trigger levels are  $V_+$  and  $V_-$ . If  $V_{\pm} = \beta L_{\pm}$ , derive a relationship between the oscillator period and the time-constant  $\tau = RC$ . (5%)
- (b) Follow 6(a), how to modify the circuit of Fig. 6 to generate a triangular waveform. You are allowed to use one more op amp. (5%)
- (c) Based on the conditions of 6(a), please derive a relationship between the oscillator period and the RC for the circuit you design in 6(b). (5%)

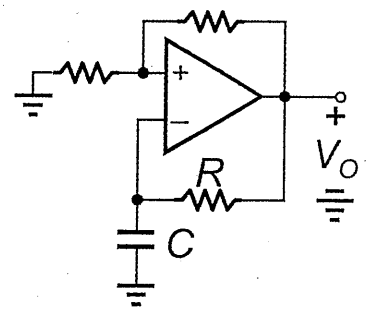


Fig. 6