

# 元智大學 103 學年度研究所 碩士班 招生試題卷

系(所)別： 電機工程學系碩士班      組別： 不分組      科目： 電子學      用紙第 1 頁共 2 頁

●不可使用電子計算機

1. (15%) For the circuit shown in Fig. 1, assume  $\lambda \neq 0$ ,  $V_b$  is DC bias voltage and transconductances of transistors  $M_1$  and  $M_2$  are  $g_{m1}$  and  $g_{m2}$ , respectively. Please derive (a) input impedance (5%), (b) output impedance (5%), and (c) voltage gain of this circuit (5%).
  
2. (15%) For the circuit shown in Fig. 2, assume  $\lambda \neq 0$ ,  $V_b$  is DC bias voltage and transconductances of transistors  $M_1$  and  $M_2$  are  $g_{m1}$  and  $g_{m2}$ , respectively. Please derive (a) input impedance (5%), (b) output impedance (5%), and (c) voltage gain of this circuit (5%).

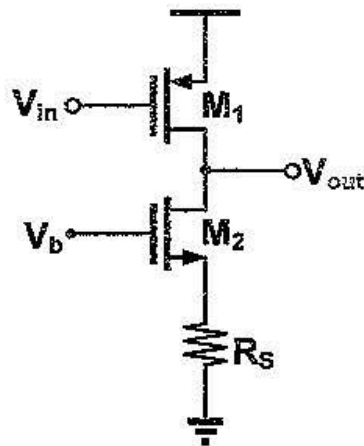


Fig. 1

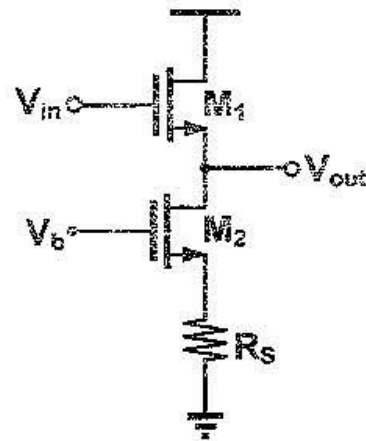


Fig. 2

3. (35%) The amplifier with feedback network is shown in Fig.3. If  $\lambda \neq 0$  and transconductances for the NMOS transistors and PMOS transistors are  $g_{mN}$  and  $g_{mP}$ , please derive
  - [Note:  $R_1 + R_2$  is very large and  $r_{o1} = r_{o2} = r_{o3}$ ,  $r_{o3} = r_{o4} = r_{oP}$ ]
  - (a) What kind of feedback topology is it? (5%)
  - (b) Please derive the open-loop voltage gain? (10%)
  - (c) Please derive the open-loop output impedance? (5%)
  - (d) Please derive the closed-loop voltage gain? (10%)
  - (e) Please derive the closed-loop output impedance? (5%)

**103036**

元智大學 103 學年度研究所 碩士班 招生試題卷

系(所)別： 電機工程學系碩  
士班

組別： 不分組

科目： 電子學

用紙第 2 頁共 2 頁

●不可使用電子計算機

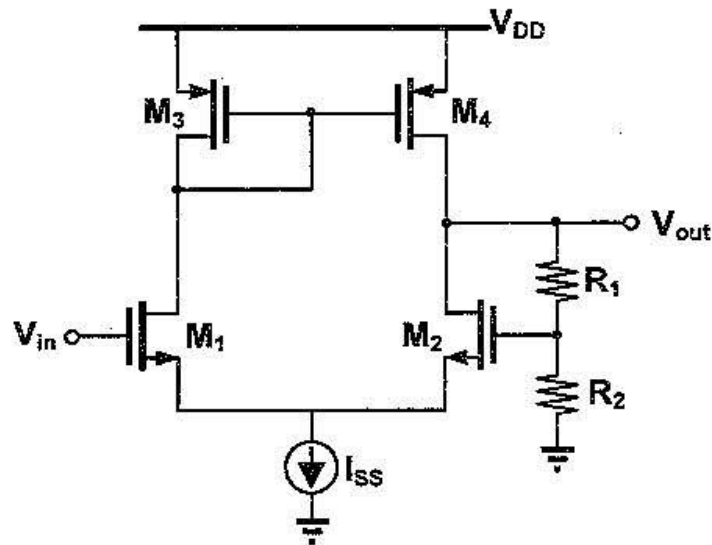


Fig. 3

4. (20%) (a) Please derive the truth table of a set/reset (SR) flip-flop. (5%)  
(b) Please draw a gate-level diagram of the SR flip-flop. (5%) (c)  
Please draw the complementary metal-oxide-semiconductor (CMOS)  
implementation of a clocked SR flip-flop. (5%) (d) Please sketch a  
rough layout of the CMOS implementation of the clocked SR  
flip-flop. (5%)
5. (15%) (a) Please describe the crosstalk effect between adjacent signal  
lines in a digital CMOS implementation. (7%) (b) Please describe the  
leakage power of a MOS circuit. (8%)

103037

