

# 國立臺灣師範大學 112 學年度碩士班招生考試試題

科目：電子學

適用系所：電機工程學系

注意：1.本試題共 4 頁，請依序在答案卷上作答，並標明題號，不必抄題。2.答案必須寫在指定作答區內，否則依規定扣分。

1. (20 points) Figure 1(a) shows an amplifier composed of a cascade of three stages. Each stage is a voltage amplifier, which is modeled as shown in Figure 1(b).

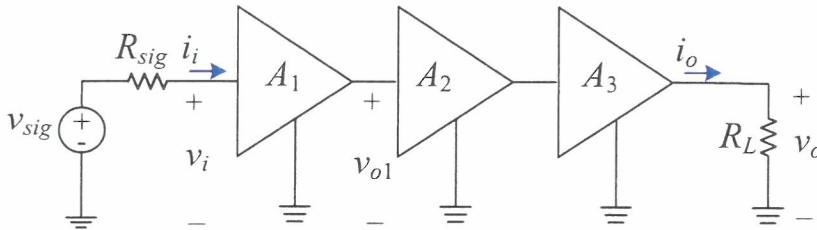


Figure 1(a)

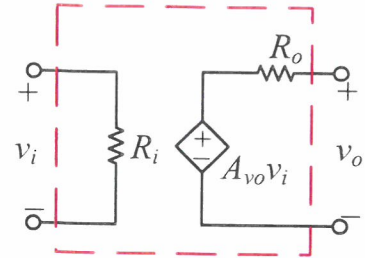


Figure 1(b)

Assume that  $R_{sig} = 20 \text{ k}\Omega$ ,  $R_L = 1 \text{ k}\Omega$ , and the parameters of each amplifier are listed as follows.

Stage	$R_i$	$R_o$	$A_{vo}$
$A_1$	$50 \text{ k}\Omega$	$5 \text{ k}\Omega$	$10 \text{ V/V}$
$A_2$	$20 \text{ k}\Omega$	$10 \text{ k}\Omega$	$20 \text{ V/V}$
$A_3$	$90 \text{ k}\Omega$	$1 \text{ k}\Omega$	$1 \text{ V/V}$

Find  $v_{o1}/v_{sig}$ ,  $v_o/v_i$ ,  $i_o/i_i$ , and the power gain  $P_o/P_i$ .

2. (20 points) Figure 2 shows an amplifier composed by an ideal op Amp.

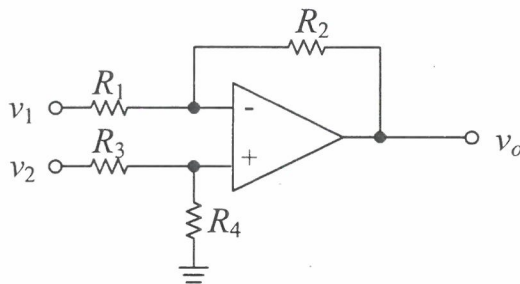


Figure 2

- (1) Assume that  $v_1 = 0 \text{ V}$ ,  $v_2 = 2 \text{ V}$ ,  $R_1 = R_3 = 1 \text{ k}\Omega$ , and  $R_2 = R_4 = 2 \text{ k}\Omega$ . Find  $v_o$ .
- (2) Assume that  $v_1 = 2 \sin(10t) - 0.01 \sin(10^4t) \text{ V}$ ,  $v_2 = 2 \sin(10t) + 0.01 \sin(10^4t) \text{ V}$ . Find  $v_o$  for each case.
  - (a)  $R_1 = R_2 = R_3 = R_4 = 2 \text{ k}\Omega$ .
  - (b)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_3 = 4 \text{ k}\Omega$ , and  $R_4 = 8 \text{ k}\Omega$ .
  - (c)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_3 = 3 \text{ k}\Omega$ , and  $R_4 = 3 \text{ k}\Omega$ .

國立臺灣師範大學 112 學年度碩士班招生考試試題

3. (20 points) Figure 3 shows an amplifier composed by an *npn* bipolar junction transistor.

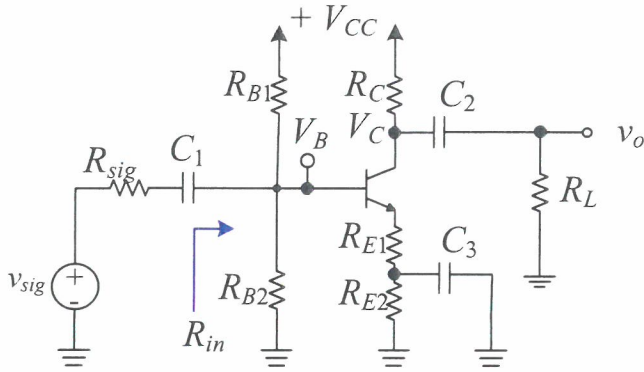


Figure 3

Assume that  $V_{CC} = 10\text{ V}$ ,  $R_{B1} = 60\text{ k}\Omega$ ,  $R_{B2} = 40\text{ k}\Omega$ ,  $R_C = 1\text{ k}\Omega$ ,  $R_{E1} = 200\ \Omega$ ,  $R_{E2} = 800\ \Omega$ ,  $R_{sig} = 10\text{ k}\Omega$ ,  $R_L = 10\text{ k}\Omega$ ,  $V_{BE} = 0.7\text{ V}$ ,  $\beta = 100$ , the thermal voltage  $V_T = 25\text{ mV}$ , and  $r_o = \infty$ .

- (1) Find the dc voltages:  $V_B$  and  $V_C$ .
- (2) Assume that the capacitors  $C_1$ ,  $C_2$ , and  $C_3$  act as a perfect short circuit as far as the signal is concerned. Find the input resistance  $R_{in}$  and the overall voltage gain  $v_o/v_{sig}$ .

# 國立臺灣師範大學 112 學年度碩士班招生考試試題

4. Fig. 4 shows a common-source amplifier biased by an ideal current source  $I$ . Let  $R_{\text{sig}} = R_D = R_L = 50 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $C_{C1} = C_{C2} = 0.1 \text{ }\mu\text{F}$ , and  $C_S = 5 \text{ }\mu\text{F}$ . The NMOS transistor is specified to have  $g_m = 4 \text{ mA/V}$ ,  $C_{gs} = 20 \text{ fF}$ , and  $C_{gd} = 5 \text{ fF}$ . Ignore the channel-length modulation, i.e.,  $\lambda = 0$ .

(a) (10 points) Find the lower 3-dB frequency  $f_L$  using the method of short-circuit time constants.

(b) (10 points) Find the upper 3-dB frequency  $f_H$  using the method of open-circuit time constants.

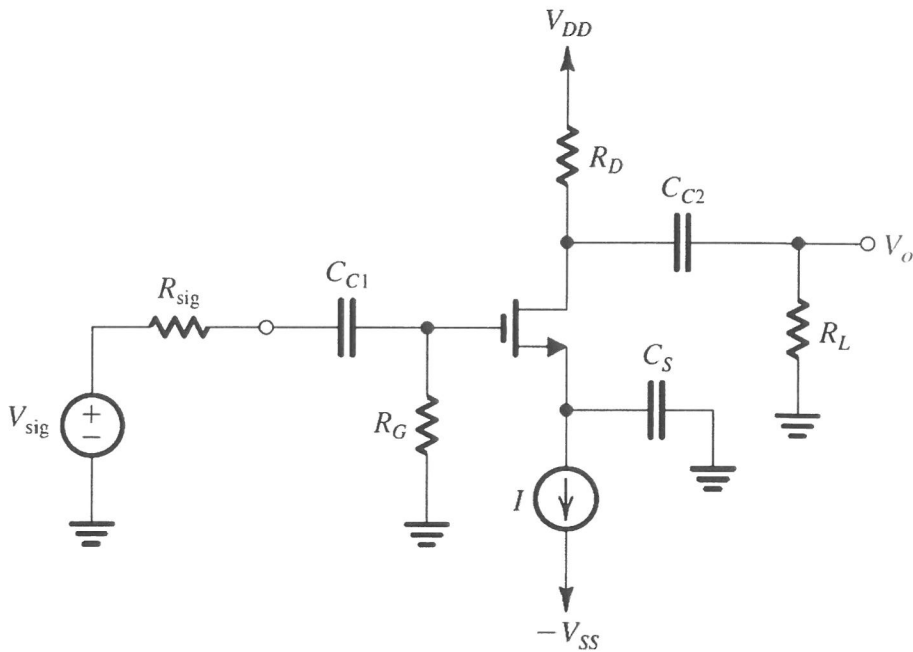


Fig. 4

國立臺灣師範大學 112 學年度碩士班招生考試試題

5. (20 points) The feedback amplifier of Fig. 5 consists of a common-gate amplifier formed by  $Q_1$  and  $R_D$ , and a feedback circuit formed by the capacitive divider ( $C_1$ ,  $C_2$ ) and the common-source transistor  $Q_f$ . Note that the bias circuit for  $Q_f$  is not shown. Assume that  $C_1$  and  $C_2$  are sufficiently small that their loading effect on the common-gate amplifier can be neglected. Also neglect  $r_o$  and body effect. Find the values of  $A_f \equiv V_o/I_s$ ,  $R_{in}$ , and  $R_{out}$  for the case in which  $g_{m1} = 5 \text{ mA/V}$ ,  $g_{mf} = 2 \text{ mA/V}$ ,  $R_D = 10 \text{ k}\Omega$ ,  $C_1 = 0.9 \text{ pF}$ ,  $C_2 = 0.1 \text{ pF}$ .

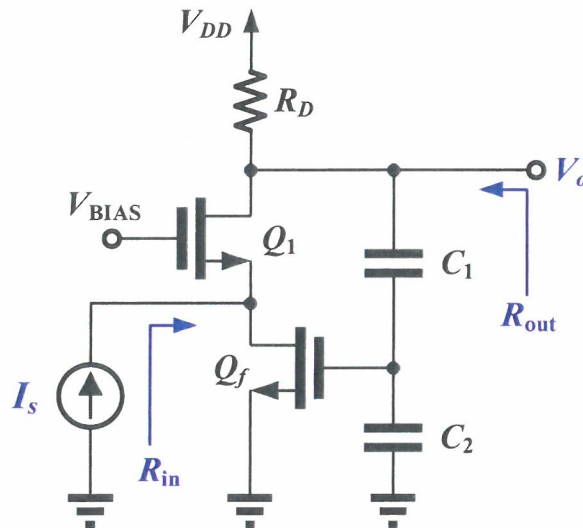


Fig. 5