

國立臺北科技大學 113 學年度碩士班招生考試

系所組別：2240 電子工程系碩士班丁組

第一節 電子學 試題

第 1 頁 共 1 頁

**注意事項：**

1. 本試題共四題，共 100 分。
2. 不必抄題，作答時請將試題題號及答案依照順序寫在答案卷上。
3. 全部答案均須在答案卷之答案欄內作答，否則不予計分。
4. 每題需詳列解題過程，僅寫答案不予計分。

一、(30%) Fig. 1 shows an ideal voltage amplifier having a gain of  $-200V/V$  with an impedance  $Z$  connect between its output and input terminals. The frequency of  $V_{sig}$  is 1 MHz, and  $PI=3.1415$ . (註：各小題答案需四捨五入到小數第一位)

1. Consider the Miller equivalent circuit for Fig. 1 when  $Z$  is a 500-k $\Omega$  resistor. Find the corresponding impedance ( $Z_1$ ) at port 1, corresponding impedance ( $Z_2$ ) at port 2, and gain  $V_o/V_{sig}$ . (15%)
2. Consider the Miller equivalent circuit of Fig. 1 when  $Z$  is a 5-pF capacitor. Find the corresponding impedance ( $Z_1$ ) at port 1, corresponding impedance ( $Z_2$ ) at port 2, and gain  $V_o/V_{sig}$ . (15%)

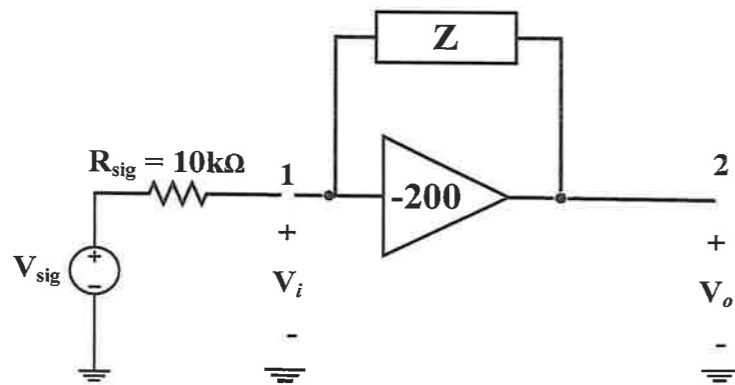


Fig. 1

二、(30%) Fig. 2 shows a common-source amplifier, and all the transistors are in saturation regions.  $W/L = 1.8 \mu m/90 \text{ nm}$  for all transistors,  $k_n' = 35 \mu A/V^2$ ,  $k_p' = 20 \mu A/V^2$ ,  $I_{REF} = 10 \mu A$ ,  $V'_{An} = 5 \text{ V}/\mu m$ , and  $V'_{Ap} = 8 \text{ V}/\mu m$ . (註：各小題答案需四捨五入到小數第一位)

1. Find the overdrive voltage of transistor  $Q_1$ . (5%)
2. Find the  $g_m$  of transistor  $Q_1$ . (5%)
3. Find the  $r_{o1}$  of transistor  $Q_1$ . (5%)
4. Find the  $r_{o2}$  of transistor  $Q_2$ . (5%)
5. Find the output resistance of the amplifier. (5%)
6. Find the voltage gain ( $v_o/v_i$ ) of the amplifier. (5%)

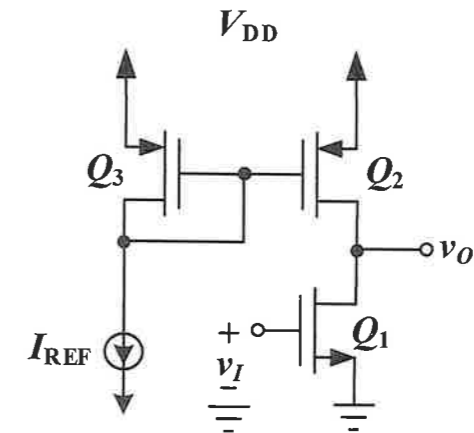


Fig. 2

三、(30%) Follow the above questions and analyze the amplifier in Fig. 2. For  $Q_1$ ,  $C_{gs}=30\text{fF}$ ,  $C_{gd}=10\text{fF}$ ,  $C_L=20\text{fF}$ , and  $R_{sig} = 10\text{k}\Omega$ , Assume the  $C_L$  includes all the capacitance introduced by  $Q_2$  at the output node. (註：各小題答案需四捨五入到小數第一位)

1. Find the overall input capacitance  $C_{in}$  by using Miller theorem. (5%)
2. Find the 3-dB frequency  $f_H$  of the amplifier by using Miller's theorem. (5%)
3. Find the time constant  $\tau_{gs}$ . (5%)
4. Find the time constant  $\tau_{gd}$ . (5%)
5. Find the time constant  $\tau_{CL}$ . (5%)
6. Find the 3-dB frequency  $f_H$  of the amplifier by the using open-circuit time constants method. (5%)

四、(10%) For a junction diode, the relationship of diode current  $i$  and diode voltage  $v$  is given in equation (1).

$$i = I_s e^{v/V_T} \tag{1}$$

where  $V_T=25.3 \text{ mV}$ ,  $I_s = 6.9 \times 10^{-13} \text{ A}$ . For a decade change in current, find the voltage change. (註：答案需四捨五入到小數第一位)