

國立成功大學

114學年度碩士班招生考試試題

編 號：123

系 所：電機工程學系

科 目：電路學

日 期：0210

節 次：第 1 節

注 意：1. 可使用計算機
2. 請於答案卷(卡)作答，於
試題上作答，不予計分。

1. In the ideal autotransformer circuit of Fig. 1, the load impedance Z_L is adjusted until it absorbs the maximum average power. Assume $V_s = 120\angle 0^\circ$ Vrms, $Z_s = 75 + j125 \Omega$, $N_1 = 600$ turns, and $N_2 = 200$ turns. Find Z_L and the maximum average power delivered to it. (25%)

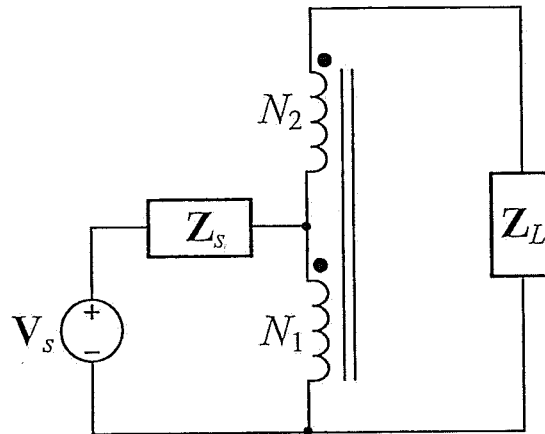


Fig. 1.

2. A special-design winding is modeled as a series combination of an inductance L_b and a resistance R_b , as shown in Fig. 2. Since an AC voltmeter measures only the effective value of a sinusoid, the following measurements are taken at 60 Hz when the circuit operates under a steady-state condition: $|V_s| = 145$ V, $|V_a| = 50$ V, and $|V_b| = 110$ V. Assume $R_a = 80 \Omega$. Use these measurements to determine the values of L_b and R_b . (25%)

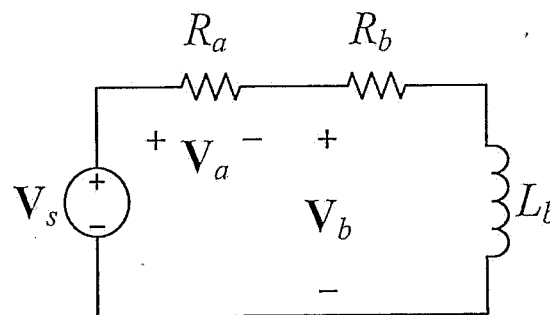


Fig. 2.

3. A mechanical system is modeled by a series RLC circuit. It is desired to produce an overdamped response with the time constants of 0.1 ms and 0.5 ms. If a series resistor of 120Ω is used, find the values of L and C . (25%)
4. A certain band-limited periodic current has only three frequencies in its Fourier series representation: DC, 50 Hz, and 100 Hz. The current may be represented as $i(t) = 4 + 6\sin 100(\pi t) + 8\cos(100\pi t) - 3\sin(200\pi t) - 4\cos(200\pi t)$ A. (1) Express the current $i(t)$ in amplitude-phase form. (2) If the current $i(t)$ flows through a resistor of 200Ω , determine the average power dissipated on it. (25%)