

國立中正大學

114 學年度碩士班招生考試

試題

[第 4 節]

科目名稱	電子學
系所組別	電機工程學系- 電磁晶片組 計算機工程組 晶片系統組

—作答注意事項—


※作答前請先核對「試題」、「試卷」與「准考證」之系所組別、科目名稱是否相符。

1. 預備鈴響時即可入場，但至考試開始鈴響前，不得翻閱試題，並不得書寫、畫記、作答。
2. 考試開始鈴響時，即可開始作答；考試結束鈴響畢，應即停止作答。
3. 入場後於考試開始 40 分鐘內不得離場。
4. 全部答題均須在試卷（答案卷）作答區內完成。
5. 試卷作答限用藍色或黑色筆（含鉛筆）書寫。
6. 試題須隨試卷繳還。

1. (20%) For an operation in triode region, the NMOS transistor is biased with $v_{DS}=0.3V$, it conducts $48\mu A$ for $v_{GS}=2V$ and $96\mu A$ for $v_{GS}=3V$, respectively.
- (5%) What is the possible threshold voltage V_{TN} ?
 - (5%) This transistor is manufactured by $0.18\mu m$ process technology and the related $k_n' (= \mu_n C_{ox})$ is $20\mu A/V^2$, what is the aspect ratio (W/L) for it?
 - (5%) How much current can be expected to flow through it with $v_{GS}=2.85V$ and $v_{DS}=0.25V$?
 - (5%) If the device operates at $v_{DS}=2V$, for what value of v_{GS} will the drain-end of the MOSFET channel just become pinch-off.

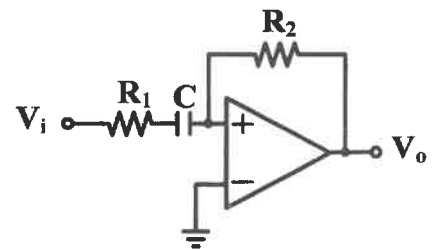
2. (20%) As shown in the right-hand-side OP-amp circuit,

- (5%) Does it behave like low-pass or high-pass? Please show it by deriving the transfer function.
- (5%) What's the high frequency gain?
- (5%) What's the 3-dB frequency?
- (5%) At what frequency does the magnitude of high frequency gain reduce to unity?




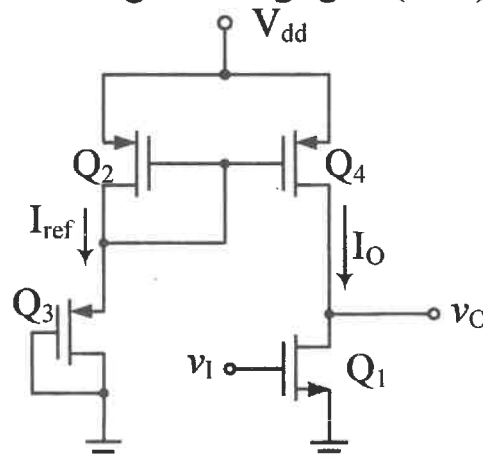3. (20%) A MOSFET amplifier with active load is biased with $V_{dd} = 3V$. The transistor parameters are $V_{TN} = 0.5V$, $V_{TP} = -0.5V$, $k_n' = 100\mu A/V^2$, $k_p' = 50\mu A/V^2$, and $\lambda_n = \lambda_p = 0.02V^{-1}$. The quiescent values are $V_O = 1.5V$ and $V_I = 1.2V$. Q_2 and Q_4 are identical.

- (5%) Taking the channel length modulation effect into considerations to design the required W/L ratio of Q_1 , Q_2 , Q_4 and Q_3 such that $I_O = I_{ref} = 100\mu A$.
- (5%) Please calculate the output resistances (r_{o1} and r_{o4}) of Q_1 and Q_4 .
- (5%) Please calculate the transconductance g_{m1} of Q_1 .
- (5%) Determine the small-signal voltage gain (v_O/v_I).



- 4 (20%) A differential amplifier using a $1\text{k}\Omega$ resistor R_{SS} to establish a 1mA dc biased current. The transistors Q_1 and Q_2 are with the properties of $k'_n (W/L) = 4\text{mA/V}^2$, $V_{TN}=0.8\text{V}$. Skip the channel length modulation effect.
- (5%) Define the required value of V_{CM} .
 - (5%) Define the value of R_D so as to get a differential gain A_d of 10 V/V .
 - (5%) What's the drain voltage over Q_1 .
 - (5%) Determine the common-mode gain $\Delta V_{D1}/\Delta V_{CM}$.

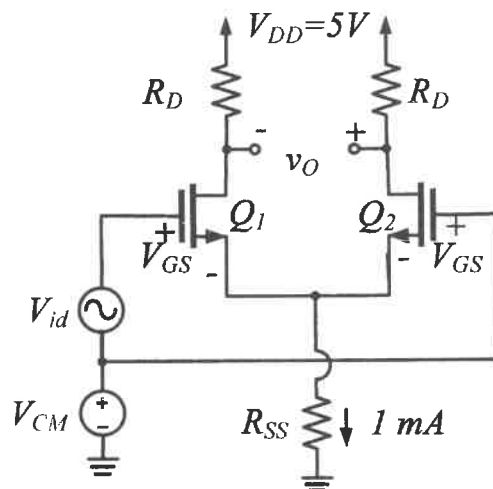

- 5 (20%) A feedback transresistance amplifier utilizes two identical MOSFETs biased by an ideal current sources $I = 0.4\text{ mA}$. The MOSFETs are sized to operate at $V_{OV} = 0.2\text{ V}$ and have $V_{TN} = 0.5\text{ V}$ and $V_A = 16\text{ V}$. The feedback resistance $R_F = 10\text{ k}\Omega$.
- (5%) What's the dc voltage at the input of Q_1 ?
 - (5%) What are g_m and r_o of Q_1 and Q_2 ?
 - (5%) Derive the open-loop gain in terms of g_{m1} , r_{o1} , g_{m2} , r_{o2} and R_F
 - (5%) Please express the gain-with-feedback (A_f)

